


**Homework Assignment No. 2 – Solutions****11.16**

$$g_{11} = \left. \frac{i_1}{v_1} \right|_{i_2=0} : v_1 = 10^4 i_1 + 101 i_1 (240\text{k}\Omega) \rightarrow g_{11} = 4.124 \times 10^{-8} \text{ S} = 4.12 \times 10^{-8} \text{ S}$$

$$g_{12} = \left. \frac{i_1}{i_2} \right|_{v_1=0} : i_1 = -\frac{240\text{k}\Omega}{240\text{k}\Omega + 10\text{k}\Omega} (i_2 + 100i_1) \rightarrow g_{12} = -9.90 \times 10^{-3}$$

$$g_{21} = \left. \frac{v_2}{v_1} \right|_{i_2=0} : v_2 = 101 i_1 (240\text{k}\Omega) \mid i_1 = g_{11} v_1 \rightarrow g_{21} = 1.00$$

$$g_{22} = \left. \frac{v_2}{i_2} \right|_{v_1=0} : i_2 = \frac{v_2}{240\text{k}\Omega} + \frac{v_2}{10\text{k}\Omega} + 100 \frac{v_2}{10\text{k}\Omega} \rightarrow g_{22} = 99.0 \text{ } \Omega$$

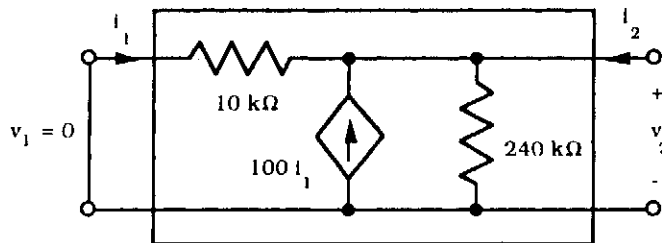**11.34**

$$V_O = V_S \frac{R_{IN}}{R_{IN} + R_S} A \frac{R_{IN}}{R_{IN} + R_{OUT}} A \frac{R_L}{R_L + R_{OUT}}$$

$$A_V = \frac{5000}{5000 + 1000} (-1000) \frac{5000}{5000 + 250} (-1000) \frac{100}{100 + 250} = +2.27 \times 10^5$$

$$A_I = \frac{I_O}{I_S} = \frac{2.27 \times 10^5 V_S}{100} \frac{1}{\frac{V_S}{6000}} = +1.36 \times 10^7$$

$$A_P = \frac{2.27 \times 10^5 V_S (+1.36 \times 10^7 I_S)}{V_S I_S} = +3.09 \times 10^{12}$$

**11.37**


$$A_V = \frac{2\pi \times 10^7 s}{(s + 20\pi)(s + 2\pi \times 10^4)} = \frac{1000s}{(s + 20\pi) \left(1 + \frac{s}{2\pi \times 10^4}\right)} \mid A_{mid} = +1000 = 60 \text{ dB}$$

$$f_L = \frac{20\pi}{2\pi} = 10 \text{ Hz} \mid f_H = \frac{2\pi \times 10^4}{2\pi} = 10 \text{ kHz} \mid \text{BW} = 10\text{kHz} - 10\text{Hz} = 9.99 \text{ kHz}$$

Bandpass Amplifier

**11.43**

Using MATLAB: `n=[2e7*pi 0]; d=[1 (20*pi+2e4*pi) 40e4*pi^2]; bode(n,d)`

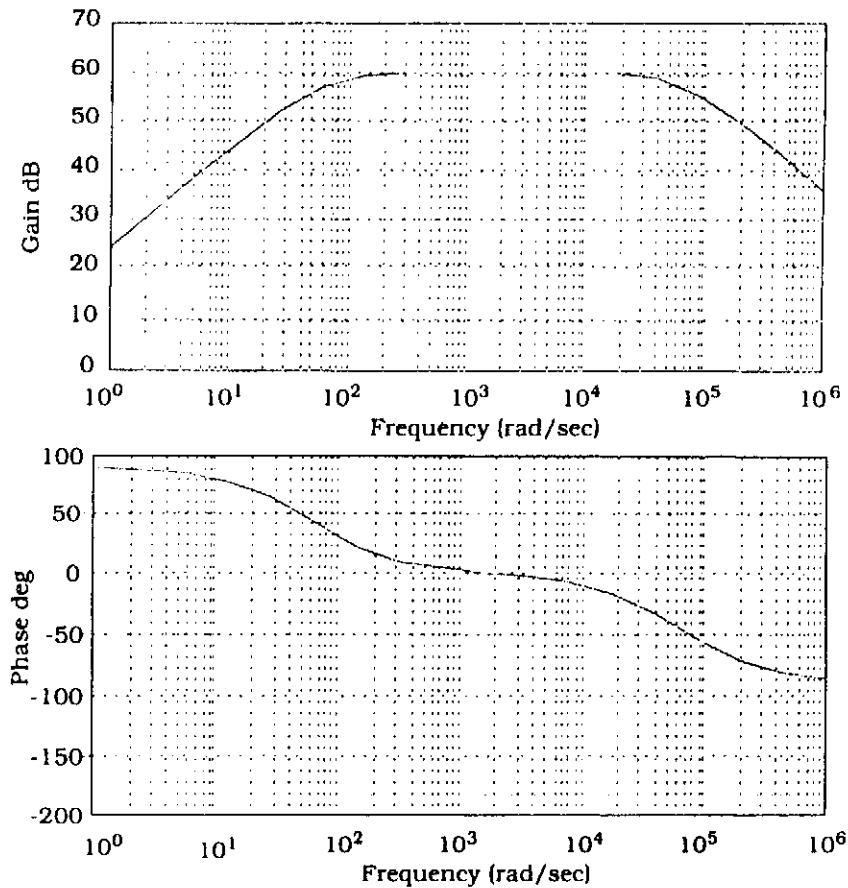**11.55**

$$(a) A_{mid} = +10^{\frac{20}{20}} = +10 \quad | \quad A_V = \frac{10}{1 + \frac{s}{2\pi \times (5 \times 10^6)}} = \frac{10}{1 + \frac{s}{10^7 \pi}} = \frac{10^8 \pi}{s + 10^7 \pi}$$

$$(b) A_{mid} = -10^{\frac{20}{20}} = -10 \quad | \quad A_V = -\frac{10^8 \pi}{s + 10^7 \pi}$$

Problem 6

(a.) Find  $V_{out}(s)/V_{in}(s)$  and identify the numerical value of the midband gain and all poles and zeros if  $g_m$  is 1mA/V.

$$\frac{V_{out}}{V_{in}} = \left( \frac{V_{out}}{V_1} \right) \left( \frac{V_1}{V_{in}} \right) = \left( \frac{g_m R_2 R_3}{R_2 + R_3 + \frac{1}{sC_1}} \right) \left( \frac{V_1}{V_{in}} \right)$$

$$V_1 = V_{in} - V_{R2} \rightarrow V_1 = V_{in} - \frac{g_m V_1 R_2 \left( R_3 + \frac{1}{sC_1} \right)}{R_2 + R_3 + \frac{1}{sC_1}} \rightarrow \frac{V_1}{V_{in}} = \frac{1}{1 + \frac{g_m R_2 \left( R_3 + \frac{1}{sC_1} \right)}{R_2 + R_3 + \frac{1}{sC_1}}}$$

$$\therefore \frac{V_{out}}{V_{in}} = \left( \frac{g_m R_2 R_3}{R_2 + R_3 + \frac{1}{sC_1}} \right) \left( \frac{R_2 + R_3 + \frac{1}{sC_1}}{R_2 + R_3 + \frac{1}{sC_1} + g_m R_2 \left( R_3 + \frac{1}{sC_1} \right)} \right)$$

$$= \frac{(g_m R_2 R_3) s}{s(R_2 + R_3 + g_m R_2 R_3) + \frac{1 + g_m R_2}{C_1}} = \left( \frac{\frac{g_m R_2 R_3}{R_2 + R_3}}{1 + \frac{g_m R_2 R_3}{R_2 + R_3}} \right) \left( \frac{s}{s + \frac{1 + g_m R_2}{C_1 (R_2 + R_3 + g_m R_2 R_3)}} \right)$$

$$\therefore \text{MBG} = \frac{\frac{g_m R_2 R_3}{R_2 + R_3}}{1 + \frac{g_m R_2 R_3}{R_2 + R_3}} = \frac{5}{6}$$

$$\begin{array}{l} \text{Zero at } s = 0 \\ \text{Pole at } s = \frac{-(1 + g_m R_2)}{C_1 (R_2 + R_3 + g_m R_2 R_3)} = -91.67 \text{ rads/sec.} \end{array}$$

(b.) The asymptotic magnitude plot for  $\frac{V_{out}(s)}{V_{in}(s)} = \frac{100 s}{s+100}$  is shown below.

