

**Homework Assignment No. 8 -Solutions**


**15.9** Note that the dc equivalent circuits are identical for  $Q_1$  and  $Q_2$ .

$$V_{EQ} = \frac{180\text{k}\Omega}{180\text{k}\Omega + 300\text{k}\Omega} 15\text{V} = 5.63\text{V} \quad | \quad R_{EQ} = 180\text{k}\Omega \parallel 300\text{k}\Omega = 113\text{ k}\Omega$$

$$I_B = \frac{5.63 - 0.7}{113 + 101(20)} \frac{\text{V}}{\text{k}\Omega} = 2.31\mu\text{A} \quad | \quad I_C = 100I_{B1} = 232\mu\text{A} \quad | \quad I_E = 101I_{B1} = 234\mu\text{A}$$

$$V_{CE} = 15 - 2 \times 10^4 I_E - 2 \times 10^4 I_C = 5.71\text{V}$$

$$r_{\pi} = \frac{100(0.025\text{V})}{232\mu\text{A}} = 10.8\text{k}\Omega \quad | \quad r_o = \frac{(70 + 5.71)\text{V}}{232\mu\text{A}} = 326\text{k}\Omega \quad - \text{Neglected}$$

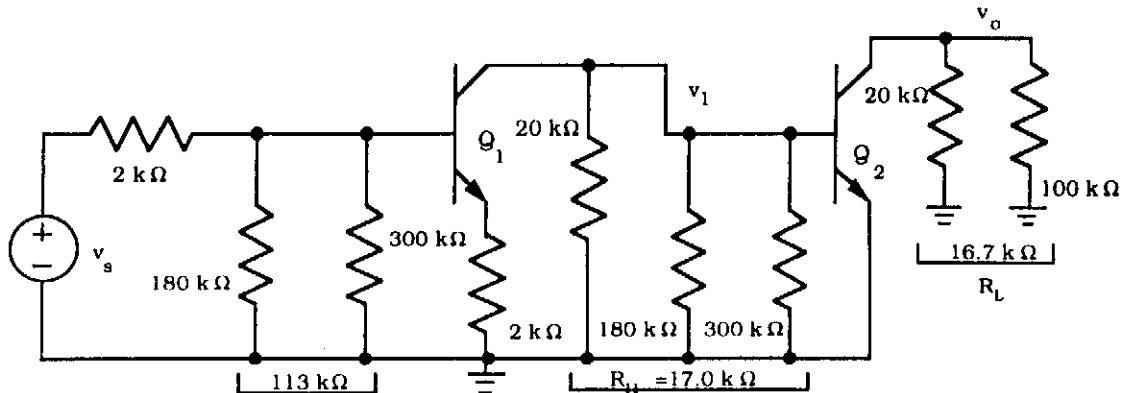

$$v_{th} = v_s \frac{113\text{k}\Omega}{113\text{k}\Omega + 2\text{k}\Omega} = 0.983v_s \quad | \quad R_{th} = 113\text{k}\Omega \parallel 2\text{k}\Omega = 1.97\text{k}\Omega$$

$$\frac{v_1}{v_s} = -0.983 \frac{\beta_{o1}(R_{I1} \parallel r_{\pi 2})}{R_{th} + r_{\pi 1} + (\beta_{o1} + 1)R_5} = -0.983 \frac{100(17\text{k}\Omega \parallel 10.8\text{k}\Omega)}{1.97\text{k}\Omega + 10.8\text{k}\Omega + (101)2\text{k}\Omega} = -3.02v_s$$

$$\frac{v_o}{v_1} = -g_{m2}R_L \quad | \quad R_L = 100\text{k}\Omega \parallel 20\text{k}\Omega = 16.7\text{k}\Omega \quad | \quad \frac{v_o}{v_1} = -40(232\mu\text{A})(16.7\text{k}\Omega) = -154v_1$$

$$A_v = \frac{v_o}{v_s} = (-3.02)(-154) = +465 \quad | \quad R_{OUT} = 20\text{k}\Omega \parallel r_{o2} \approx 20\text{k}\Omega$$

$$R_{IN} = R_{B1} \parallel (r_{\pi 1} + (\beta_{o1} + 1)R_5) = 113\text{k}\Omega \parallel [10.8\text{k}\Omega + (101)2\text{k}\Omega] = 73.8\text{k}\Omega$$

**15.14**

$$I_{C1} = 80 \frac{0.7 - (-9)}{100 + 81(24)} \frac{\text{V}}{\text{k}\Omega} = 325\mu\text{A} \quad | \quad V_{EQ2} = 9 - 9100I_{C1} = 6.04\text{V} \quad | \quad R_{EQ2} = 9.1\text{k}\Omega$$


$$I_{C2} = 80 \frac{9 - 0.7 - 6.04}{9.1 + 81(12)} \frac{\text{V}}{\text{k}\Omega} = 184\mu\text{A} \quad | \quad V_{C1} = 9 - 9.1\text{k}\Omega(I_{C1} - I_{B2}) = 6.06\text{V}$$

$$V_{E1} = -9 + I_{E1}(24\text{k}\Omega) = -1.10\text{V} \quad | \quad V_{CE1} = 6.06 - (-1.10) = 7.16\text{V}$$

$$V_{C2} = -9 + I_{C2}(43\text{k}\Omega) = -1.09\text{V} \quad | \quad V_{E2} = V_{C1} + 0.7 = 6.76\text{V} \quad | \quad V_{EC2} = 7.85\text{V}$$

$$Q_1: (325\mu\text{A}, 7.16\text{V}) \quad Q_2: (184\mu\text{A}, 7.85\text{V})$$

5.14 - Cont'd

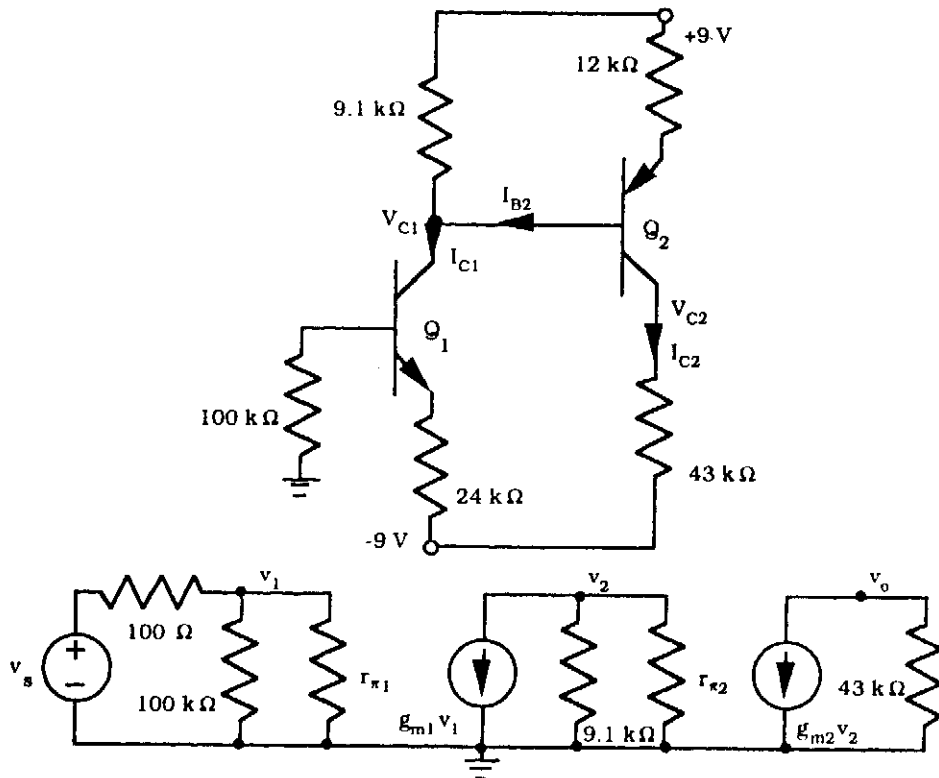

$$g_{m1} = 40(325\mu\text{A}) = 13.0\text{mS} \quad | \quad r_{\pi 1} = \frac{80}{13.0\text{mS}} = 6.15\text{k}\Omega$$

$$g_{m2} = 40(184\mu\text{A}) = 7.36\text{mS} \quad | \quad r_{\pi 2} = \frac{80}{7.36\text{mS}} = 10.9\text{k}\Omega$$


$$v_{th} = v_s \frac{100\text{k}\Omega}{100\Omega + 100\text{k}\Omega} = 0.999v_s \quad | \quad R_{th} = 100\text{k}\Omega \parallel 100\Omega = 99.9\Omega$$

$$v_o = -g_{m2}R_{C2}v_2 = -(7.36\text{mS})(43\text{k}\Omega)v_2 = -317v_2$$

$$v_2 = -v_{th} \frac{80(R_{C1} \parallel r_{\pi 2})}{R_{th} + r_{\pi 1}} = -0.999v_s \frac{80(9.1\text{k}\Omega \parallel 10.9\text{k}\Omega)}{99.9\Omega + 6.15\text{k}\Omega} = -63.5v_s$$

$$A_v = \frac{v_o}{v_s} = -317(-63.5) = +2.01 \times 10^4 \quad \text{or} \quad 86.1\text{ dB}$$

**15.17** dc equivalent circuit:

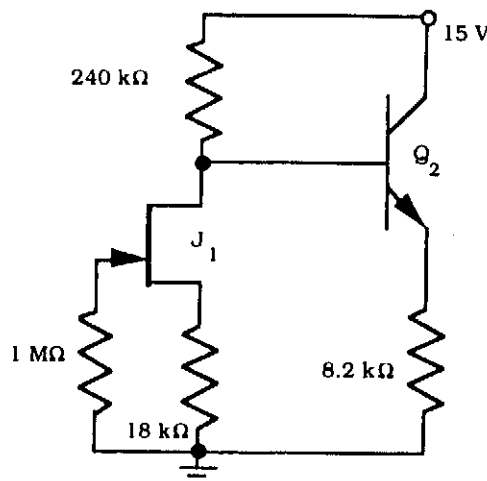

We assume saturation for \$J\_1\$ and forward-active region operation for \$Q\_2\$.

## Problem 15.17 - Continued


$$I_{DS1} = I_{DSS} \left( 1 - \frac{V_{GS1}}{V_P} \right)^2 \quad | \quad I_{DS1} = 0.005 \left( 1 - \frac{-18000 I_{DS1}}{-1} \right)^2 \rightarrow I_{DS1} = 50 \mu\text{A}$$

$$V_{EQ2} = 15 - I_{DS1}(240\text{k}\Omega) = 3.00\text{V} \quad | \quad R_{EQ2} = 240\text{k}\Omega \quad | \quad I_{C2} = 100 \frac{3 - 0.7}{240 + 101(8.2)} \frac{\text{V}}{\text{k}\Omega} = 215 \mu\text{A}$$

$$V_{CE2} = 15 - 8200 I_{E2} = 13.2\text{V} \quad | \quad \text{Checking } V_{DS1}: V_{D1} = 15 - (50 + 2.15)(\mu\text{A})(240\text{k}\Omega) = 2.48\text{V}$$

$$V_{DS1} = 2.48 - (50\mu\text{A})(18\text{k}\Omega) = 1.58\text{V} \quad | \quad V_{GS1} - V_P = -(50\mu\text{A})(18\text{k}\Omega) + 1 = 0.1\text{V} \rightarrow M_1 \text{ is saturated.}$$

ac equivalent circuit:

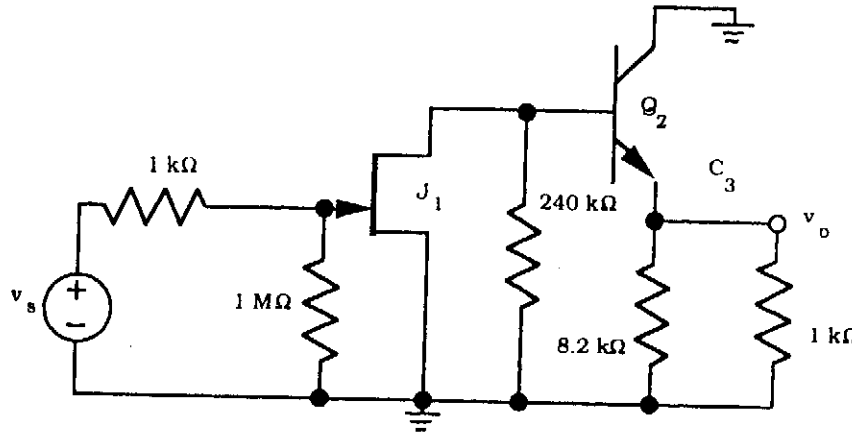

$$g_{m1} = \frac{2}{|-1|} \sqrt{(5\text{mA})50\mu\text{A}} = 1.00\text{mS} \quad | \quad r_{\pi 2} = \frac{100(0.025\text{V})}{215\mu\text{A}} = 11.6\text{k}\Omega$$

$$A_{V1} = \frac{v_1}{v_s} = -\frac{10^6}{10^6 + 10^3} g_{m1} R_{L1} = -\frac{10^6}{10^6 + 10^3} g \left[ R_{D1} \parallel (r_{\pi 2} + (\beta_{o2} + 1)R_{L2}) \right]$$

$$R_{L2} = R_{E2} \parallel R_L = 8.2\text{k}\Omega \parallel 1\text{k}\Omega = 891\Omega \quad | \quad A_{V1} = (-1.00\text{mS}) \left[ 240\text{k}\Omega \parallel (11.6\text{k}\Omega + 101(891\Omega)) \right] = -71.4$$

$$A_{V2} = \frac{v_o}{v_1} = +\frac{101(0.891\text{k}\Omega)}{11.6\text{k}\Omega + 101(0.891\text{k}\Omega)} = 0.886 \quad | \quad A_V = -71.4(0.866) = -63.2 \quad | \quad R_{IN} = 1\text{M}\Omega$$

$$R_{OUT} = R_{E2} \parallel \frac{R_{th2} + r_{\pi 2}}{\beta_{o2} + 1} = 8.2\text{k}\Omega \parallel \frac{240\text{k}\Omega + 11.6\text{k}\Omega}{101} = 8.2\text{k}\Omega \parallel 2.49\text{k}\Omega = 1.91\text{k}\Omega$$

Note:  $R_{OUT}$  and  $A_V$  would be lower if  $r_{o1}$  were also included.

$$(b) A_{V1} = \frac{v_1}{v_s} = -\frac{10^6}{10^6 + 10^3} \frac{g_{m1} R_{L1}}{1 + g_{m1} R_S}$$

$$A_{V1} = -0.999 \frac{(1.00\text{mS}) \left[ 240\text{k}\Omega \parallel (11.6\text{k}\Omega + 101(0.891\text{k}\Omega)) \right]}{1 + (1.00\text{mS})(18\text{k}\Omega)} = -3.75$$

$$A_{V2} = \frac{v_o}{v_1} = +\frac{101(0.891\text{k}\Omega)}{11.6\text{k}\Omega + 101(0.891\text{k}\Omega)} = 0.886 \quad | \quad A_V = -3.75(0.866) = -3.25$$

**15.30**

$$(a) I_C = \alpha_F I_E = \frac{1}{2} \frac{\beta_F}{\beta_F + 1} \frac{12 - V_{BE}}{R_{EE}} = \frac{1}{2} \frac{100}{101} \frac{12 - 0.7}{2.7 \times 10^5} = 20.7 \mu\text{A} \quad | \quad V_C = 12 - 3.3 \times 10^5 I_C = 5.17\text{V}$$

$$V_{CE} = V_C - (-0.7\text{V}) = 5.87\text{V} \quad | \quad Q\text{-Point} = (20.7 \mu\text{A}, 5.87\text{V})$$

$$(b) A_{dd} = -g_m R_C = -40(20.7 \mu\text{A})(330\text{k}\Omega) = -273$$

$$R_{ID} = 2r_\pi = 2 \frac{\beta_o V_T}{I_C} = 2 \frac{100(0.025\text{V})}{20.7 \mu\text{A}} = 243 \text{ k}\Omega \quad | \quad R_{OD} = 2R_C = 660 \text{ k}\Omega$$

$$(c) A_{cc} = -\frac{\beta_o R_C}{r_\pi + (\beta_o + 1)2R_{EE}} = -\frac{100(330\text{k}\Omega)}{122\text{k}\Omega + 2(101)270\text{k}\Omega} = -0.604$$

$$A_{dd} = -\frac{g_m R_C}{2} = -137 \quad | \quad A_{cd} = A_{cc} \quad | \quad \text{CMRR} = \left| \frac{-137}{-0.604} \right| = 227$$

$$R_{IC} = \frac{r_\pi + (\beta_o + 1)2R_{EE}}{2} = \frac{122\text{k}\Omega + 2(101)270\text{k}\Omega}{2} = 27.3 \text{ M}\Omega$$

**15.52**

$$2I_S = \frac{12 - V_{GS}}{220\text{k}\Omega} \Rightarrow 2 \frac{K_n}{2} (V_{GS} - V_{TN})^2 = \frac{12 - V_{GS}}{220\text{k}\Omega} \quad \text{and for } K_n = 400 \frac{\mu\text{A}}{\text{V}^2} \text{ and } V_{TN} = 1\text{V}$$

$$12 - V_{GS} = 88(V_{GS}^2 - 2V_{GS} + 1) \quad \text{or } 88V_{GS}^2 - 175V_{GS} + 76 = 0 \quad \text{and } V_{GS} = 1.348\text{V}$$

$$I_D = I_S = \frac{1}{2} \left( \frac{12 - 1.35}{220\text{k}\Omega} \right) = 24.2 \mu\text{A} \quad V_D = 12 - 3.3 \times 10^5 (I_D) = 4.01\text{V}$$

$$V_{DS} = 4.01 - (-V_{GS}) = 5.36\text{V} \quad (> V_{GS} - V_{TN}) \quad Q\text{-Point} = (24.2 \mu\text{A}, 5.36\text{V})$$

$$g_m = \frac{2I_D}{V_{GS} - V_{TN}} = \frac{2(24.2 \times 10^{-6})}{0.348} = 1.39\text{mS} \quad | \quad A_{dd} = -g_m R_D = -1.39\text{ms}(330\text{k}\Omega) = -45.9$$

$$A_{cc} = -\frac{g_m R_D}{1 + 2g_m R_{SS}} = \frac{1.39\text{ms}(330\text{k}\Omega)}{1 + 2(1.39\text{ms})(220\text{k}\Omega)} = -0.738$$

$$\text{For a differential output: } A_{dm} = A_{dd} = -45.9 \quad | \quad A_{cm} = 0 \quad | \quad \text{CMRR} = \infty$$

$$\text{For a single-ended output: } A_{dm} = \frac{A_{dd}}{2} = -23.0 \quad | \quad A_{cm} = A_{cc} = -0.738$$

$$\text{CMRR} = \frac{23.0}{0.738} = 31.2 \quad | \quad \text{CMRR}_{\text{db}} = 29.8 \text{ dB} \quad | \quad R_{ID} = \infty \quad | \quad R_{IC} = \infty$$