

Homework Assignment No. 11 - Solutions**18.1**

$$S_A^{A_v} = \frac{A}{A_v} \frac{\partial A_v}{\partial A} \quad A_v = \frac{A}{1+A\beta}$$

$$\frac{\partial A_v}{\partial A} = \frac{(1+A\beta)1 - A\beta}{(1+A\beta)^2} = \frac{1}{(1+A\beta)^2} \quad S_A^{A_v} = \frac{A}{\frac{A}{1+A\beta}} \frac{1}{(1+A\beta)^2} = \frac{1}{1+A\beta} \approx \frac{1}{A\beta}$$

$$S_A^{A_v} = \frac{1}{1+10^5(0.01)} = \frac{1}{1001}$$

$$\frac{\partial A_v}{A_v} = S_A^{A_v} \frac{\partial A}{A} = \frac{1}{1001} 10\% = 9.99 \times 10^{-3}\%$$

18.4

$$A_v = \frac{A}{1+A\beta} \quad | \quad \text{From Chapter 12, } GE = \frac{1}{1+A\beta} \approx \frac{1}{A\beta}$$

$$\frac{1}{\beta} = 200 \quad | \quad GE = \frac{200}{A} \leq 0.002 \rightarrow A \geq \frac{200}{0.002} = 10^5 \quad | \quad A \geq 100 \text{ dB}$$

18.6 (a) Series-shunt (b) Shunt-series (c) Series-series (d) Shunt-shunt**18.9** (a)

$$h_{11}^A = \left. \frac{v_1}{i_1} \right|_{v_2=0} = 15 \text{ k}\Omega \quad | \quad h_{11}^F = 4.3 \text{ k}\Omega \parallel 39 \text{ k}\Omega = 3.87 \text{ k}\Omega \quad | \quad h_{11}^T = 18.9 \text{ k}\Omega$$

$$h_{22}^A = \left. \frac{i_2}{v_2} \right|_{i_1=0} = (1 \text{ k}\Omega)^{-1} = (1 \text{ k}\Omega)^{-1} \quad | \quad h_{22}^F = (39 \text{ k}\Omega + 4.3 \text{ k}\Omega)^{-1} = (43.3 \text{ k}\Omega)^{-1} \quad | \quad h_{22}^T = 1.02 \text{ mS}$$

$$h_{21}^A = \left. \frac{i_2}{i_1} \right|_{v_2=0} = -\frac{15 \text{ k}\Omega(5000)}{1 \text{ k}\Omega} = -75,000 \quad | \quad h_{21}^F = \left. \frac{i_2}{i_1} \right|_{v_2=0} = -\frac{4.3 \text{ k}\Omega}{39 \text{ k}\Omega + 4.3 \text{ k}\Omega} = -0.0993$$



$$h_{12}^A = \left. \frac{v_1}{v_2} \right|_{i_1=0} = 0 \quad | \quad h_{12}^F = \left. \frac{v_1}{v_2} \right|_{i_1=0} = \frac{4.3 \text{ k}\Omega}{39 \text{ k}\Omega + 4.3 \text{ k}\Omega} = 0.0993$$

$$(b) A = \frac{-h_{21}^A}{(R_S + h_{11}^T)(h_{22}^T + G_L)} = \frac{-(-75000)}{(1 \text{ k}\Omega + 15 \text{ k}\Omega + 3.87 \text{ k}\Omega) \left(\frac{1}{5.6 \text{ k}\Omega} + \frac{1}{1 \text{ k}\Omega} + \frac{1}{43.3 \text{ k}\Omega} \right)} = 3140$$

$$\beta = 0.0993$$

$$(c) A_v = \frac{3140}{1 + 3140(0.0993)} = 10.0 \quad | \quad h_{21}^A \gg h_{21}^F \quad | \quad h_{12}^F \gg h_{12}^A \quad | \quad (R_{IN} = 6.22 \text{ M}\Omega, R_{OUT} = 2.66 \text{ }\Omega)$$

18.11

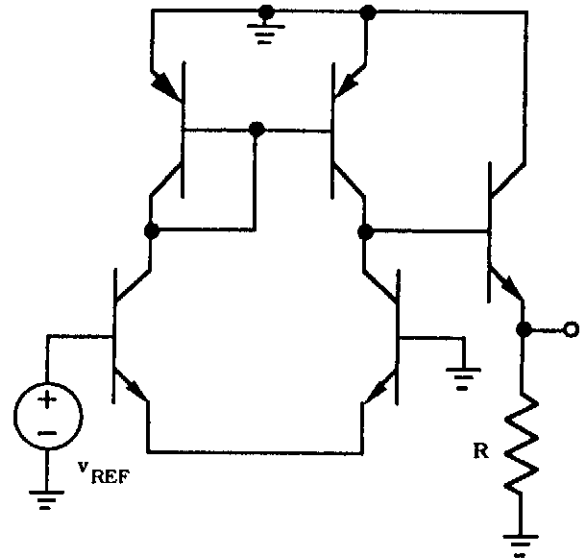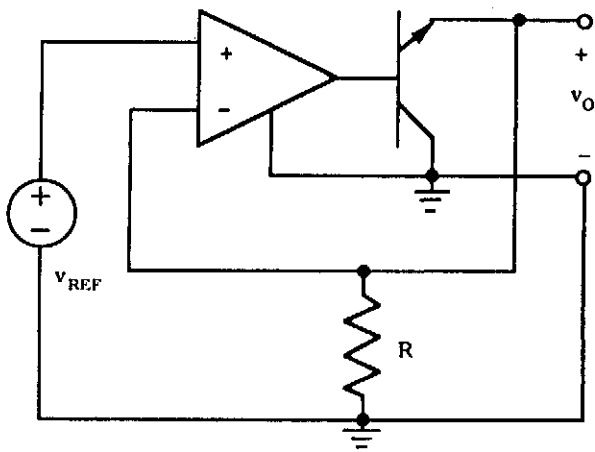

A-Circuit

$$h_{11}^F = \left. \frac{v_1}{i_1} \right|_{v_2=0} = 0 \quad | \quad h_{22}^F = \left. \frac{i_2}{v_2} \right|_{i_1=0} = \frac{1}{R} \quad | \quad h_{12}^F = \left. \frac{v_1}{v_2} \right|_{i_2=0} = 1$$

$$A = g_{m1} (r_{o1} \parallel r_{o4} \parallel [r_{\pi 5} + (\beta_o + 1)R]) \frac{(\beta_o + 1)R}{r_{\pi 5} + (\beta_o + 1)R} = g_{m1} \frac{r_{o1} \parallel r_{o4}}{(r_{o1} \parallel r_{o4}) + r_{\pi 5} + (\beta_o + 1)R} (\beta_o + 1)R$$

$$r_{o1} = \frac{50 + 1.4}{10^{-4}} = 514 \text{ k}\Omega \quad | \quad r_{o4} = \frac{50 + 11.3}{10^{-4}} = 613 \text{ k}\Omega \quad | \quad r_{o1} \parallel r_{o4} = 280 \text{ k}\Omega$$

$$I_{C5} = \frac{12}{10^4} = 1.2 \text{ mA} \quad | \quad r_{\pi 5} = \frac{100(0.025)}{1.2 \text{ mA}} = 2.08 \text{ k}\Omega$$

$$A = 40(10^{-4})(280 \text{ k}\Omega) \frac{(101)10 \text{ k}\Omega}{280 \text{ k}\Omega + 2.08 \text{ k}\Omega + (101)10 \text{ k}\Omega} = 876$$

$$A_V = \frac{A}{1 + T} = \frac{876}{1 + 876(1)} = \frac{109}{110} = 0.999$$

$$R_{IN} = R_{ID}(1 + T) = 2r_{\pi 1}(1 + T) = 2 \frac{100(0.025)}{10^{-4}}(877) = 43.9 \text{ M}\Omega$$

$$R_{OUT} = \frac{R \parallel \frac{r_{\pi 5} + r_{o2} \parallel r_{o4}}{\beta_o + 1}}{1 + T} = \frac{10 \text{ k}\Omega \parallel \frac{2.08 \text{ k}\Omega + 280 \text{ k}\Omega}{101}}{877} = 2.49 \text{ }\Omega$$

$$i_o = \alpha_o i_e = \alpha_o \frac{v_o}{R} \quad | \quad \frac{i_o}{v_{ref}} = \frac{\alpha_o}{R} \frac{v_o}{v_{ref}} = \frac{100}{101} \left(\frac{1}{10^4} \right) (0.999) = 98.9 \text{ }\mu\text{S}$$