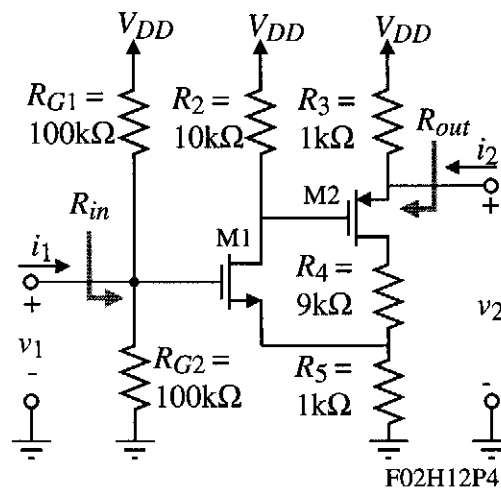



**Homework Assignment No. 12**Due on Monday, November 11, 2002

- 1.) Problem 18.11 of the text.
- 2.) Problem 18.16 of the text.
- 3.) Problem 18.22 of the text.
- 4.) Use the method of feedback analysis to find the numerical values of  $v_2/v_1$ ,  $R_{in} = v_1/i_1$ , and  $R_{out} = v_2/i_2$ . Assume that all transistors are matched and that  $g_{m1} = g_{m2} = 1\text{mS}$ . Neglect  $r_{ds}$  of the transistors.




5.) For each of the MOSFET amplifiers shown below, show how to connect a single resistor from the output to the input that achieves a series-shunt, series-series, shunt-shunt and shunt-series negative feedback amplifier. For each of the four configurations, identify on the schematic the correct variables (voltage or current) for  $x_s$ ,  $x_f$ ,  $x_i$ , and  $x_o$ . The outputs should be at the drain or source of M3.


Series-Shunt

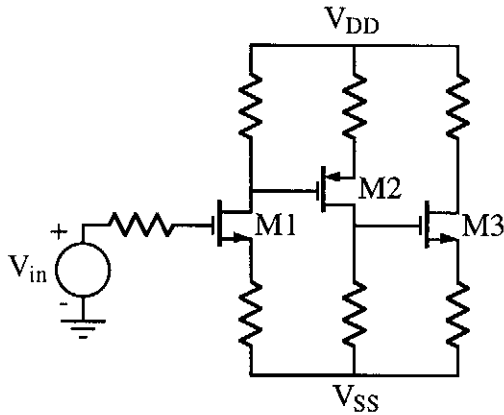

Series-Series

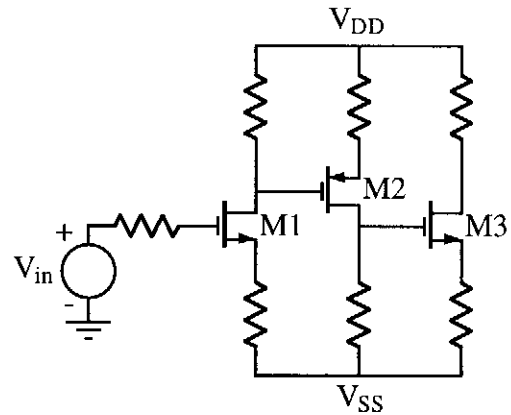

Shunt-Shunt

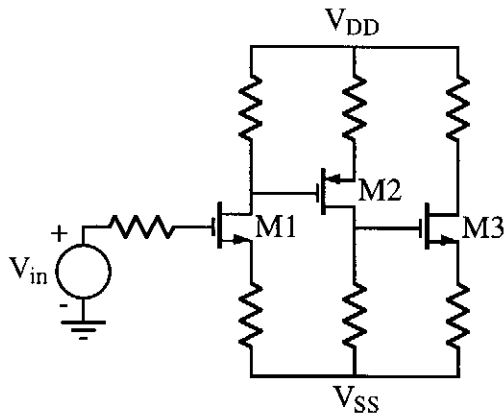

Shunt-Series

