

Review of Chapter 3 - Diodes


① Diode basics -

Large signal model

$$i_D = I_S \left[\exp\left(\frac{V_D}{nV_T}\right) - 1 \right] \quad V_T = \frac{kT}{q}$$


I_S = saturation current (10^{-9} A)

n = nonideal factor ($= 1$)

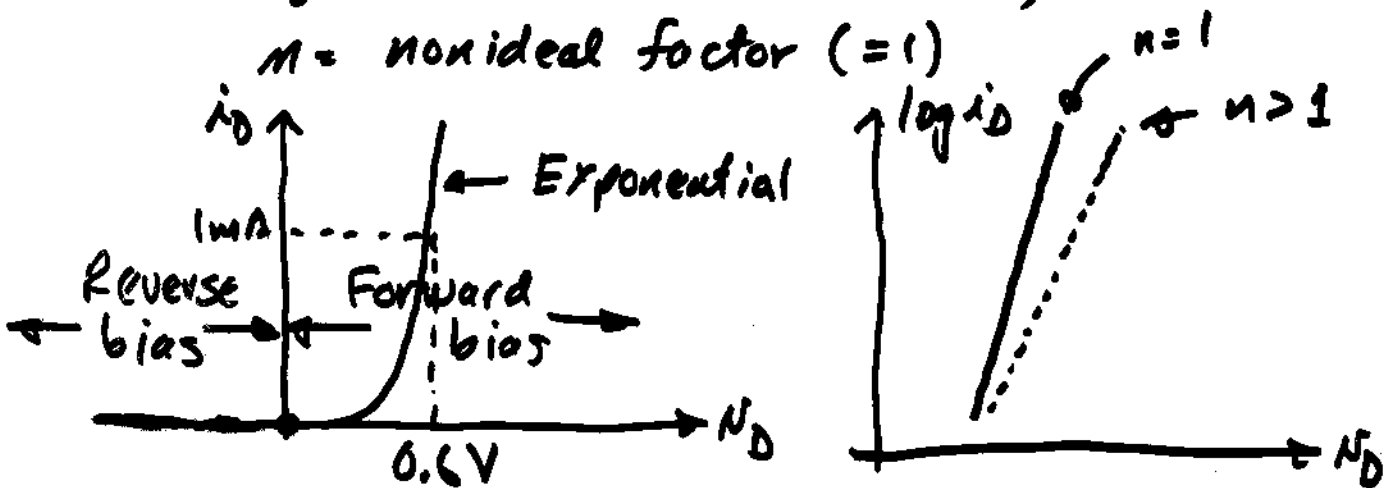


Slope \propto transconductance \rightarrow Gain in amplifiers

② Biasing

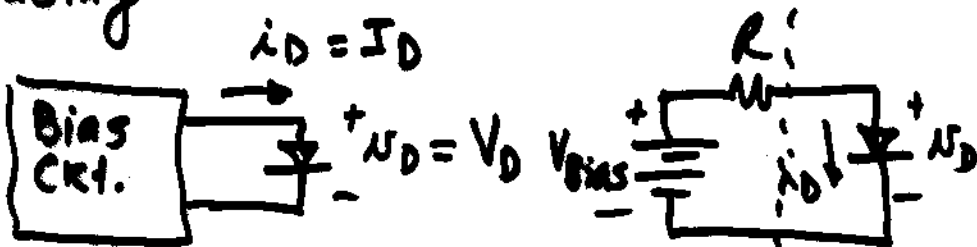

$$i_D = \frac{V_{bias} - V_D}{R} \quad ; \quad i_D = I_S \left[\exp\left(\frac{V_D}{V_T}\right) - 1 \right]$$

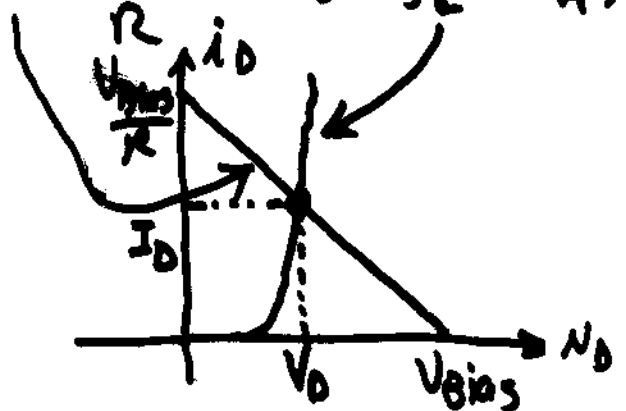Mathematical solution
Iteration
Graphical solution -



3) Temperature dependence

Forward bias - $\frac{dV_D}{dT} \approx \underline{-2mV/^\circ C}$

$$V_D = V_T \ln\left(\frac{I_D}{I_S}\right)$$

$$I_S = K_1 T^3 \exp\left(\frac{V_{G0}}{N_T V_T}\right)$$



Reverse bias -

$$I_D \approx -I_S \quad \frac{dI_D}{dT} \Rightarrow \frac{dI_S}{dT}$$

$$TCF \rightarrow \frac{1}{I_S} \frac{dI_S}{dT} = \frac{3}{T} + \frac{V_{G0}}{V_T T} \approx \frac{V_{G0}}{T V_T}$$

I_S approx. doubles every 5-10°C increase

4) Diode breakdown

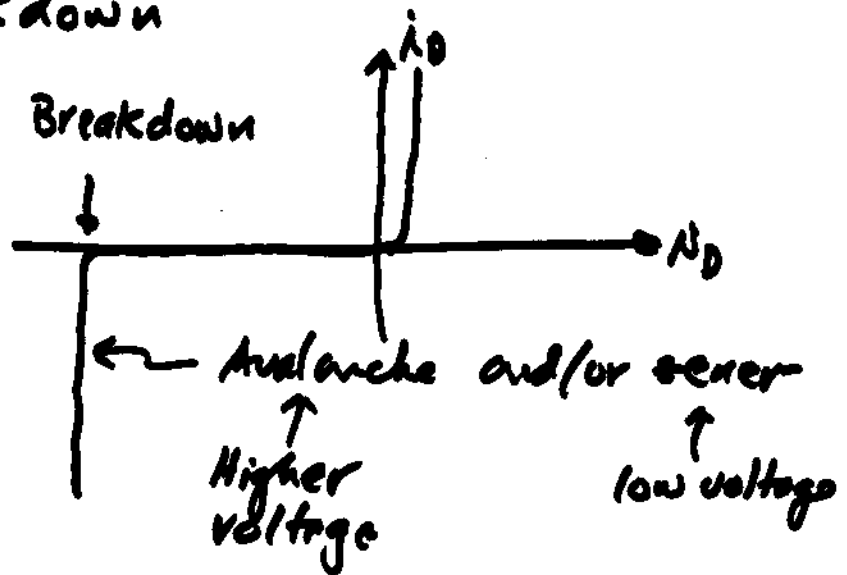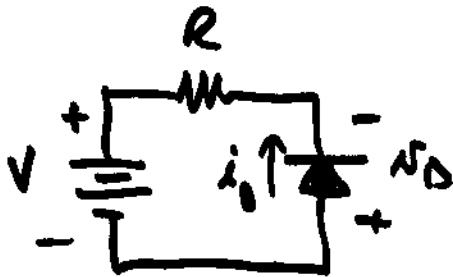

5.) Capacitance

Depletion
Diffusion


$$C_j = \frac{dQ_j}{dV_D} = \frac{C_{j0}}{\sqrt{1 - \frac{V_D}{\phi_j}}}$$



$$C_D = \frac{dQ_D}{dV_D} = \frac{I_D \tau_F}{V_T}$$

Forward
time
constant

5.) cont'd

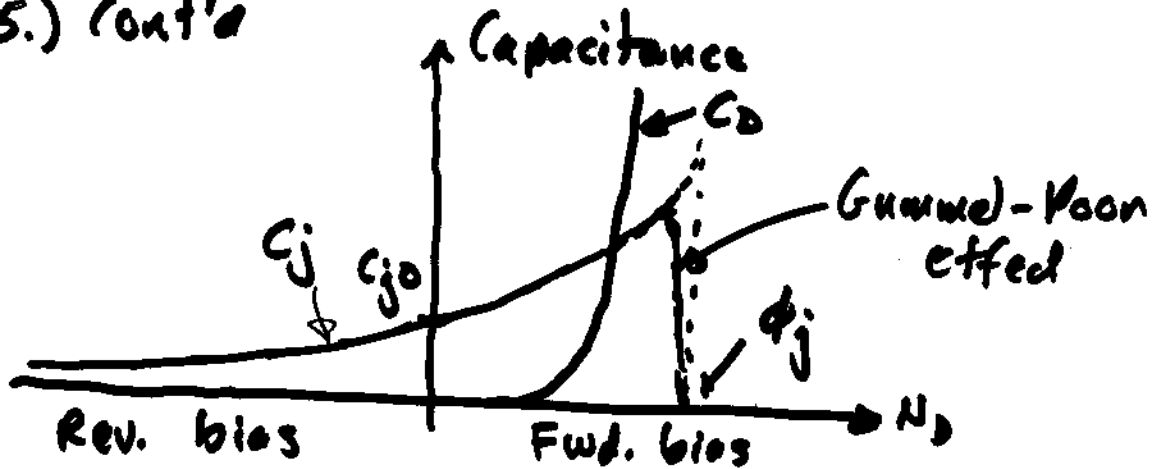

6.) Approximate diode models

a.) Short-circuit/open-circuit model


Ideal diode

b.) Constant voltage drop (CVD)

Ideal diode in series with a battery

c.) Variable voltage drop (VVD)

Ideal diode + Battery + R

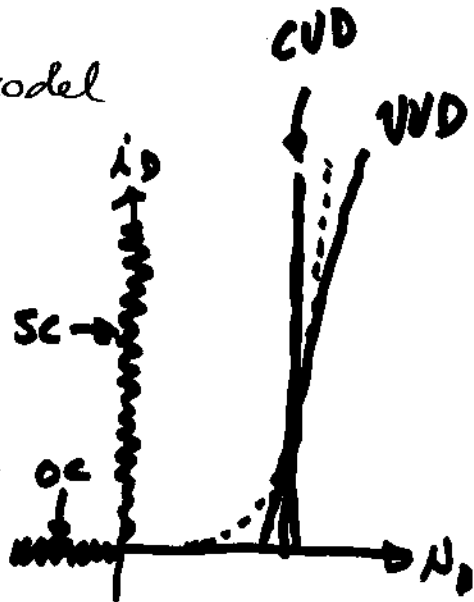

Ideal

CVD

VVD

7.) Small-Signal model