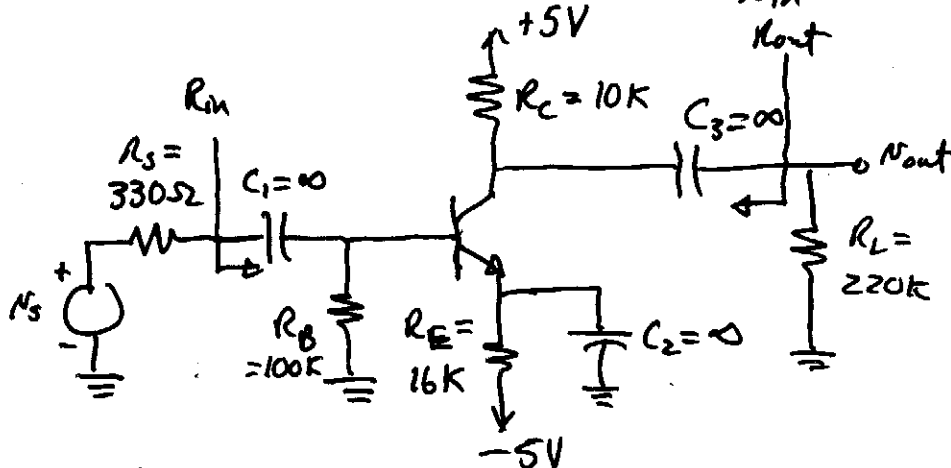


Example 1



1.) BJT, NPN CE Inverting Amplifier

$\beta_F = 65$, $V_A = 50$ Find $\frac{N_{out}}{N_{in}}$, R_{in} , and R_{out} .



a.) Find the Q point.

Assume $V_{BE} \approx 0.7V$

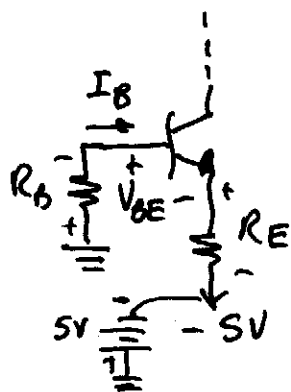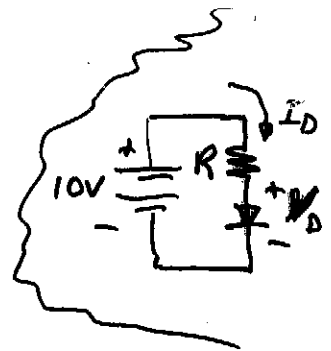

$$0 = I_B R_B + V_{BE} + (1 + \beta) I_B R_E - 5V = 0$$

$$I_B = \frac{5 - V_{BE}}{R_B + (1 + \beta) R_E} = \frac{4.3}{100k + 66(16k)} = 3.72 \mu A$$

$$I_C = 65 \cdot 3.72 \mu A = 242 \mu A$$

$$V_{CE} \approx 10 - I_C (R_C + R_E) = 3.71V$$

b.) Calculate g_m and r_o (and r_{π})


$$g_m = \frac{I_C}{V_T} = \frac{242 \mu A}{25 mV} = 9.68 mS$$

$$r_{\pi} = \frac{\beta_F}{g_m} = \frac{65}{9.68 mS} = 6.71 k\Omega$$


$$r_o = \frac{V_A + V_{CE}}{I_C} = \frac{50V + 3.71V}{242 \mu A} = 222 k\Omega$$

Example 1 - Cont'd

c.) S.S. circuit

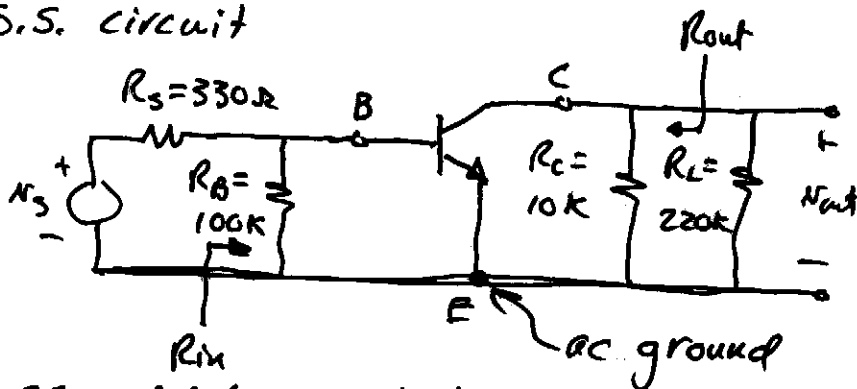

d.) SS model (schematic)

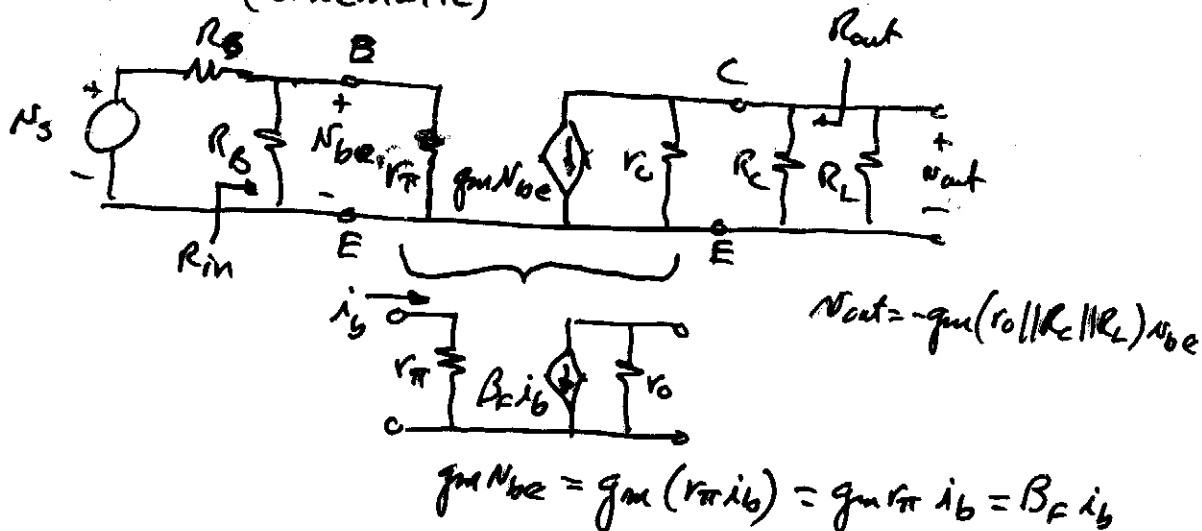

$$N_{out} = -g_m (r_o || R_C || R_L) N_{be}$$

$$g_m N_{be} = g_m (r_{\pi} i_b) = g_m r_{\pi} i_b = \beta_F i_b$$


$$R_{in} = R_B || r_{\pi} = \underline{6.288 k\Omega} \quad R_{out} = r_o || R_C = \underline{9.17 k\Omega}$$

$$\frac{N_{out}}{N_s} = \left(\frac{N_{out}}{N_{be}} \right) \left(\frac{N_{be}}{N_s} \right) = \left(-g_m (r_o || R_C || R_L) \right) \left(\frac{R_B || r_{\pi}}{R_s + R_B || r_{\pi}} \right) \overset{R_{in}}{\leftarrow}$$

$$\frac{N_{out}}{N_s} = (-9.68 \times 9.170) \left(\frac{6.29k}{0.33k + 6.29k} \right) = \underline{-84.3 V/V}$$

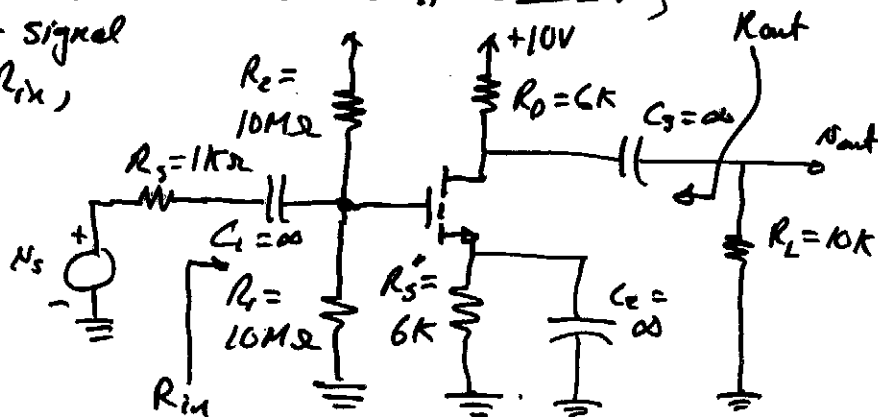
2.) Example 2 - CS, NMOS Inverting Amplifier

If $k_n = 0.5 \text{ mA/V}^2$, $V_{TN} = 1\text{V}$, and $\lambda = 0.01 \text{ V}^{-1}$, find the small-signal voltage gain, R_{in} , and R_{out} .



a.) Find Q point

Thevenin eq. from gate

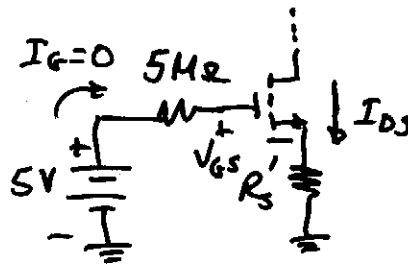

$$5 = V_{GS} + I_{DS} R_{S'}$$

Assume saturation and replace I_{DS}

$$5 = V_{GS} + R_{S'} \left[\frac{k_n}{2} (V_{GS} - V_T)^2 \right] \rightarrow 5 = V_{GS} + (6k) \left(\frac{0.5mA}{2V^2} \right) (V_{GS} - 1)^2$$


Finally,

$$V_{GS}^2 - \frac{5}{3} V_{GS} - \frac{2}{3} = 0$$

$$V_{GS} = \frac{5}{6} \pm 1.667 = 2V$$

$$I_D = 0.5 \frac{(2-1)^2}{2} = \underline{0.5mA}$$
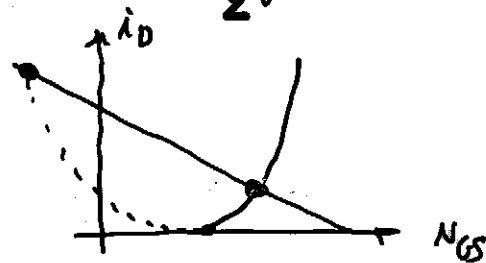
$$V_{DS} = 10 - I_{DS}(R_D + R_{S'}) = \underline{4V} \Rightarrow V_{DS} > V_{GS} - V_T = 1V$$




b.) Small signal model parameters

$$g_m = \sqrt{2k_n I_{DS} (1 + \lambda V_{DS})} = \sqrt{2 \cdot \frac{1}{2} \cdot \frac{1}{2} (1 + 0.04)} = 0.721mS$$

$$r_o = \frac{V_{DS} + \frac{1}{\lambda}}{I_{DS}} = \frac{4 + 100}{0.5} k = 208k\Omega$$

c.) Small-signal circuit -

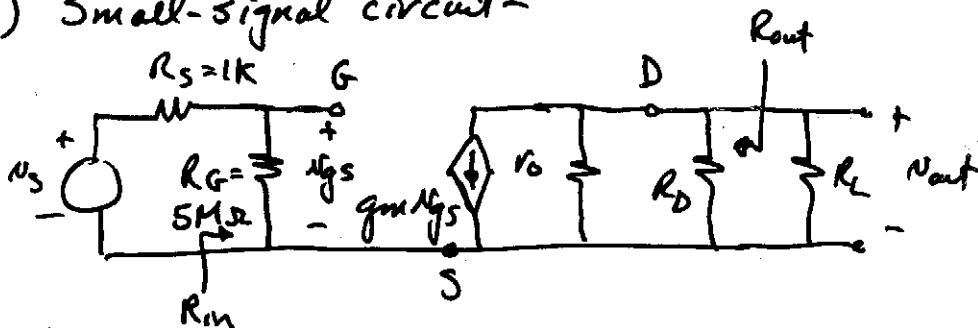

d.) $R_{in} = R_G = \underline{5M\Omega}$ $R_{out} = r_o || R_D = \underline{5.83k\Omega}$

$$\frac{v_{out}}{v_{in}} = \left(\frac{v_{out}}{v_{gs}} \right) \left(\frac{v_{gs}}{v_s} \right) = (-g_m r_o || R_D || R_L) \left(\frac{R_G}{R_s + R_G} \right)$$

$$\frac{v_{out}}{v_{in}} = (-2.13) \left(\frac{5}{5.001} \right) = \underline{-2.13 V/V}$$