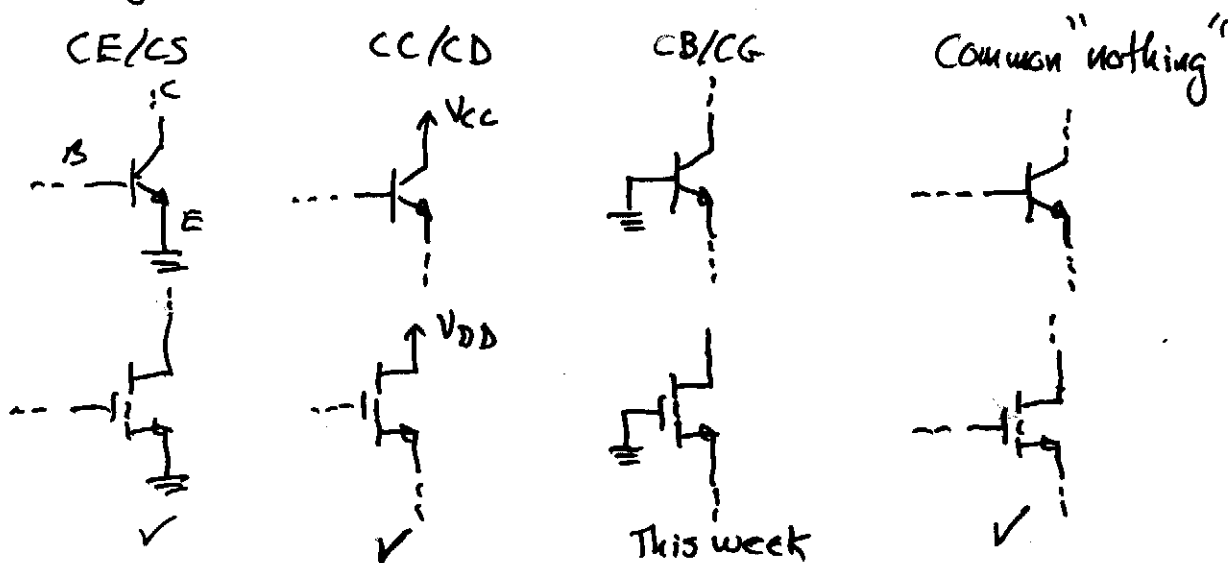


Configurations of the transistor



Small-signal analysis -

- 1.) R_{in}
 - 2.) R_{out}
 - 3.) Voltage gain
 - 4.) Current gain
- } Must be defined

$$r_o = \frac{1}{\lambda} \frac{V_{CE} + V_A}{I_C}$$

Memorize -

- 1.) Formulas for g_m

$$g_m(\text{FET}) = \sqrt{2K_n I_{D_S}}$$

$$g_m(\text{BJT}) = \frac{I_C}{V_T}$$

$$\frac{I_{D_S}}{V_p^2}$$

$$2.) r_o(\text{FET}) \approx \frac{1}{\lambda I_{D_S}}$$


$$r_o(\text{BJT}) \approx \frac{V_A}{I_C}$$

$$r_{\pi} = \frac{\beta_0}{g_m}$$

3.) Configuration	R_{in}	R_{out}	Voltage Gain
CE/CS	$> r_{\pi}$	Large	Neg. & large
CC/CD	Very large	Small $\approx \frac{1}{g_m}$	$< +1$
CB/CG	Medium-small	Large	Positive & large
Common Nothing	Large	Large	Neg. & moderate

CB Amplifier

1.) Circuit $V_{cc} = 12V$

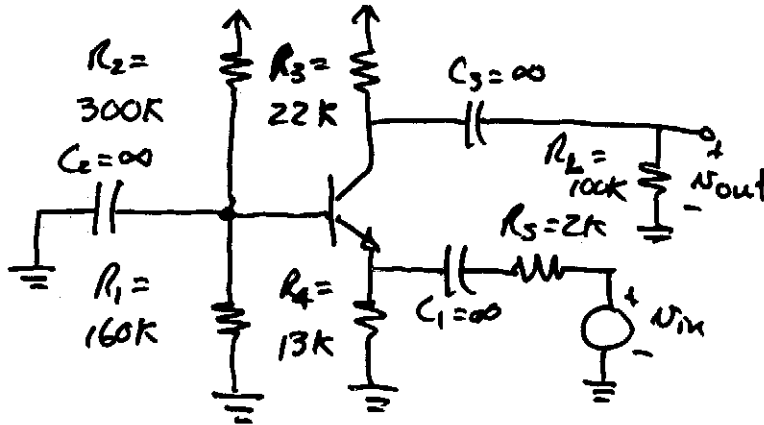

$\beta_F = 100$



$V_A = 50$

DC Analysis:



$I_C = 245 \mu A$

$V_{CE} \approx 3.4V$

2.) AC circuit

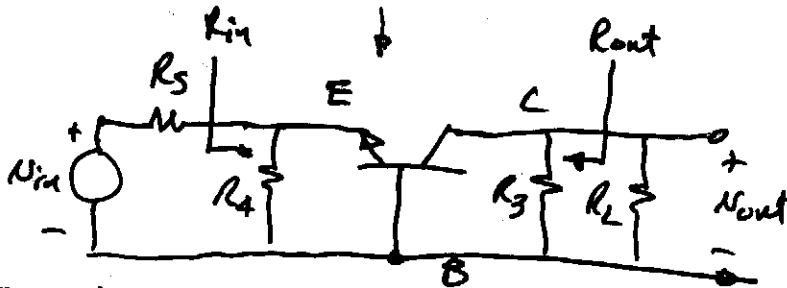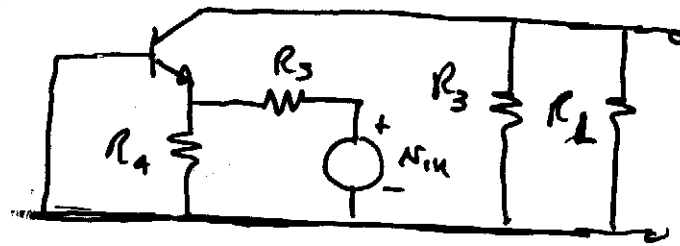


3.) Small-signal model

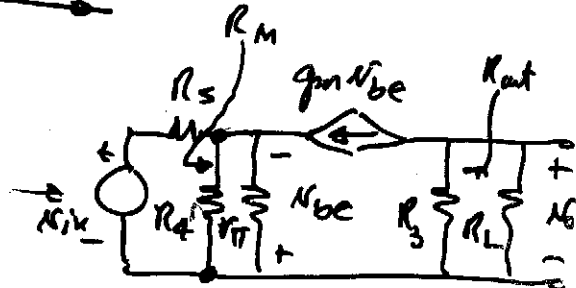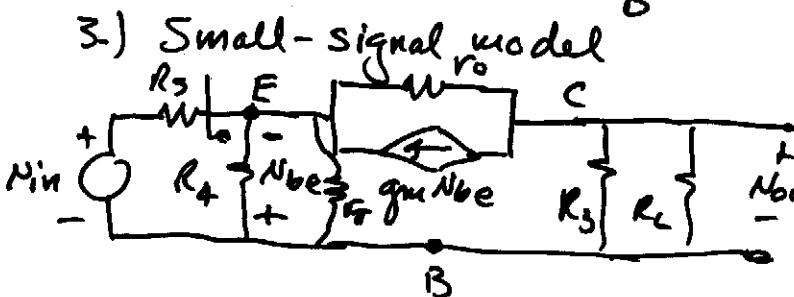

$R_{out} = R_S = 22k$

$R_m = ?$

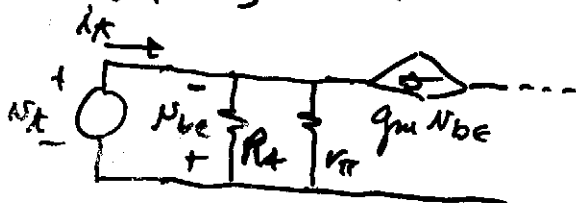


$i_x = \frac{N_x}{R_4} + \frac{N_x}{r_{\pi}} - g_m N_{be}$

$i_x = N_x \left[\frac{1}{R_4} + \frac{1}{r_{\pi}} + g_m \right]$

$R_{in} = \frac{N_x}{i_x} = \frac{1}{\frac{1}{R_4} + \frac{1}{r_{\pi}} + g_m} = \frac{1}{g_m} \parallel r_{\pi} \parallel R_4 \approx \frac{1}{g_m}$

Voltage gain

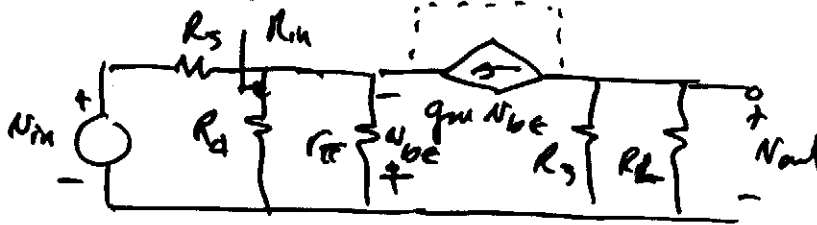

$$\begin{aligned} \frac{v_{out}}{v_{in}} &= \left(\frac{v_{out}}{v_{be}} \right) \left(\frac{v_{be}}{v_{in}} \right) = \left(-g_m R_3 \parallel R_L \right) \left(\frac{-R_{in}}{R_{in} + R_s} \right) \\ &= \frac{+g_m (R_3 \parallel R_L) R_{in}}{R_{in} + R_s} \end{aligned}$$

Done after lecture


Numerical evaluation of the above example

$$g_m = 9.8 \text{ ms}, \quad r_{\pi} = 10.2 \text{ k}, \quad \text{and } r_o = 204 \text{ k}$$

$$R_{out} = \underline{\underline{22 \text{ k}}} \quad R_{in} \approx \frac{1}{g_m} = \underline{\underline{102 \Omega}} \quad A_v = +8.98 \text{ V/V}$$

Question by Dee Dee - What is the current gain?

after class

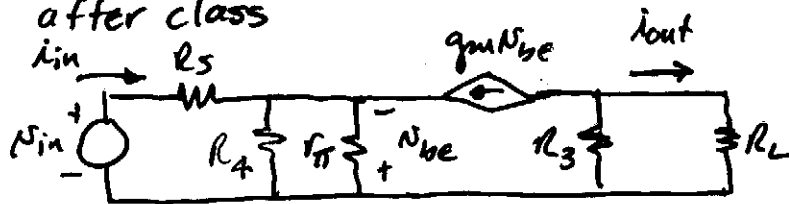

$$\frac{i_{out}}{i_{in}} = \left(\frac{i_{out}}{v_{be}} \right) \left(\frac{v_{be}}{i_{in}} \right) = \left(-\frac{g_m R_3}{R_3 + R_L} \right) (-R_{in}) = \frac{g_m R_3 i_{in}}{R_3 + R_L}$$

$$\frac{i_{out}}{i_{in}} = \frac{(9.8)(22) 0.102}{122} = \underline{\underline{0.18 \text{ A/A}}}$$

(losing most of the current in R_3 as opposed to i_{out} which is thru R_L .)