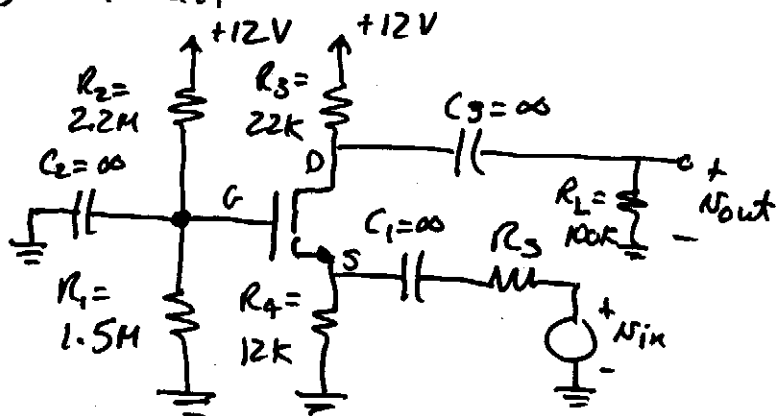


# Common-Gate FET Amplifier


1.) Circuit



$K_n = 500 \mu A/V^2$   
 $V_{TN} = 1V$   
 $\lambda = 0$   
 $I_{DS} = 241 \mu A$


$g_m(BJT) = \frac{I_c}{V_t}$

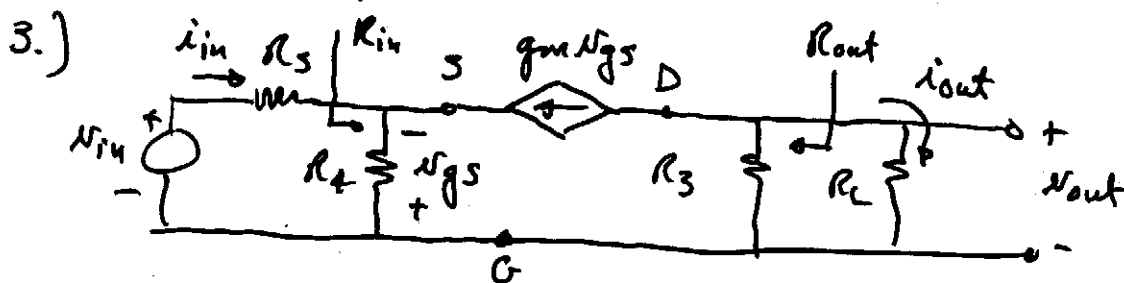2.) Calculate  $g_m = \sqrt{2 K_n \cdot I_{DS}} = 509 \mu S$      $g_m(FET) = \sqrt{2 \cdot K_n I_{DS}}$



4.) Find  $R_{in}$ ,  $R_{out}$ ,  $\frac{v_{out}}{v_{in}}$ , and  $\frac{i_{out}}{i_{in}}$ .


a.)  $R_{out}$

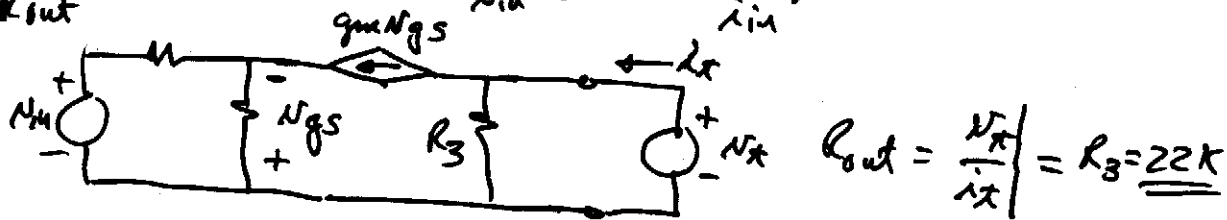

$R_{out} = \frac{v_x}{i_x} = R_3 = \underline{\underline{22K}}$

$v_{in} = 0 \Rightarrow v_{gs} = 0$


b.)  $R_{in}$

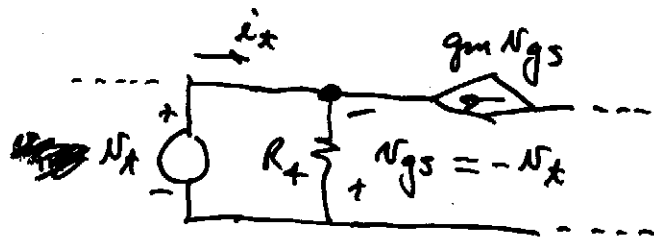

$i_x + \frac{v_x}{R_4} + g_m v_{gs} = 0$

$i_x = \frac{v_x}{R_4} + g_m v_x$

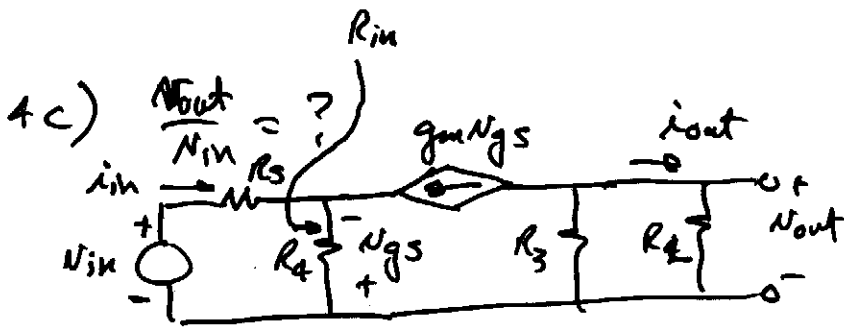$R_{in} = \frac{v_x}{i_x} = \frac{1}{\frac{1}{R_4} + g_m} = \frac{1}{g_m} \parallel R_4 \approx \frac{1}{g_m} = \underline{\underline{1.96 k\Omega}}$



$$\frac{v_{out}}{v_{in}} = \left( \frac{v_{out}}{v_{gs}} \right) \left( \frac{v_{gs}}{v_{in}} \right) = \left( -g_m R_{3||R_L} \right) \left( -\frac{R_{in}}{R_s + R_{in}} \right)$$


$$= (-0.509 \times 18) \left( -\frac{1.96k}{3.96k} \right) = +4.54 \text{ V/V}$$

4d)

$$\frac{i_{out}}{i_{in}} = \left( \frac{i_{out}}{i_{gs}} \right) \left( \frac{i_{gs}}{i_{in}} \right) \left( \frac{i_{in}}{i_{in}} \right) = \left( -g_m \frac{R_3}{R_3 + R_L} \right) \left( -\frac{R_{in}}{R_s + R_{in}} \right) \left( R_s + R_{in} \right)$$

$$\frac{i_{out}}{i_{in}} = (-0.509 \times 18) \left( -\frac{1.96k}{3.96k} \right) 3.96k \approx 18 \text{ A/A}$$


Source follower with  $V_{BS} \neq 0$

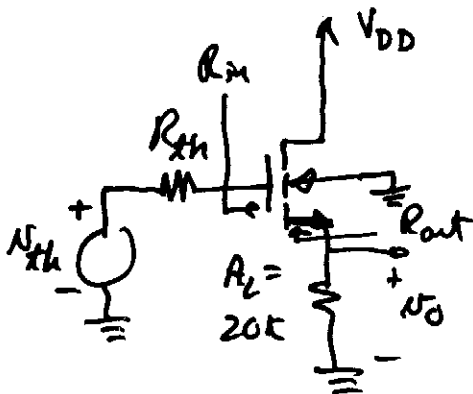


Find  $\frac{v_{out}}{v_{th}}$ ,  $R_{in}$  &  $R_{out}$

$k_n = 500 \frac{\mu A}{V^2}$ ,  $V_{TN} = 1$ ,  $\lambda = 0$ ,  
 $\gamma_N = 0.75 \text{ V}^{+1/2}$  and  $2\phi_F = 0.6 \text{ V}$   
 $I_{DS} = 241 \mu A$  &  $V_0(\text{DC}) = 5 \text{ V}$ .

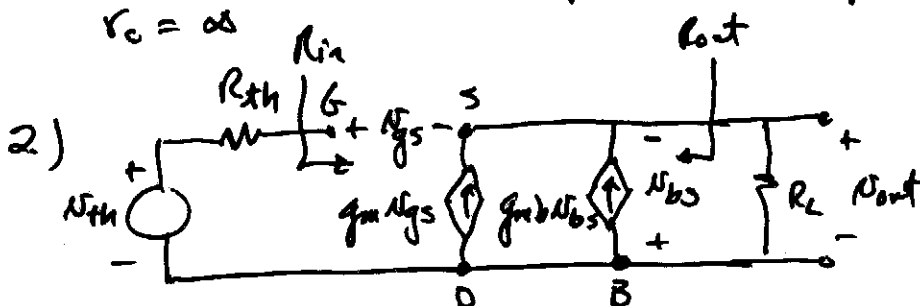1.)  $g_m = 509 \mu S$ ,  $g_{mb} = \frac{\gamma g_m}{2\sqrt{V_{SB} + 2\phi_F}} = \frac{0.75(509 \mu S)}{2\sqrt{5 + 0.6}} = 77.8 \mu S$



3)  $R_{in} = \infty$

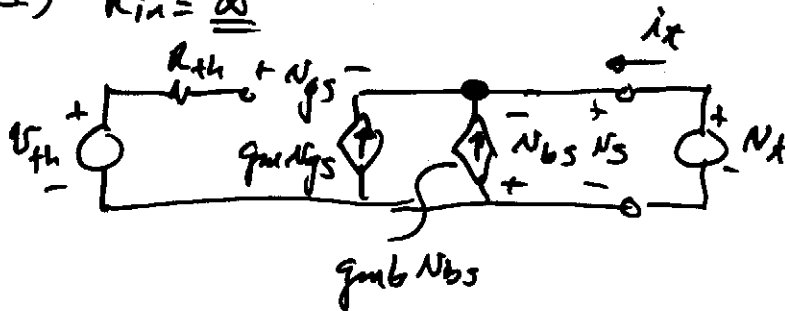

$$i_x + g_m V_{gs} + g_m V_{bs} = 0$$

$$i_x + g_m (V_x - V_x) - g_m V_x = 0$$

$$i_x - g_m V_x - g_m V_x = 0$$

$$i_x = V_x (g_m + g_m) \rightarrow R_{out} = \frac{V_x}{i_x} = \frac{1}{g_m + g_m} = \frac{10^6}{50 + 77.8} \approx \underline{\underline{1.76k}}$$

(Note that  $g_m$  includes  $\lambda \neq 0$ )

Should use  $g_m = 491 \mu S$

$$\frac{V_{out}}{V_{in}} = \frac{g_m R_L}{1 + g_m R_L + g_m R_L} = \frac{(0.491)(20)}{1 + 0.491 \cdot 20 + 77.8 \cdot 20} = \underline{\underline{0.793 V/V}}$$