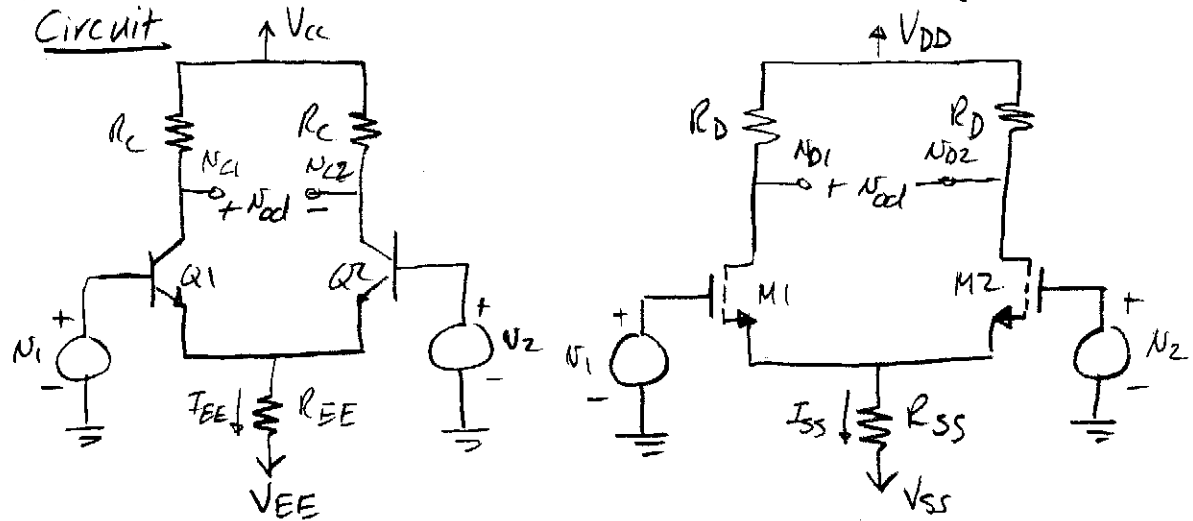


LECTURE 23Differential Amplifiers

Amplifiers that amplify the difference between two voltages and reject the average of the two voltages.



DC Analysis (Assume  $v_1 = v_2 = 0$ )

$$I_{EE} = \frac{V_{EE} - V_{BE}}{R_{EE}}$$

$$I_E = \frac{I_{EE}}{2}, I_C = \alpha I_E$$

$$I_B = \frac{I_C}{\beta_F}$$

$$V_C = V_{CC} - I_C R_C$$

$$I_{SS} = \frac{V_{SS} - V_{GS}}{R_{SS}}$$

$$I_{DS} = \frac{I_{SS}}{2}$$

$$V_D = V_{DD} - I_{DS} R_D$$

Example:

$$V_{DD} = 5V, V_{SS} = -5V, R_{SS} = 10K, R_C = 10K, \mu_n = 1mA/V^2, V_{TN} = 1V$$

$$V_{SS} = V_{GS} + I_{SS} R_{SS} = V_{GS} + 2I_{DS} R_{SS}$$

$$V_{SS} = V_{GS} + 2R_{SS} \frac{1}{2} \mu_n (V_{GS} - V_{TN})^2 = V_{GS} + 10(V_{GS} - 1)^2$$

$$\therefore V_{GS}^2 - 2V_{GS} + \frac{1}{10} V_{GS} + 0.5 = V_{GS}^2 - 1.9V_{GS} + 0.5 = 0$$


$$V_{GS} = 0.95 \pm 0.634 = 1.584V$$

$$\therefore I_{DS} = \frac{1mA/V^2}{2} (0.584)^2 = \underline{170.8 \mu A}$$

$$I_{SS} = 341.6 \mu A \quad V_D = 5 - 10(0.1708) = 3.29V$$

$$V_S = -1.584V \rightarrow V_{DS} = \underline{4.876} \rightarrow \text{saturated}$$
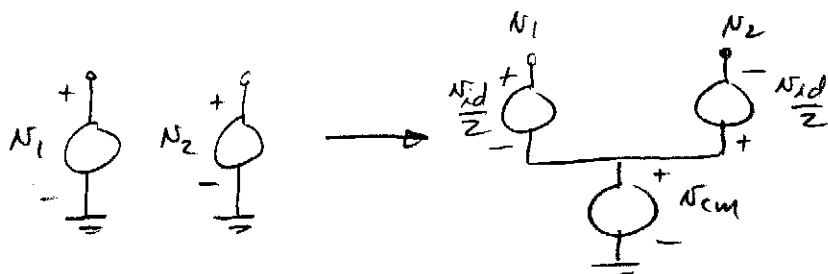
# AC Analysis of the Differential Amplifier







Differential-mode input:  $N_{id} = N_1 - N_2$

Common mode input:  $N_{cm} = \frac{N_1 + N_2}{2}$

$\therefore N_1 = \frac{N_{id}}{2} + N_{cm}$  and  $N_2 = -\frac{N_{id}}{2} + N_{cm}$

Differential mode Half Circuit -

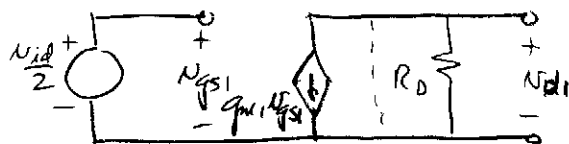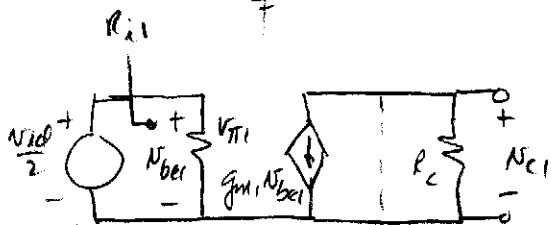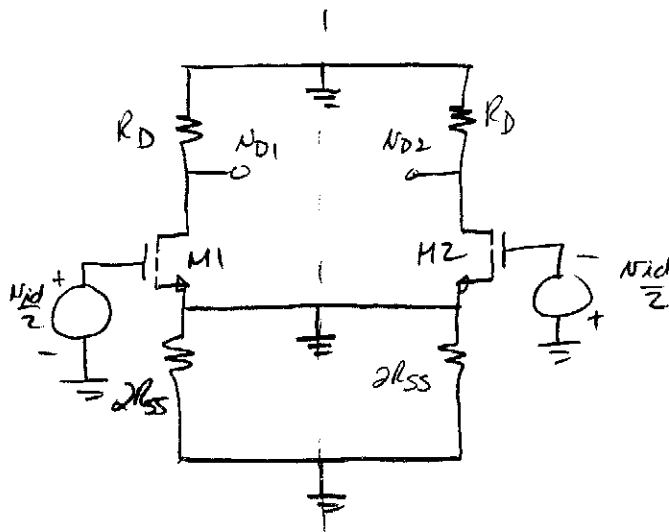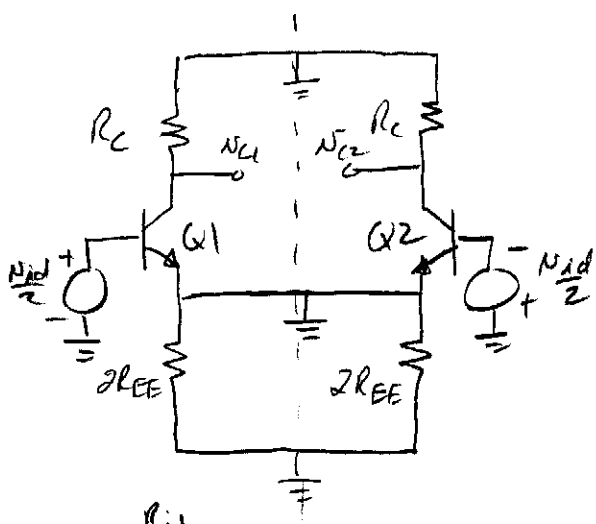

$$N_{c1} = -g_{m1} R_c \frac{N_{id}}{2}$$

$$N_{d1} = -g_{m1} R_D \frac{N_{id}}{2} = -\frac{g_{m1} R_D}{2} N_{id}$$

$$\therefore A_{vd} = \frac{N_{c1}}{N_{id}} = -\frac{g_{m1} R_c}{2}$$

$$\frac{N_{od}}{N_{id}} = g_{m1} R_c$$

$$\therefore A_{vd} = \frac{N_{d1}}{N_{id}} = -\frac{g_{m1} R_D}{2}$$

$$\frac{N_{od}}{N_{id}} = g_{m1} R_D$$

$$R_{i1} = r_{\pi}$$

$$R_{id} = \infty$$

$$R_{id} = \frac{N_{id}}{i_b} = \frac{N_{id}}{\frac{N_{id}/2}{r_{\pi}}} = 2r_{\pi}$$

$$R_{od} = 2(R_D || r_o)$$

$$R_{od} = 2(R_c || r_o)$$