

17.2 How do you find poles and zeros


- 1.) Direct analysis
- 2.) Approximate methods

17.3 Short-circuit time constant method to find ω_L .

$$\omega_L \approx \sum_{i=1}^n \frac{1}{R_{iS} C_i} \quad \left(\begin{array}{l} \text{Poles must be real} \\ \text{Ignores the zeros} \end{array} \right)$$


17.4/5 High freq. ss model for transistors

BJT - Hybrid- π model

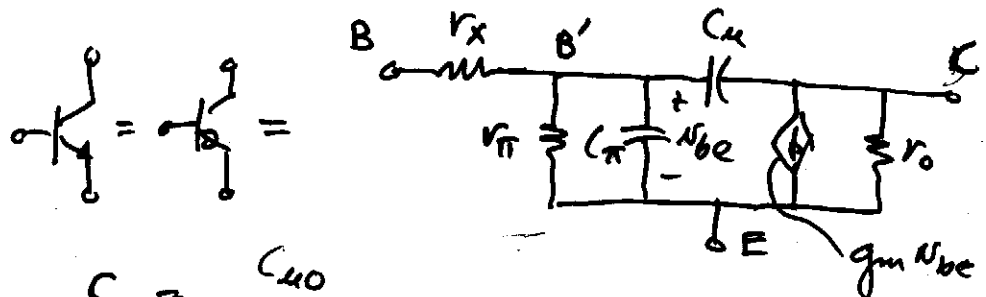


$$C_{\mu} = \frac{C_{\mu 0}}{\sqrt{1 + |V_{CB}| / \phi_{jc}}} \quad V_{CB} \approx V_{CE}$$

$$C_{\pi} = g_m \tau_F$$

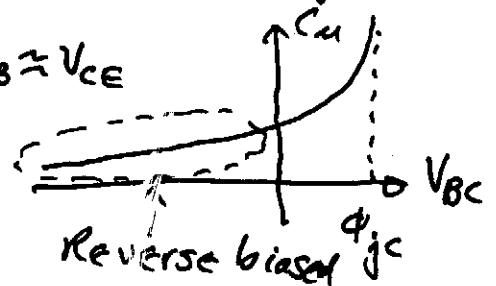

UGBW


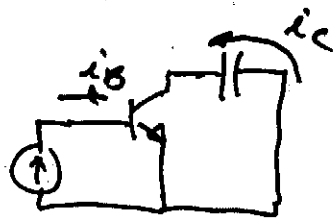


$$\frac{i_c}{i_b} = \beta(j\omega) = 1 \rightarrow \omega = \omega_T$$

$$\omega_T = \frac{g_m}{C_{\pi} + C_{\mu}}$$


$$C_{\pi} \approx 10 C_{\mu}$$

MOSFET (JFET):

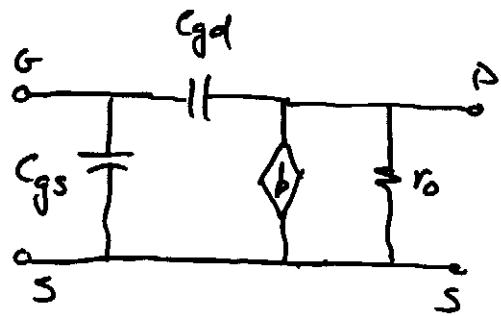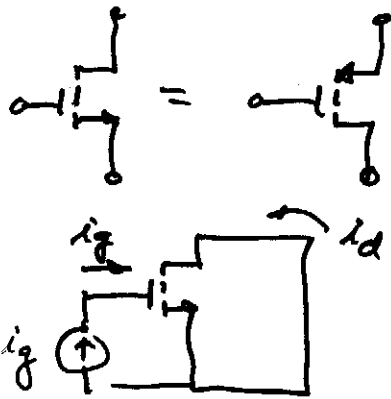

$$\omega_T = \frac{g_m}{C_{gs} + C_{gd}} \rightarrow f_T = 10\text{GHz} - 50\text{GHz}$$

17.6 What is ω_H ?

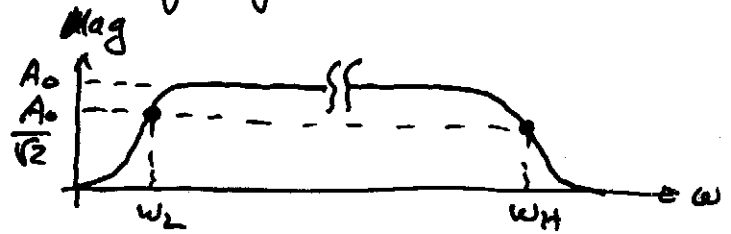


1.) Direct analysis (messy)

2.) Approximate method

$$s^2 + A_1s + A_0 \rightarrow \text{roots}$$

$$p_1 \approx -\frac{1}{A_1}, p_2 \approx -\frac{A_0}{A_1}$$


17.7 Miller Multiplication

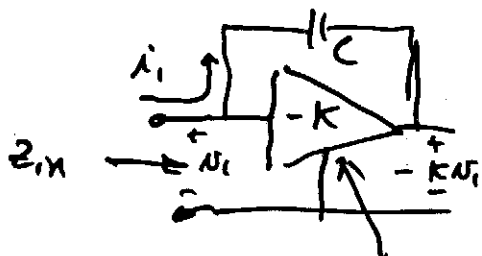

$$Z_{in} = \frac{N_i}{i_1} = ?$$

$$i_1 = \frac{N_i - (-KN_i)}{1/sC}$$
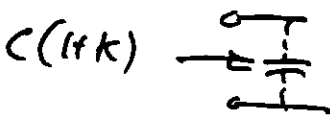
$$Z_{in} = \frac{N_i}{s(N_i + KN_i)} = \frac{1}{sC(1+K)}$$



Common source
Common emitter



Dominant pole $\approx \omega_H$

17.8 Open-circuit T.C. method

$$\omega_H \approx \frac{1}{\sum_{i=1}^n R_{i0} C_i}$$

(Real poles & ignores zero)

Prob. 17.14

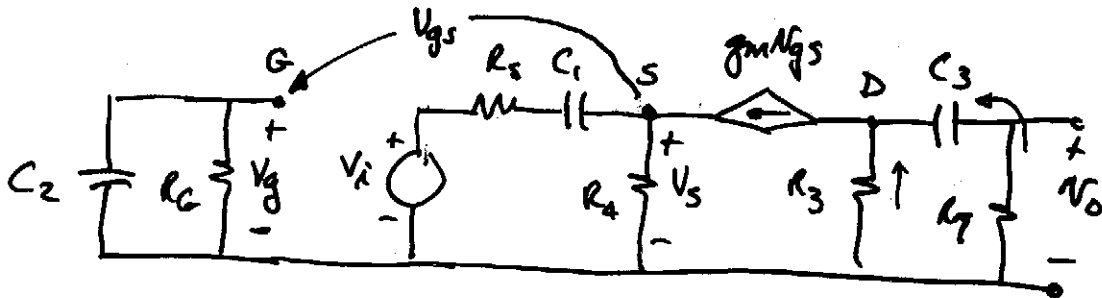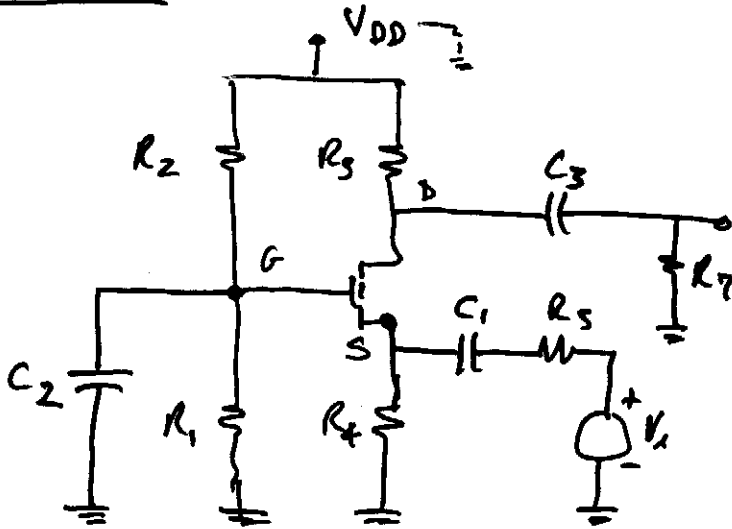

$$R_G = R_1 || R_2$$

$$\frac{V_o}{V_i} = \left(\frac{V_o}{V_{gs}} \right) \left(\frac{V_{gs}}{V_s} \right) \left(\frac{V_s}{V_i} \right)$$


$$V_o = (-g_m V_{gs}) \left(\frac{R_3}{R_3 + R_7 + \frac{1}{sC_3}} \right) (R_7)$$

$$V_{gs} = V_g - V_s \quad (V_g = 0)$$

$$\frac{V_o}{V_{gs}} = \left(\frac{-g_m R_3 R_7}{R_3 + R_7} \right) \left(\frac{1}{1 + \frac{1}{sC_3(R_3 + R_7)}} \right)$$

$$V_s = g_m V_{gs} \left[R_4 || \left(R_5 + \frac{1}{sC_1} \right) \right]$$

$$V_s = V_i \frac{R_4 || \frac{1}{g_m}}{R_4 || \frac{1}{g_m} + R_5 + \frac{1}{sC_1}}$$

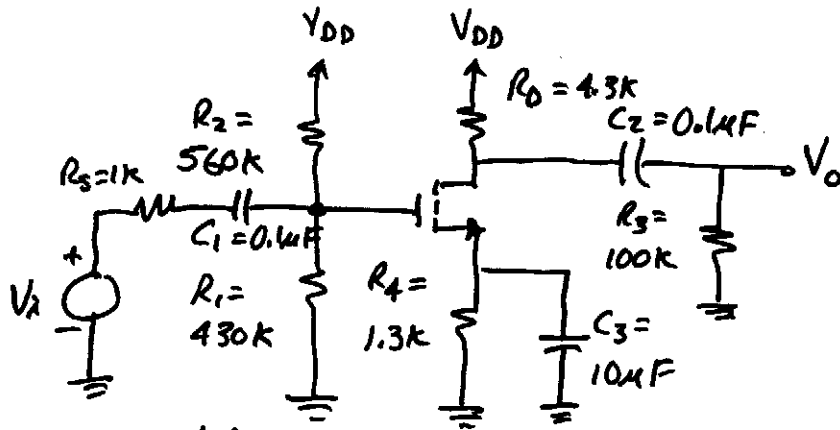

SS model

