

LECTURE 33 - FEEDBACK (CONTINUED)


Transconductance Amplifiers - Series-Series Feedback

1.) Find $Z_{iF} = \frac{N_1 I}{I_1} \Big|_{i_2=0}$ (input resistance of fb. ckt. with output OC)

2.) Find $Z_{oF} = \frac{N_2 E}{i_2} \Big|_{i_1=0}$ (output resistance of fb. ckt. with input OC)

3.) Find $Z_{12F} = \frac{N_1 I}{i_2} \Big|_{i_1=0}$ (transresistance from output to input of fb. ckt. with input OC)

4.) $A = \frac{i_2}{N_1}$

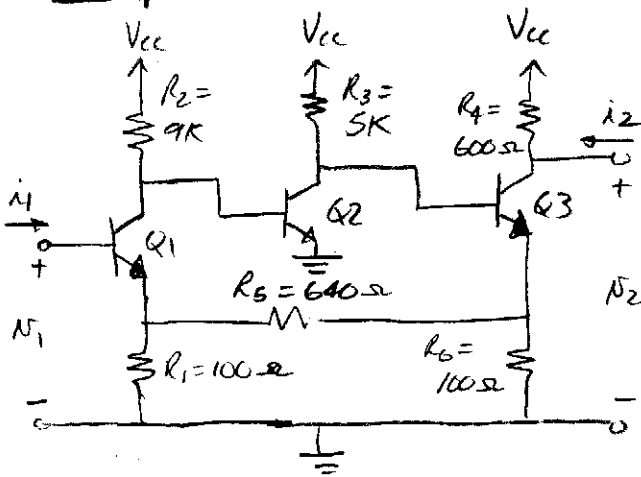Example

If $h_{fe} = 100$ and $I_{C1} = 0.6 \text{ mA}$,

$I_{C2} = 1 \text{ mA}$ and $I_{C3} = 4 \text{ mA}$, find

$\frac{N_2}{N_1}$, $\frac{N_1}{i_1}$, and $\frac{N_2}{i_2}$.


$$r_{\pi 1} = \frac{100 \cdot 25}{0.6} = 4.16 \text{ K}, \quad r_{\pi 2} = \frac{100 \cdot 25}{1} = 2.5 \text{ K}$$

$$r_{\pi 3} = \frac{100 \cdot 25}{4} = 625 \Omega$$

1.) $Z_{iF} = R_1 \parallel (R_5 + R_6) = 88.15 \Omega$ 2.) $Z_{oF} = R_6 \parallel (R_1 + R_5) = 88.15 \Omega$

3.) $\beta = Z_{12F} = \frac{R_6}{R_1 + R_5 + R_6} \times R_1 = 11.95 \Omega$

4.)

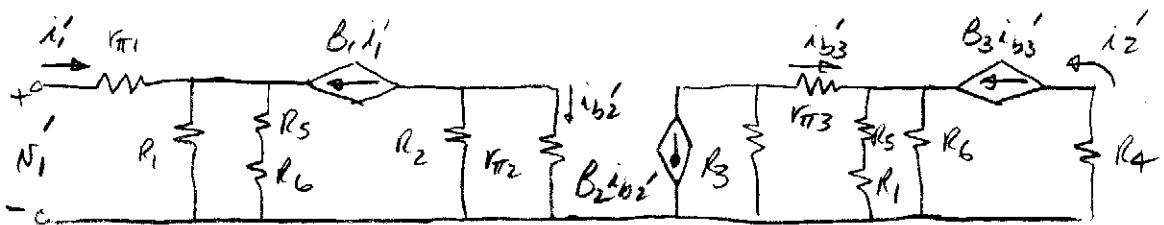

$$A = \frac{i_2'}{N_1} = \left(\frac{i_2'}{i_{b3}'} \right) \left(\frac{i_{b3}'}{i_{b2}'} \right) \left(\frac{i_{b2}'}{i_{b1}'} \right) \left(\frac{i_{b1}'}{N_1'} \right) = (\beta) \left(\frac{-\beta R_3}{R_3 + r_{\pi 3} + (1+\beta)[R_6 \parallel (R_1 + R_5)]} \right) \left(\frac{-\beta R_2}{R_2 + r_{\pi 2}} \right) \left(\frac{1}{r_{\pi 1} + (1+\beta)[R_1 \parallel (R_5 + R_6)]} \right)$$

$$= (100)(-34.43)(-78.3) \left(\frac{1}{12.97 \text{ K}} \right) = 20.78 \text{ A/V}$$

$$\therefore \frac{i_2}{N_1} = \frac{A}{1 + A\beta} = \frac{20.78}{1 + (20.78)(11.9)} = \frac{20.78}{1 + 247.2} = 0.0837 \text{ A/V}$$


$$\frac{N_1}{i_1} = R_{iNF} = (Z_{iF} + R_5)(1 + A\beta) = [88.15 + (1 + \beta)(R_6 \parallel (R_1 + R_5))](248.2) = (12.97 \text{ K})(248.2) = 3.22 \text{ M}\Omega$$

$$\frac{N_2}{N_1} = \frac{i_2 R_4}{N_1} = \frac{i_2}{N_1} R_4 = 50.2 \text{ V/V}$$

$$\frac{N_2}{i_2} = 600 \Omega \quad (\text{Not influenced by fb - outside the loop})$$

$$R_{OUTF} = (Z_{22T} + R_L)(1 + AB)$$

$$Z_{22T} = \left. \frac{V_2}{i_2} \right|_{i_1=0}$$

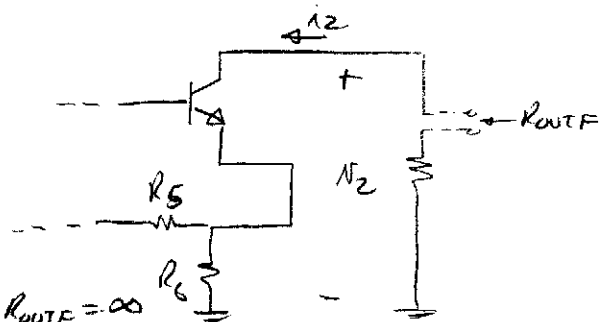

$$i_2 = 0 \rightarrow Z_{22T} = \infty + R_{OUTH} = \infty$$

$$\text{Now - } R_{out} = (R_{OUTH} \parallel R_L) \parallel R_L = \infty \parallel R_L = R_L$$