

## QUIZ NO. 5

NAME \_\_\_\_\_ Score \_\_\_\_\_ /10

A PMOS common-drain amplifier is shown. Assume the parameters of the transistor are  $k_p = 0.5 \text{ mA/V}^2$ ,  $V_{TP} = -1 \text{ V}$ , and  $\lambda = 0$ . (a.) If  $I_{SD} = 0.5 \text{ mA}$ , find the small signal model parameter values for  $g_m$  and  $r_o$ . (b.) Find an algebraic expression for the small signal input resistance,  $R_{in}$ , the output resistance,  $R_{out}$ , and the voltage gain,  $v_{out}/v_{in}$ . (c.) Numerically evaluate the small signal input resistance,  $R_{in}$ , the output resistance,  $R_{out}$ , and the voltage gain,  $v_{out}/v_{in}$ .

