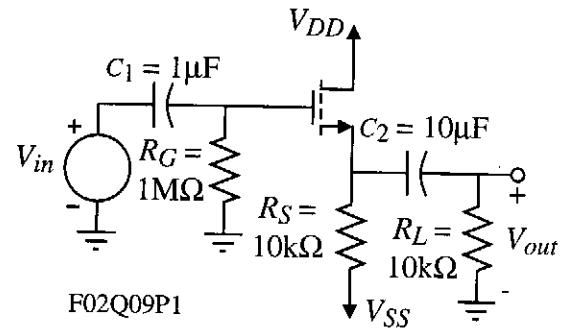


QUIZ NO. 9 - SOLUTION

(Average Score = 6.2/10 for only those who took the quiz.)


1.) If the g_m of the MOSFET is 0.1mA/V, find the midband gain and the location of all zeros and poles of the circuit shown.

2.) If the amplifier above has two zeros at the origin and a pole at -1 rads/sec and -4 rads/sec., what is the lower -3 dB frequency in Hz?



Solution

1.) Small-signal model:

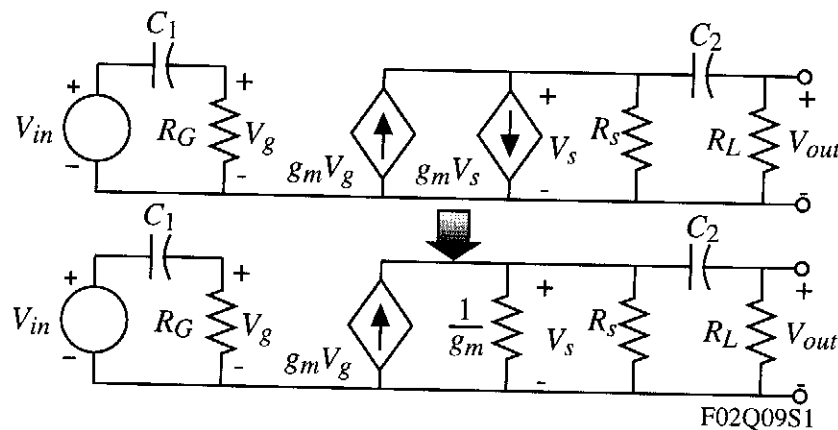

$$\begin{aligned} \frac{V_{out}}{V_{in}} &= \left(\frac{g_m (1/g_m) \parallel R_s}{(1/g_m) \parallel R_s + R_L + \frac{1}{sC_2}} \times R_L \right) \left(\frac{R_G}{R_G + \frac{1}{sC_1}} \right) = \left(\frac{5k}{15k + \frac{1}{sC_2}} \right) \left(\frac{1M}{1M + \frac{1}{sC_1}} \right) \\ &= \left(\frac{1}{3} \right) \left(\frac{s}{s + \frac{1}{15k C_2}} \right) \left(\frac{s}{s + \frac{1}{1M C_1}} \right) = \left(\frac{1}{3} \right) \left(\frac{s}{s + 6.67} \right) \left(\frac{s}{s + 1} \right) \end{aligned}$$

\therefore MGB = 0.333, two zeros at 0 rads/sec. and poles at -1 rad/sec and -6.67 rads/sec.

$$2.) \omega_L \approx \sqrt{p_1^2 + p_2^2 - 2(z_1^2 + z_2^2)} = \sqrt{1^2 + 4^2 - 2(0)} = \sqrt{17} = 4.123 \text{ rads/sec.}$$

$$\therefore f_L = \frac{4.123}{6.28} = \underline{0.656 \text{ Hz}}$$