


QUIZ NO. 10 - SOLUTION

(Average Score = 7.0/10 for only those who took the quiz.)

A BJT transistor amplifier is shown. If $g_m = 100\text{mA/V}$, $r_\pi = 1\text{k}\Omega$, $C_\mu = 1\text{pF}$, and $C_\pi = 20\text{pF}$, find numerical values for the midband gain (MBG) and the upper -3dB frequency (ω_H).

Solution

Midband gain: Small signal model-

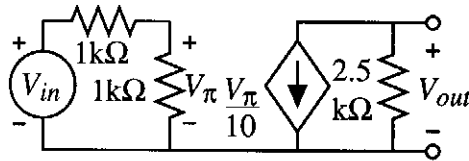

$$\text{MGB} = (0.5) \left(\frac{-2500}{10} \right) = -125 \text{ V/V}$$

High frequency response:

1.) Use the Miller approach.

$$\frac{V_o}{V_\pi} = -g_m(2.5\text{k}\Omega) = -250$$

$$C_{eq} = C_\pi + (251)C_\mu = 20\text{pf} + 251 \cdot 1\text{pF} = 271\text{pF} \quad \text{and} \quad R_{eq} = 1\text{K} \parallel 1\text{K} = 500\Omega$$

$$\therefore \omega_H = \frac{1}{500 \cdot 271\text{pF}} = 7.38 \times 10^6 \text{ rads/sec} \Rightarrow f_H = 1.175 \text{ MHz}$$

2.) Open-Circuit Time Constant Approach.

$$R_{C\pi} = R_s \parallel r_\pi = 500\Omega$$




$R_{C\mu} = ?$ See model.

$$\begin{aligned} v_t &= V_\pi + (i_t + g_m V_\pi) 2.5\text{k}\Omega \\ &= V_\pi (1 + g_m 2.5\text{k}\Omega) + i_t 2.5\text{k}\Omega \\ &= i_t (R_s \parallel r_\pi) (1 + g_m 2.5\text{k}\Omega) + i_t 2.5\text{k}\Omega \end{aligned}$$

$$\therefore R_{C\mu} = \frac{v_t}{i_t} = 0.5\text{k}\Omega(251) + 2.5\text{k}\Omega = 128\text{k}\Omega$$

$$\omega_H = \frac{1}{R_{C\pi} C_\pi + R_{C\mu} C_\mu} = \frac{10^9}{0.5 \times 20 + 128 \times 1} = 7.246 \times 10^6 \text{ rads/sec.} \Rightarrow f_H = 1.15 \text{ MHz}$$

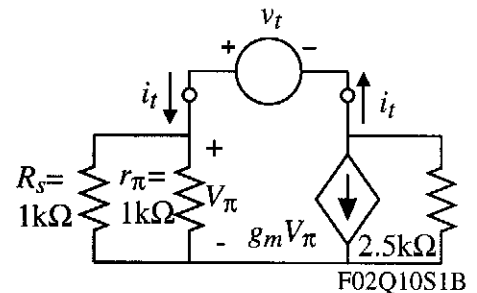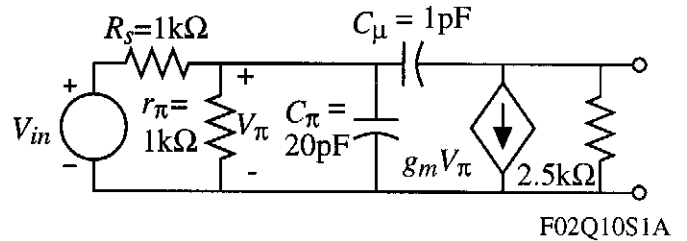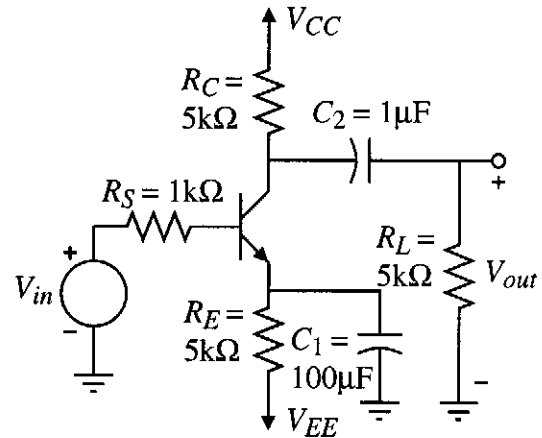The open-circuit time constant approach agrees reasonably well with the Miller approach.



Low frequency response (Not required): Small signal model-

Use the superposition approach which will be exact because C_1 and C_2 are electrically isolated.

C_1 : A bypass capacitor.

$$\text{Zero} = \frac{1}{5\text{k}\Omega \cdot 100\mu\text{F}} = 2 \text{ rads/sec} \quad \text{Pole} = \frac{1}{100\mu\text{F} \left(\frac{2\text{k}\Omega}{101} \parallel 5\text{k}\Omega \right)} = \frac{1}{100\mu\text{F} \cdot 19.7} = 507 \text{ rads/sec}$$

C_2 : A coupling capacitor. (Zero is at origin)

$$\text{Zero} = 0 \text{ rads/sec} \quad \text{Pole} = \frac{1}{1\mu\text{F}(5\text{k}\Omega + 5\text{k}\Omega)} = 100 \text{ rads/sec}$$

$$\omega_L \approx \sqrt{(507)^2 + (100)^2 - 2(2)^2} = 517 \text{ rads/sec} \Rightarrow f_L = 82.3 \text{ Hz}$$

