

Homework Assignment No. 1 – Solutions**Problem 1**

(a.) The first thing to do is to find Thevenin's equivalent circuit seen from the diode.

The Thevenin voltage is,

$$V_{TH} = V_{IN} \left(\frac{2}{3} - \frac{1}{3} \right) = \frac{V_{IN}}{3}$$

The Thevenin resistance is,

$$R_{TH} = 1\text{k}\Omega \parallel 2\text{k}\Omega + 1\text{k}\Omega \parallel 2\text{k}\Omega = \frac{4}{3} \text{ k}\Omega$$



The equivalent circuit now becomes,

Now, with $V_{IN} = 10\text{V}$, we know the diode is forward biased. Therefore, replacing it with a short-circuit gives,

$$V_D = \underline{0\text{V}} \quad \text{and} \quad I_D = \frac{10}{3} \times \frac{3}{4\text{k}\Omega} = \underline{2.5\text{mA}}$$

(b.) With $V_{IN} = -10\text{V}$, we know the diode is reverse biased. Therefore replacing it with an open-circuit gives,

$$V_D = \underline{-3.33\text{V}} \quad \text{and} \quad I_D = \underline{0\text{mA}}$$

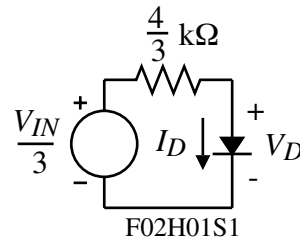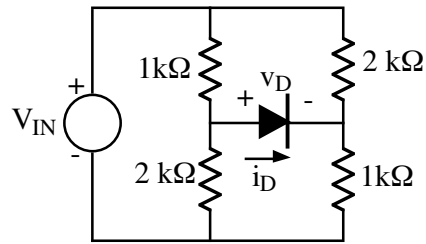



Problem 2

If $\beta_F = 100$ and $V_{BEQ} = 0.6\text{V}$, solve for the dc values of I_B , I_C , I_E , V_B , V_C , and V_E of the transistor circuit shown.

Solution

The first step is to find a Thevenin equivalent circuit seen from the base to ground. This circuit is shown below where
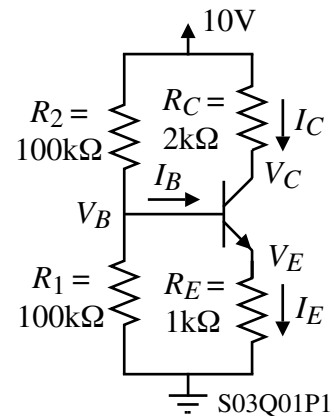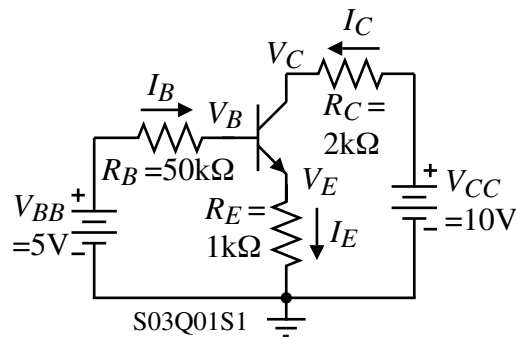
$$V_{BB} = \frac{10 \cdot R_1}{R_1 + R_2} = 5\text{V} \quad \text{and} \quad R_B = R_1 \parallel R_2 = 50\text{k}\Omega$$



The base current, I_B , can be found from the base-emitter voltage loop.

$$V_{BB} = I_B R_B + V_{BEQ} + I_B (1 + \beta_F) R_E \rightarrow I_B = \frac{V_{BB} - 0.6}{R_B + (1 + \beta_F) R_E} = \frac{4.4\text{V}}{151\text{k}\Omega} = \underline{29.14\mu\text{A}}$$

$$\therefore I_C = \beta_F I_B = \underline{2.914\text{mA}} \quad \text{and} \quad I_E = I_C + I_B = \underline{2.943\text{mA}}$$

The voltages of the transistor can be found as follows.


$$V_C = 10\text{V} - I_C R_C = 10 - 2.914\text{mA} \cdot 2\text{k}\Omega = 10 - 5.83 = \underline{4.17\text{V}}$$

$$V_E = I_E R_E = 2.942\text{mA} \cdot 1\text{k}\Omega = \underline{2.942\text{V}}$$

$$V_B = V_E + V_{BEQ} = 2.942 + 0.6 = \underline{3.543\text{V}}$$

Problem 3

A pnp BJT circuit is shown. (a.) Find the dc values of I_E , I_C , I_B , V_E , V_C and V_B if $\beta = 50$ and $V_{EB(\text{on})} = 0.65\text{V}$. (b.) For what value of R_C does the BJT become saturated? (Recall that saturation of a BJT corresponds to the BE and BC junctions forward biased.)

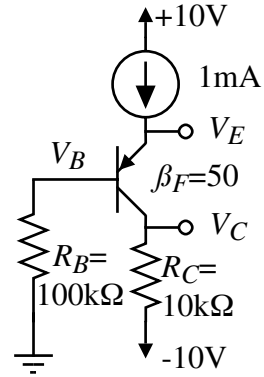Solution

(a.) Note that $I_E = 1\text{mA}$ $\alpha_F = \frac{\beta_F}{1 + \beta_F} = \frac{50}{51} = 0.98$

$$\therefore I_C = \alpha_F I_E = 0.98 \cdot 1\text{mA} = 0.98\text{mA} \Rightarrow I_C = 0.98\text{mA}$$

$$I_B = \frac{I_C}{\beta_F} = \frac{0.98\text{mA}}{50} = 19.6\mu\text{A} \Rightarrow I_B = 19.6\mu\text{A}$$


$$\text{Now, } V_B = I_B \cdot 100\text{k}\Omega = 1.96\text{V} \Rightarrow V_B = 1.96\text{V}$$

$$V_E = V_B + V_{EB(\text{on})} = 1.96\text{V} + 0.65\text{V} = 2.61\text{V} \Rightarrow V_E = 2.61\text{V}$$

$$\text{Finally, } V_C = -10\text{V} + I_C \cdot 10\text{k}\Omega = -10\text{V} + 0.98\text{mA} \cdot 10\text{k}\Omega = -0.2\text{V} \Rightarrow V_C = -0.2\text{V} \approx 0\text{V}$$

(b.) Saturation occurs when $V_{BC} = 0$ or $V_B = V_C$. Therefore, $V_C = 1.96\text{V}$. The current through R_C is still 0.98mA , so solving for R_C gives,


$$R_C = \frac{V_C + 10\text{V}}{I_C} = \frac{11.96\text{V}}{0.98\text{mA}} = 12.20\text{k}\Omega \Rightarrow R_C = 12.2\text{k}\Omega$$

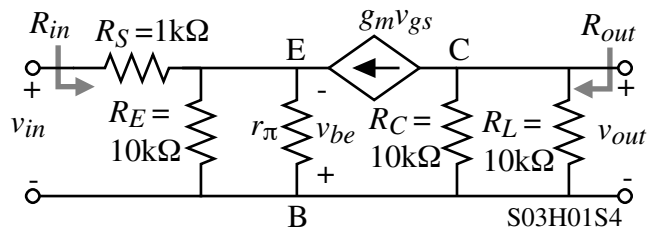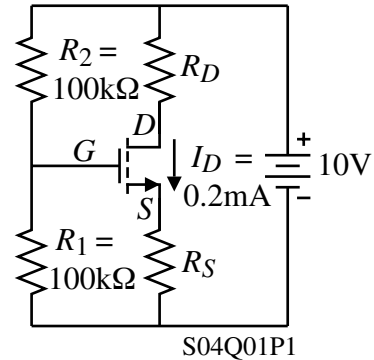

Problem 4

The NMOS transistor shown has the parameters of $K_n = 1\text{mA/V}^2$, $V_{TN} = 1\text{V}$ and $\lambda_N = 0\text{V}^{-1}$. In saturation, the large signal model is $i_D = 0.5K_n(v_{GS} - V_T)^2$.

- Assume the NMOS transistor is saturated and find the value of R_S that gives a drain current of 0.2mA .
- What value of R_D will cause the MOSFET to go from the saturation to the active region when $I_D = 0.2\text{mA}$?

Solution

- Let us solve for the value of V_{GS} that gives $I_D = 0.2\text{mA}$ when the MOSFET is saturated.

$$I_D = 0.5K_n(V_{GS} - V_{TN})^2 = 0.5(V_{GS} - 1)^2 = 0.2$$

$$0.4 = V_{GS}^2 - 2V_{GS} + 1 \quad \rightarrow \quad V_{GS}^2 - 2V_{GS} + 0.6 = 0$$

$$\therefore V_{GS} = 1 \pm 0.5\sqrt{4 - 0.6(4)} = 1 \pm 0.5\sqrt{1.6} = 1 \pm 0.632\text{V} \quad \rightarrow \quad V_{GS} = 1.632\text{V} \quad (2)$$

Since we know that $V_G = 5\text{V}$ (1), then $V_S = 5 - 1.632 = 3.367\text{V}$

Therefore,
$$R_S = \frac{V_S}{I_D} = \frac{3.367}{0.2\text{mA}} = \underline{16.84\text{k}\Omega} \quad (3)$$

- To find the value of R_D that will cause the MOSFET to leave the saturation region and enter the active region, we will use the following relationship that gives the conditions at the boundary of the two regions.

$$V_{DS} = V_{GS} - V_{TN} \quad (1)$$

This relationship can be rewritten as,

$$V_D - V_S = V_G - V_S - V_{TN} \quad \rightarrow \quad V_D = V_G - V_{TN} = V_G - 1 \quad (1)$$

Therefore, $V_D = 5 - 1 = 4\text{V}$ is when the MOSFET will be at the boundary of the two regions. Thus, the voltage drop across R_D is 6V and the current through it is 0.2mA .

From Ohm's law, we get,

$$R_D = \frac{(10 - V_D)}{I_D} = \frac{6\text{V}}{0.2\text{mA}} = \underline{30\text{k}\Omega} \quad (2)$$

Problem 5

The following questions give the dc voltages at the terminals of an active device. You are to calculate the designated dc current.

- a.) Find the diode current, I_D , where $I_S = 100\text{fA}$ and $V_T = 0.025\text{V}$ (2 pts).


Obviously, the diode is forward biased. Therefore,

$$I_D = I_S \exp\left(\frac{V_D}{V_T}\right) = 10^{-13} \exp\left(\frac{0.6}{0.025}\right) = \underline{2.65 \text{ mA}}$$

- b.) Find the drain-source current, I_{DS} , where $K_n' = 25\mu\text{A}/\text{V}^2$, $V_{TN} = 1\text{V}$ and $W/L = 10$ (2 pts).

We see that the enhancement, n-channel MOSFET is in the saturation region. Therefore,
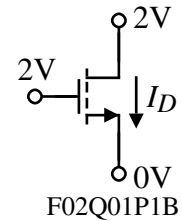
$$I_{DS} = \frac{K_n' W}{2L} (V_{GS} - V_{TN})^2 = \frac{25 \cdot 10}{2} (2-1)^2 = \underline{125 \mu\text{A}}$$




- c.) Find the collector, emitter, and base currents, I_C , I_E , and I_B if $I_S = 100\text{fA}$, $V_T = 0.025\text{V}$ and $\beta_F = 100$ (4 pts).

We see that the npn BJT is in the forward active region. Therefore,

$$I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) = 10^{-13} \exp\left(\frac{0.7}{0.025}\right) = \underline{144.6 \text{ mA}}$$
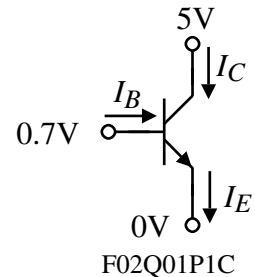
$$I_B = \frac{I_C}{\beta_F} = \underline{1.446 \text{ mA}} \quad \text{and} \quad I_E = I_C + I_B = \underline{146 \text{ mA}}$$



- d.) Repeat (b.) if $V_D = 1\text{V}$ and $V_G = 3\text{V}$ (2 pts).

We see that the enhancement, n-channel MOSFET is in the linear region. Therefore,

$$I_{DS} = K_n' \frac{W}{L} \left(V_{GS} - V_{TN} - \frac{V_{DS}}{2} \right) V_{DS} = 25 \cdot 10 (3-1-0.5)(1) = \underline{375 \mu\text{A}}$$