


Homework Assignment No. 2 - Solutions**Problem 10.20 (11.16)**

$$g_{11} = \left. \frac{\mathbf{i}_1}{\mathbf{v}_1} \right|_{\mathbf{i}_2=0} : \mathbf{v}_1 = 10^4 \mathbf{i}_1 + 101 \mathbf{i}_1 (240 \text{ k}\Omega) \rightarrow g_{11} = 4.124 \times 10^{-8} \text{ S} = 4.12 \times 10^{-8} \text{ S}$$

$$g_{12} = \left. \frac{\mathbf{i}_1}{\mathbf{i}_2} \right|_{\mathbf{v}_1=0} : \mathbf{i}_1 = -\frac{240 \text{ k}\Omega}{240 \text{ k}\Omega + 10 \text{ k}\Omega} (\mathbf{i}_2 + 100 \mathbf{i}_1) \rightarrow g_{12} = -9.90 \times 10^{-3}$$

$$g_{21} = \left. \frac{\mathbf{v}_2}{\mathbf{v}_1} \right|_{\mathbf{i}_2=0} : \mathbf{v}_2 = 101 \mathbf{i}_1 (240 \text{ k}\Omega) \mid \mathbf{i}_1 = g_{11} \mathbf{v}_1 \rightarrow g_{21} = 1.00$$

$$g_{22} = \left. \frac{\mathbf{v}_2}{\mathbf{i}_2} \right|_{\mathbf{v}_1=0} : \mathbf{i}_2 = \frac{\mathbf{v}_2}{240 \text{ k}\Omega} + \frac{\mathbf{v}_2}{10 \text{ k}\Omega} + 100 \frac{\mathbf{v}_2}{10 \text{ k}\Omega} \rightarrow g_{22} = 99.0 \text{ }\Omega$$

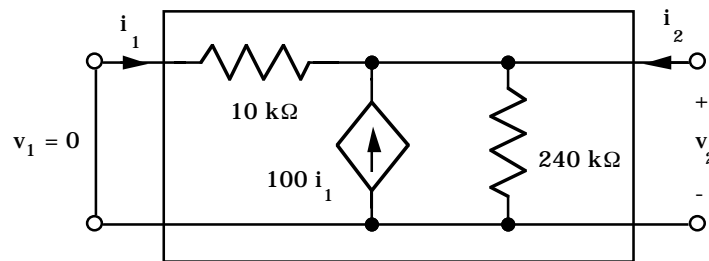**Problem 10.48 (11.34)**

$$V_O = V_S \frac{R_{IN}}{R_{IN} + R_S} A \frac{R_{IN}}{R_{IN} + R_{OUT}} A \frac{R_L}{R_L + R_{OUT}}$$

$$A_V = \frac{5000}{5000 + 1000} (-1000) \frac{5000}{5000 + 250} (-1000) \frac{100}{100 + 250} = +2.27 \times 10^5$$

$$A_I = \frac{I_O}{I_S} = \frac{2.27 \times 10^5 V_S}{100} \frac{1}{\frac{V_S}{6000}} = +1.36 \times 10^7$$

$$A_P = \frac{2.27 \times 10^5 V_S (+1.36 \times 10^7 I_S)}{V_S I_S} = +3.09 \times 10^{12}$$

Problem 10.57 (11.37)


$$A_V = \frac{2\pi \times 10^7 \text{ s}}{(s + 20\pi)(s + 2\pi \times 10^4)} = \frac{1000 \text{ s}}{(s + 20\pi) \left(1 + \frac{s}{2\pi \times 10^4}\right)} \mid A_{\text{mid}} = +1000 = 60 \text{ dB}$$

$$f_L = \frac{20\pi}{2\pi} = 10 \text{ Hz} \mid f_H = \frac{2\pi \times 10^4}{2\pi} = 10 \text{ kHz} \mid \text{BW} = 10 \text{ kHz} - 10 \text{ Hz} = 9.99 \text{ kHz}$$

Bandpass Amplifier

Problem 10.63 (11.43)

Using MATLAB: `n=[2e7*pi 0]; d=[1 (20*pi+2e4*pi) 40e4*pi^2]; bode(n,d)`

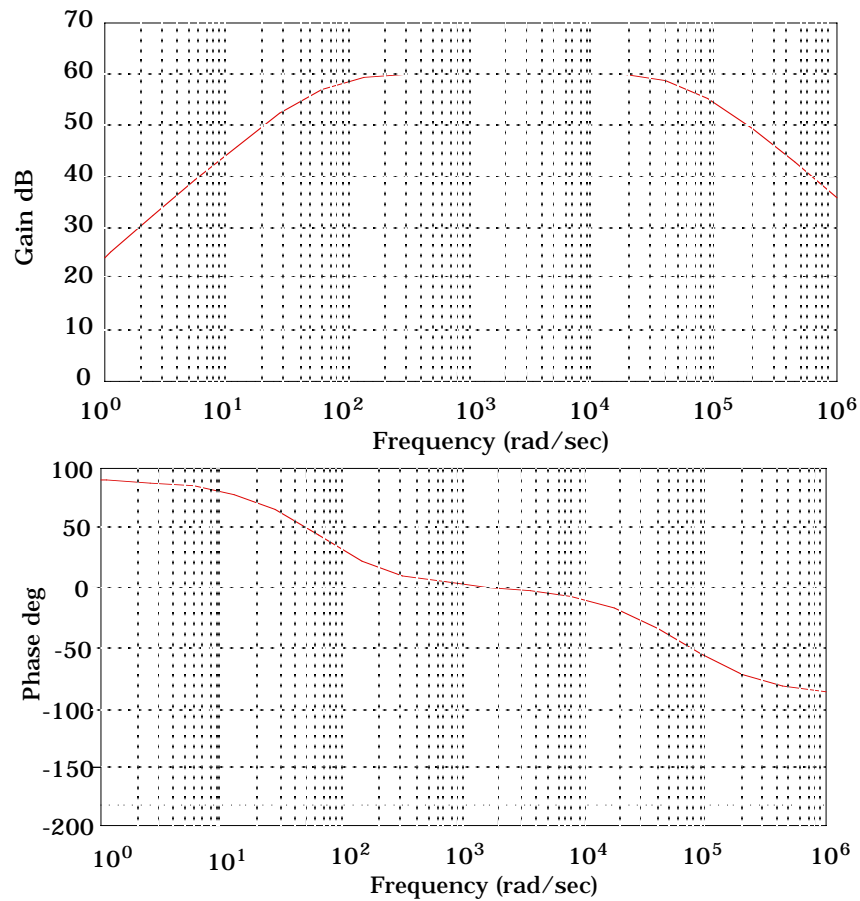Problem 10.75 (11.55)

$$(a) A_{\text{mid}} = +10^{\frac{20}{20}} = +10 \quad | \quad A_V = \frac{10}{1 + \frac{s}{2\pi \times (5 \times 10^6)}} = \frac{10}{1 + \frac{s}{10^7 \pi}} = \frac{10^8 \pi}{s + 10^7 \pi}$$

$$(b) A_{\text{mid}} = -10^{\frac{20}{20}} = -10 \quad | \quad A_V = -\frac{10^8 \pi}{s + 10^7 \pi}$$