

**Homework Assignment No. 5 - Solution**

1.) Problem 13.102 (13.91) of the text.

$$g_m = \sqrt{2\left(500 \frac{\mu A}{V^2}\right)(100 \mu A)(1 + 0.02(5))} = 332 \mu S \quad | \quad r_o = \frac{50 + 5V}{100 \mu A} = 550 k\Omega$$

$$A_v = -\left(\frac{6.8 M\Omega}{6.8 M\Omega + 0.1 M\Omega}\right)(332 \mu S)(550 k\Omega \| 50 k\Omega \| 120 k\Omega) = -10.9$$

2.) Problem 13.111 (13.100) of the text. [ $A_v = -4.60 \text{ V/V}$ ]

$$g_m = \frac{2}{3} \sqrt{1mA(1mA)[1 + 0.015(9)]} = 710 \mu S \quad | \quad r_o = \frac{\frac{1}{0.015} + 9V}{1mA} = 75.7 k\Omega$$

$$A_v = -\left(\frac{1 M\Omega}{1 M\Omega + 10 k\Omega}\right)(710 \mu S)(75.7 k\Omega \| 7.5 k\Omega \| 160 k\Omega) = -4.60 \text{ V/V}$$

3.) Problem 13.118 (13.108) of the text.


$$R_{in} = R_G = 6.8 M\Omega \quad | \quad R_{out} = 50 k\Omega \| r_o$$

$$r_o = \frac{(50 + 5)V}{0.1mA} = 550 k\Omega \quad | \quad R_{out} = 50 k\Omega \| 550 k\Omega = 45.8 k\Omega$$

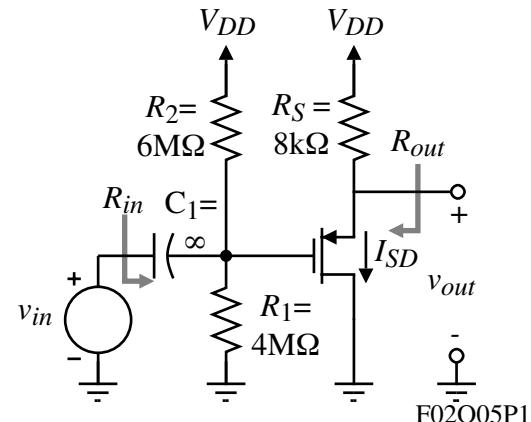4.) A PMOS common-drain amplifier is shown.

Assume the parameters of the transistor are  $k_F =$


$0.5 \text{ mA/V}^2$ ,  $V_{TP} = -1 \text{ V}$ , and  $\lambda = 0$ . (a.) If  $I_{SD} = 0.5 \text{ mA}$ , find the small signal model parameter values for  $g_m$  and  $r_o$ . (b.) Find an algebraic expression for the small signal input resistance,  $R_{in}$ , the output resistance,  $R_{out}$ , and the voltage gain,  $v_{out}/v_{in}$ . (c.) Numerically evaluate the small signal input resistance,  $R_{in}$ , the output resistance,  $R_{out}$ , and the voltage gain,  $v_{out}/v_{in}$ .



Solution

(a.)  $g_m = \sqrt{2I_{SD}k_P} = \sqrt{2 \cdot 0.5 \cdot 0.5} \text{ mS} = 0.707 \text{ mS}$  and  $r_o = \infty$

(b.) First we need a small signal model.

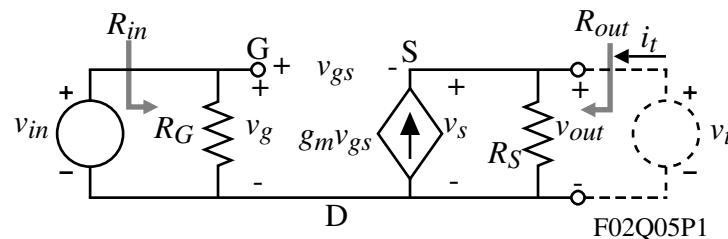

Obviously,  $R_{in} = R_G = R_1 \| R_2$ . For  $R_{out}$  we apply the voltage source,  $v_t$ , and set  $v_{in} = 0$  and solve for  $v_t/i_t$  which is equivalent to  $R_{out}$ .

## Problem 4 - Continued

$$\begin{aligned}\therefore i_t &= G_S v_t - g_m v_{gs} = G_S v_t - g_m(v_g - v_s) = G_S v_t - g_m(0 - v_s) \\ &= G_S v_t + g_m v_s = G_S v_t + g_m v_t = (G_S + g_m) v_t\end{aligned}$$


$$\therefore R_{out} = \frac{v_t}{i_t} = \frac{1}{G_S + g_m} = \frac{R_S}{1 + g_m R_S} \rightarrow \boxed{R_{out} = \frac{R_S}{1 + g_m R_S}}$$

The output voltage can be expressed as,


$$\begin{aligned}v_{out} &= g_m R_S v_{gs} = g_m R_S (v_g - v_s) = g_m R_S (v_{in} - v_{out}) \\ \therefore v_{out}(1 + g_m R_S) &= g_m R_S v_{in} \rightarrow \boxed{\frac{v_{out}}{v_{in}} = \frac{g_m R_S}{1 + g_m R_S}}\end{aligned}$$

$$(c.) R_{in} = R_G = R_1 \parallel R_2 = \underline{2.4M\Omega}, R_{out} = \frac{8k\Omega}{1+0.707 \cdot 8} = \underline{1.2k\Omega} \text{ and } \frac{v_{out}}{v_{in}} = \frac{0.707 \cdot 8}{1+0.707 \cdot 8} = \underline{0.85V/V}$$

5.) A NMOS common-source inverting amplifier is shown. Assume the parameters of the transistor are  $K_N = 1\text{mA/V}^2$ ,  $V_{TN} = 1\text{V}$ , and  $\lambda = 0$ . (a.) Find the small signal model parameter values for  $g_m$  and  $r_{ds}$ . (b.) Find an algebraic expression for the small signal input resistance,  $R_{in}$ , the output resistance,  $R_{out}$ , and the voltage gain,  $v_{out}/v_s$ . (c.) Numerically evaluate the small signal input resistance,  $R_{in}$ , the output resistance,  $R_{out}$ , and the voltage gain,  $v_{out}/v_s$ .

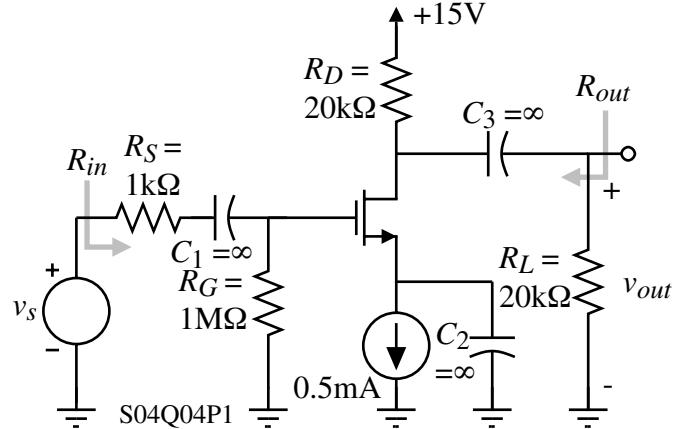Solution

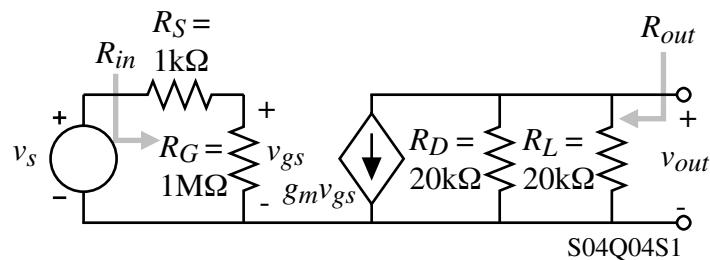(a.) Small-signal model (Note the dc current source is replaced by an infinite):



$$\text{Find } g_m \text{ and } r_{ds}: \quad g_m = \sqrt{2K_N I_D} = \sqrt{2 \cdot 1 \cdot 0.5} = \underline{1\text{mS}} \quad \text{and} \quad r_{ds} = \underline{\infty} \text{ (ignore } V_{DS})$$

(b.) Find  $R_{in}$ ,  $R_{out}$ , and  $v_{out}/v_s$ .

$$\boxed{R_{in} = R_S + R_G}$$

$$\boxed{R_{out} = R_D \parallel R_L}$$

Problem 5 - Continued

$$\frac{v_{out}}{v_s} = \frac{v_{out}}{v_{gs}} \frac{v_{gs}}{v_s} = (-g_m R_{out}) \left( \frac{R_G}{R_G + R_S} \right) = -g_m \left( \frac{R_D R_L}{R_D + R_L} \right) \left( \frac{R_G}{R_G + R_S} \right)$$

$$\boxed{\frac{v_{out}}{v_s} = -g_m \left( \frac{R_D R_L}{R_D + R_L} \right) \left( \frac{R_G}{R_G + R_S} \right)}$$

(c.) Evaluate  $R_{in}$ ,  $R_{out}$ , and  $v_{out}/v_s$ ..

$$R_{in} = 1\text{k}\Omega + 1\text{M}\Omega \approx \underline{1\text{M}\Omega} \quad R_{out} = R_D \parallel R_L = \underline{10\text{k}\Omega}$$

$$\frac{v_{out}}{v_s} = \frac{v_{out}}{v_{gs}} \frac{v_{gs}}{v_s} = -g_m \left( \frac{R_D R_L}{R_D + R_L} \right) \left( \frac{R_G}{R_G + R_S} \right) = (-1\text{mS})(10\text{k}\Omega)(1) = \underline{-10\text{V/V}}$$