


Homework Assignment No. 5

Due on Monday, September 20, 2004

Problems in () refer to the first edition.

- 1.) Problem 13.102 (13.91) of the text.
- 2.) Problem 13.111 (13.100) of the text. [$A_v = -4.60$ V/V]
- 3.) Problem 13.118 (13.108) of the text.

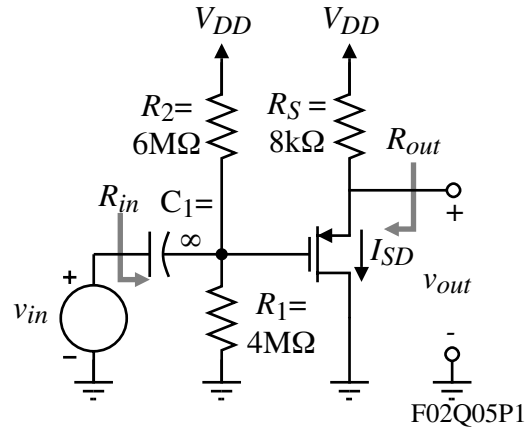- 4.) A PMOS common-drain amplifier is shown. Assume the parameters of the transistor are $k_F = 0.5\text{mA/V}^2$, $V_{TP} = -1\text{V}$, and $\lambda = 0$. (a.) If $I_{SD} = 0.5\text{mA}$, find the small signal model parameter values for g_m and r_o . (b.) Find an algebraic expression for the small signal input resistance, R_{in} , the output resistance, R_{out} , and the voltage gain, v_{out}/v_{in} . (c.) Numerically evaluate the small signal input resistance, R_{in} , the output resistance, R_{out} , and the voltage gain, v_{out}/v_{in} .



- 5.) A NMOS common-source inverting amplifier is shown. Assume the parameters of the transistor are $K_N = 1\text{mA/V}^2$, $V_{TN} = 1\text{V}$, and $\lambda = 0$. (a.) Find the small signal model parameter values for g_m and r_{ds} . (b.) Find an algebraic expression for the small signal input resistance, R_{in} , the output resistance, R_{out} , and the voltage gain, v_{out}/v_{in} . (c.) Numerically evaluate the small signal input resistance, R_{in} , the output resistance, R_{out} , and the voltage gain, v_{out}/v_{in} .

