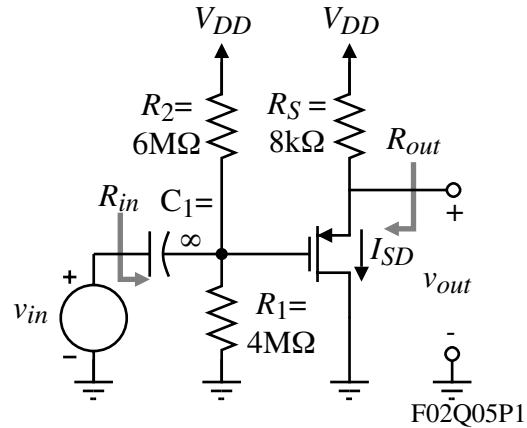


Homework Assignment No. 6 - Solution

1 An NPN BJT common-emitter inverting amplifier is shown. Assume the parameters of the transistor are $\beta_o = 100$, $V_T = 25\text{mV}$, and $V_A = 100\text{V}$. (a.) If $I_C = 0.5\text{mA}$ and $V_{CE} = 3\text{V}$, find the small signal model parameter values for g_m , r_π and r_o . (b.) Find the numerical value for the small signal voltage gain, v_{out}/v_{in} , the input resistance, R_{in} , and the output resistance, R_{out} . Assume $r_o = \infty$ in this part of the problem.

**Solution**

$$(a.) \quad g_m = \frac{I_C}{V_T} = \frac{0.5\text{mA}}{25\text{mV}} = \underline{20\text{mS}}$$

$$r_\pi = \beta_F \frac{V_T}{I_C} = \frac{100}{20\text{mS}} = \underline{5\text{k}\Omega}$$

$$r_o = \frac{V_A + V_{CE}}{I_C} = \frac{102}{0.5\text{mA}} = \underline{204\text{k}\Omega}$$

(b.) The small signal model for this problem is shown (note a current controlled generator has been chosen for this problem).


Using the BE impedance reflection principle we get,

$$R_{in} = r_\pi + (1 + \beta_o)R_E \\ = 5\text{k}\Omega + (101)1\text{k}\Omega = \underline{106\text{k}\Omega}$$

($R_B = R_1 \parallel R_2$ is not part of this because it is in parallel with v_{in} and is not a part of R_{in} .)

$$R_{out} = R_C = \underline{10\text{k}\Omega}$$
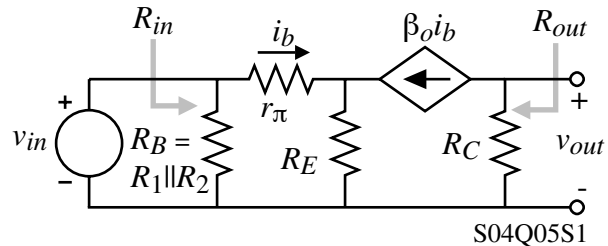
$$\frac{v_{out}}{v_{in}} = \left(\frac{v_{out}}{i_b} \right) \left(\frac{i_b}{v_{in}} \right) = (-\beta_o R_C) \left(\frac{1}{R_{in}} \right) = \frac{-100 \cdot 10\text{k}\Omega}{106\text{k}\Omega} = \underline{-9.434 \text{ V/V}}$$



2.) Problem 14.16 (no equivalent problem in first edition of the text).

$$V_{EQ} = 12 \frac{62k\Omega}{20k\Omega + 62k\Omega} = 9.07V \quad | \quad R_{EQ} = 20k\Omega || 62k\Omega = 15.1k\Omega$$

$$I_B = \frac{(12 - 0.7 - 9.07)V}{15.1k\Omega + (75 + 1)3.9k\Omega} = 7.16\mu A \quad | \quad I_C = 537 \mu A \quad | \quad V_{EC} = 12 - 3900I_E - 8200I_C = 5.47 V$$

Active region is correct. $| \quad r_\pi = \frac{75(0.025V)}{537\mu A} = 3.49k\Omega \quad | \quad V_A$ not specified, choose $r_o = \infty$

$$R_{in} = 15.1k\Omega || 3.49k\Omega = 2.83 k\Omega \quad | \quad R_{out} = r_o || 8.2k\Omega = 8.2 k\Omega \quad | \quad g_m = 40I_C = 21.5 mS$$

$$R_L = r_o || 8.2k\Omega || 100k\Omega = 8.2k\Omega || 100k\Omega = 7.58k\Omega$$

$$A_v = -g_m R_L \left(\frac{R_{in}}{R_I + R_{in}} \right) = -(21.5mS)(7.58k\Omega) \left(\frac{2.83k\Omega}{1k\Omega + 2.83k\Omega} \right) = -120$$

$$A_i = \frac{R_B}{R_B + r_\pi} (-\beta_o) \frac{R_{out}}{R_{out} + R_3} = \frac{15.1k\Omega}{15.1k\Omega + 3.49k\Omega} (-75) \frac{8.2k\Omega}{8.2k\Omega + 100k\Omega} = -4.62$$

$$v_{be} = v_i \frac{R_{in}}{R_I + R_{in}} = v_i \frac{2.83k\Omega}{1k\Omega + 2.83k\Omega} = 0.739v_i \quad | \quad v_i = \frac{5.00mV}{0.739} = 6.76 mV$$

$A_v \cong -10V_{CC} = -10(12) = -120.$ $|$ The voltage gain is identical to the rule - of - thumb estimate.

3.) Problem 14.19 (14.15) of the text.

$$V_{GS} = -(11k\Omega)I_D = -(11k\Omega)(20mA) \left(1 - \frac{V_{GS}}{-4} \right)^2 \rightarrow V_{GS} = -3.50V, I_D = -\frac{V_{GS}}{11k\Omega} = 318 \mu A$$

$$V_{DS} = 20 - I_D(11k\Omega + 39k\Omega) = 4.10V \quad | \quad \text{Active region operation is correct.}$$

$$g_m = \frac{2}{|-4|} \sqrt{20mA(318\mu A)} = 1.26mS \quad | \quad \text{Assume } \lambda = 0, r_o = \infty. \quad | \quad R_L = 39k\Omega || 500k\Omega = 36.2k\Omega$$

$$R_{in} = R_G = 1.00 M\Omega \quad | \quad R_{out} = 39k\Omega$$

$$A_v = -\frac{g_m R_L}{1 + g_m R_S} \left(\frac{R_{in}}{R_I + R_{in}} \right) = -\frac{1.26mS(36.2k\Omega)}{1 + 1.26mS(11k\Omega)} \left(\frac{1M\Omega}{500\Omega + 1M\Omega} \right) = -3.07$$

$$A_i = -R_G \left(\frac{g_m}{1 + g_m R_S} \right) \left(\frac{R_D}{R_D + R_3} \right) = -10^6 \left[\frac{1.26mS}{1 + 1.26mS(11k\Omega)} \right] \left(\frac{39k\Omega}{39k\Omega + 500k\Omega} \right) = -6.14$$

$$v_{gs} = \frac{R_{in}}{R_I + R_{in}} v_i = 1.00v_i \quad | \quad V_{GS} - V_P = -3.5 - (-4) = 0.500V$$

$$v_{gs} \leq 0.2(V_{GS} - V_P)(1 + g_m R_S) \quad | \quad v_i \leq 0.2(0.5)[1 + 1.26mS(11k\Omega)] = 1.49 V$$

4.) Problem 14.27 (14.21) of the text.

$$V_{EQ} = 18 \frac{51k\Omega}{51k\Omega + 100k\Omega} = 6.08V \quad | \quad R_{EQ} = 51k\Omega || 100k\Omega = 33.8k\Omega$$

$$I_B = \frac{(6.08 - 0.7 + 18)V}{33.8k\Omega + (126)(4.7k\Omega)} = 37.3\mu A \quad | \quad I_C = 4.67 \text{ mA} \quad | \quad V_{CE} = 36 - 2000I_C - 4700I_E = 4.54 \text{ V}$$

$$\text{Active region is correct. } | \quad r_\pi = \frac{125(0.025V)}{4.67mA} = 669\Omega \quad | \quad r_o = \frac{(50 + 4.54)V}{4.67mA} = 11.7k\Omega$$

$$R_B = R_1 || R_2 = 51k\Omega || 100k\Omega = 33.8k\Omega \quad | \quad R_L = R_3 || R_E || r_o = 24k\Omega || 4.7k\Omega || 11.7k\Omega = 2.94k\Omega$$

$$R_{in} = R_B || [r_\pi + (\beta_o + 1)R_L] = 33.8k\Omega || [669\Omega + (126)(2.94k\Omega)] = 31.0 \text{ k}\Omega$$

$$A_v = + \frac{(\beta_o + 1)R_L}{r_\pi + (\beta_o + 1)R_L} \left(\frac{R_{in}}{R_I + R_{in}} \right) = \frac{126(2.94k\Omega)}{0.669k\Omega + 126(2.94k\Omega)} \left(\frac{31.0k\Omega}{500\Omega + 31.0 \text{ k}\Omega} \right) = 0.982$$

$$v_{be} = v_i \left(\frac{R_{in}}{R_I + R_{in}} \right) \left(\frac{r_\pi}{r_\pi + (\beta_o + 1)R_L} \right) = \left(\frac{31.0k\Omega}{500\Omega + 31.0 \text{ k}\Omega} \right) \left[\frac{0.669k\Omega}{0.669k\Omega + 126(2.94k\Omega)} \right] = 1.77 \times 10^{-3} v_i$$

$$v_i \leq \frac{0.005V}{1.77 \times 10^{-3}} = 2.82 \text{ V} \quad | \quad R_{out} = R_E || \frac{(R_B || R_I) + r_\pi}{\beta_o + 1} = 4.7k\Omega || \frac{(33.8k\Omega || 500\Omega) + 669\Omega}{126} = 9.22 \Omega$$

5.) Problem 14.28 (14.23) of the text

$$V_{GS} = 5V \quad | \quad I_D = \frac{4 \times 10^{-4}}{2} (5 - 1)^2 = 3.2 \text{ mA} \quad | \quad V_{DS} = 5 - (-5) = 10V \quad - \text{ Pinchoff region}$$

$$\text{operation is correct. } | \quad g_m = \sqrt{2(4 \times 10^{-4})(3.2 \text{ mA})[1 + 0.02(10)]} = 1.75 \text{ mS}$$

$$r_o = \frac{1}{0.02} + 10 \frac{V}{\text{mA}} = 18.8 \text{ k}\Omega \quad - \text{ Cannot neglect! } \quad | \quad R_L = 18.8 \text{ k}\Omega || 100 \text{ k}\Omega = 15.8 \text{ k}\Omega$$

$$R_{in} = R_G = 1 \text{ M}\Omega \quad | \quad R_{out} = \frac{1}{g_m} || r_o = 555 \Omega$$

$$A_v = + \frac{R_{in}}{R_I + R_{in}} \left(\frac{g_m R_L}{1 + g_m R_L} \right) = + \frac{1 \text{ M}\Omega}{10 \text{ k}\Omega + 1 \text{ M}\Omega} \left(\frac{1.75 \text{ mS}(15.8 \text{ k}\Omega)}{1 + 1.75 \text{ mS}(15.8 \text{ k}\Omega)} \right) = 0.956$$

$$v_{gs} = v_i \left(\frac{R_{in}}{R_I + R_{in}} \right) \left(\frac{1}{1 + g_m R_L} \right) = v_i \left(\frac{10^6 \Omega}{10^4 \Omega + 10^6 \Omega} \right) \left[\frac{1}{1 + 1.75 \text{ mS}(15.8 \text{ k}\Omega)} \right] = 0.0346 v_i$$

$$v_i \leq \frac{0.2(5 - 1)}{0.0346} = 23.2 \text{ V} \quad \text{But, } v_{DS} \text{ must exceed } v_{GS} - V_{TN} \cong V_{GS} - V_{TN} = 4V \text{ for pinchoff.}$$

$$V_{DS} = 10 - v_o = 10 - 0.956 v_i \geq 4 \rightarrow v_i \leq 6.28 \text{ V} \quad - \text{ Limited by the Q - point voltages}$$