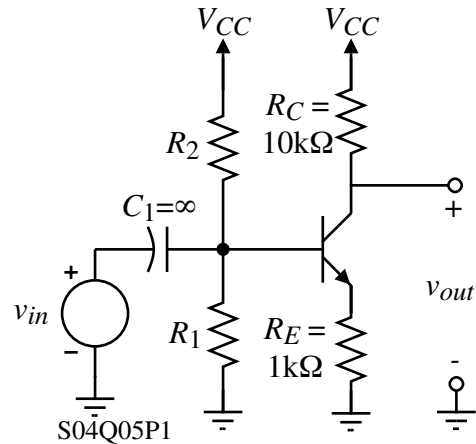


Homework Assignment No. 6Due on Monday, September 27, 2004

Problems in first edition are indicated in ().

1.) An NPN BJT common-emitter inverting amplifier is shown. Assume the parameters of the transistor are $\beta_F = 100$, $V_T = 25\text{mV}$, and $V_A = 100\text{V}$. (a.) If $I_C = 0.5\text{mA}$ and $V_{CE} = 3\text{V}$, find the small signal model parameter values for g_m , r_π and r_o . (b.) Find the numerical value for the small signal voltage gain, v_{out}/v_{in} , the input resistance, R_{in} , and the output resistance, R_{out} . Assume $r_o = \infty$ in this part of the problem.



- 2.) Problem 14.16 (no equivalent problem in first edition of the text).
- 3.) Problem 14.19 (14.15) of the text.
- 4.) Problem 14.27 (14.21) of the text.
- 5.) Problem 14.28 (14.23) of the text