

Homework Assignment No. 13 - Solutions



Problem 1

Use the method of feedback analysis to find v_2/v_1 , $R_{in} = v_1/i_1$, and $R_{out} = v_2/i_2$. Assume that all transistors are matched and that $g_{m1} = g_{m2} = 1\text{mS}$. Neglect r_{ds} .

Solution

The topology is series-series.

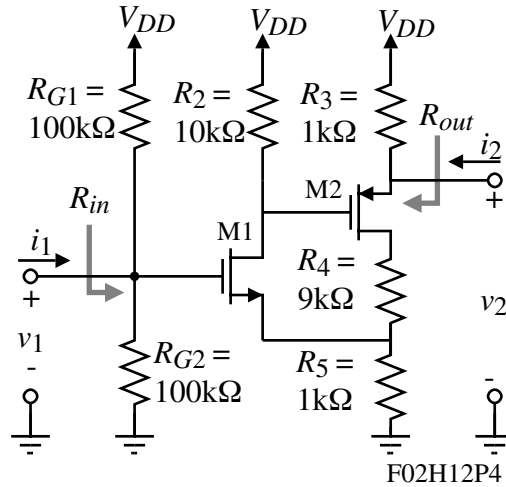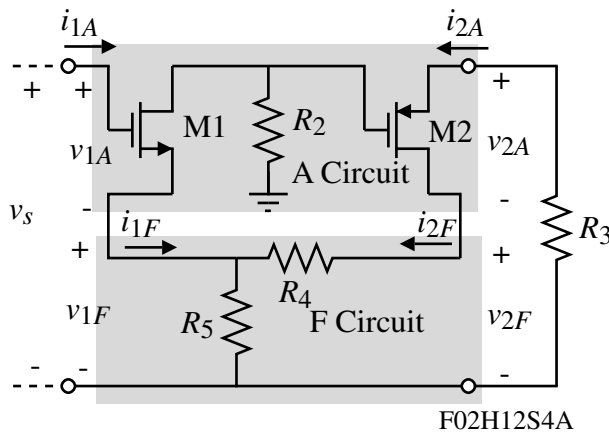The circuit is redrawn below in order to help identify the various terms for the analysis:





$$z_{11F} = \left. \frac{v_{1F}}{i_{1F}} \right|_{i_{2F}=0} = R_5 = 1\text{k}\Omega$$

$$z_{22F} = \left. \frac{v_{2F}}{i_{2F}} \right|_{i_{1F}=0} = R_4 + R_5 = 10\text{k}\Omega$$

$$z_{12F} = \beta = \left. \frac{v_{1F}}{i_{2F}} \right|_{i_{1F}=0} = R_5 = 1\text{k}\Omega$$

Calculation of the A circuit:

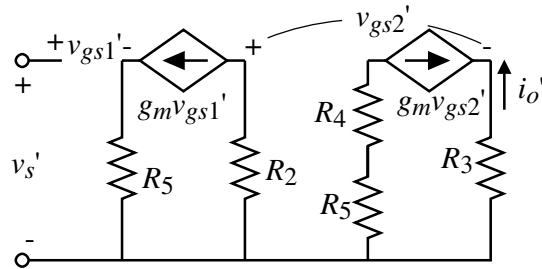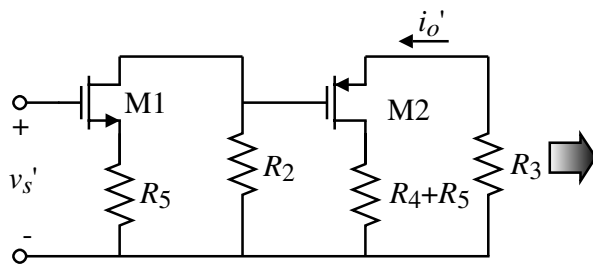

$$A = \frac{i_o'}{v_s'} = \left(\frac{i_o'}{v_{gs2'}} \right) \left(\frac{v_{gs2'}}{v_{gs1'}} \right) \left(\frac{v_{gs1'}}{v_s'} \right) = (-g_m) \left(\frac{-g_m R_2}{1 + g_m R_3} \right) \left(\frac{1}{1 + g_m R_5} \right) = (10^{-3})(-5)(-0.5) = 2.5 \text{ mS}$$

$$\therefore \frac{i_o}{v_s} = \frac{A}{1 + A\beta} = \frac{2.5\text{mS}}{1 + 2.5} = 0.714\text{mS}$$

Since, $z_{11A} = \infty$, then $R_{in} = 50\text{k}\Omega \parallel \infty = \underline{50\text{k}\Omega}$

$$\frac{v_2}{v_1} = \frac{-i_o R_3}{v_s} = \frac{-i_o}{v_s} R_3 = -0.714\text{mS}(1\text{k}\Omega) = \underline{-0.714 \text{ V/V}}$$


$$R_o = (z_{22T} + R_3)(1 + A\beta) = \left(\frac{1}{g_m} + R_3 \right) (1 + A\beta) = 2\text{k}\Omega(3.5) = 7\text{k}\Omega$$

However, the output resistance specified by the problem, R_{out} , is found as

$$R_{out} = (R_o - R_3) \parallel R_3 = 6\text{k}\Omega \parallel 1\text{k}\Omega = \underline{857\Omega}$$

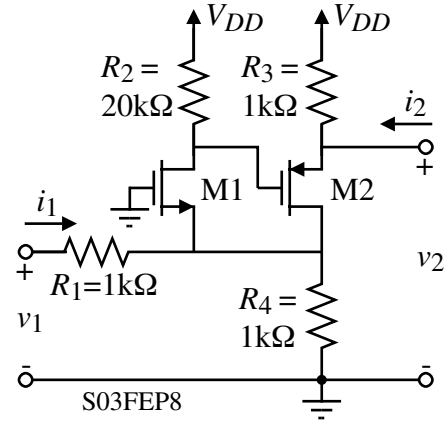
Problem 2

A feedback amplifier is shown. Use the methods of feedback analysis to find the numerical values of v_2/v_1 , v_1/i_1 , and v_2/i_2 . Assume that all transistors are matched and that $g_m = 1\text{mS}$, and $r_{ds} = \infty$.




Solution

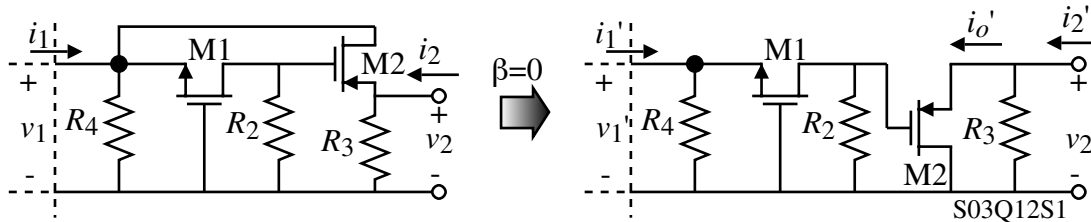The feedback circuit is shunt-series. You should know by now not to include R_1 in the feedback circuit. The simplified transistor circuit and the open-loop equivalent is shown below. It is easy to see that $\beta = i_{1F}/i_{2F} (v_{1F}=0) = -1$.



The small-signal, open-loop circuit is,

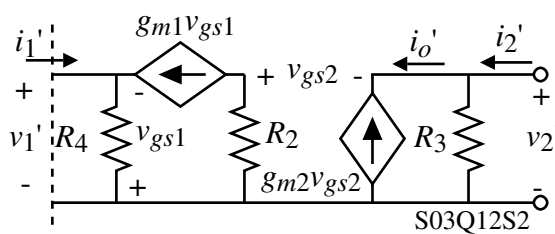

$$A = \frac{i_o'}{i_1'} = \left(\frac{i_o'}{v_{gs2}'} \right) \left(\frac{v_{gs2}'}{v_{g2}'} \right) \left(\frac{v_{g2}'}{v_{gs1}'} \right) \left(\frac{v_{gs1}'}{i_1'} \right)$$

$$v_{gs2}' = v_{g2}' - v_{s2}' = v_{g2}' - g_{m2}R_3 v_{gs2}'$$

$$\therefore v_{gs2}'(1 + g_{m2}R_3) = v_{g2}'$$

$$\text{Also, } i_1' + \frac{v_{gs1}'}{R_4} + g_{m1}v_{gs1}' = 0 \quad \Rightarrow \quad i_1' = -\left(\frac{1}{R_4} + g_{m1} \right) v_{gs1}'$$

$$\therefore A = \frac{i_o'}{i_1'} = (-g_{m2}) \left(\frac{1}{1 + g_{m2}R_3} \right) (-g_{m1}R_2) \left(\frac{-1}{\frac{1}{R_4} + g_{m1}} \right) = (-1\text{mS})(0.5)(-20)(-0.5\text{k}\Omega) = -5 \text{ A/A}$$

$$\text{Now, } \frac{i_o}{i_1} = \frac{-5}{1 + (-1)(-5)} = -\frac{5}{6} \text{ A/A}$$

$$R_{in}(\beta=0) = R_4 \parallel (1/g_{m1}) = 0.5\text{k}\Omega, \quad R_{inF} = \frac{0.5\text{k}\Omega}{1+5} = \frac{1}{12} \text{ k}\Omega = 83.33\Omega \quad \frac{v_1}{i_1} = \underline{\underline{1083.33\Omega}}$$


$$\frac{v_2}{v_1} = \frac{i_o}{i_1} \left(\frac{-R_3}{(v_1/i_1)} \right) = -\frac{5}{6} \frac{-1000}{1083.33} = \frac{10}{13} = \underline{\underline{0.7692 \text{ V/V}}}$$

$$R_o(\beta=0) = R_3 + (1/g_{m2}) = 2\text{k}\Omega, \quad R_{oF} = 2\text{k}\Omega(1+5) = 12\text{k}\Omega$$

$$\frac{v_2}{i_2} = (12\text{k}\Omega - 1\text{k}\Omega) \parallel 1\text{k}\Omega = 11\text{k}\Omega \parallel 1\text{k}\Omega = \frac{11}{12} \text{ k}\Omega = \underline{\underline{916.67\Omega}}$$

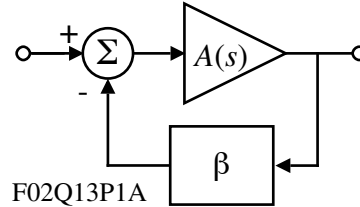Problem 3 - The amplifier in the feedback circuit shown has a transfer function of

$$A(s) = \frac{100}{\frac{s}{10^5} + 1}$$



What value of β will increase the upper -3dB frequency by a factor of 10 for the closed loop gain? What is the closed loop, low frequency gain?

Solution

$$A_F = \frac{A}{1+A\beta} = \frac{1}{\frac{1}{A} + \beta} = \frac{1}{\frac{s/10^5 + 1}{100} + \beta} = \frac{100}{\frac{s}{10^5} + 1 + 100\beta} = \left(\frac{100}{1+100\beta}\right) \frac{1}{\frac{s}{10^5(1+100\beta)} + 1}$$

$$\therefore 10^5(1+100\beta) = 10^6 \quad \rightarrow \quad 1+100\beta = 10 \quad \rightarrow \quad \underline{\underline{\beta = 9/100 = 0.09}}$$

The closed-loop, low frequency gain is,

$$A_F(0) = \frac{100}{1+100\beta} = \frac{100}{1+9} = 10 \quad \rightarrow \quad \underline{\underline{A_F(0) = 10}}$$

4.) Problem 18.40 of the text.

$$T = \frac{v_o}{v_x} = g_{m2}(r_{o2} \parallel r_{o4}) \frac{(\beta_o + 1)R}{(r_{o2} \parallel r_{o4}) + r_{\pi3} + (\beta_o + 1)R} \quad | \quad g_{m1} = 40(10^{-4}) = 4.00\text{mS}$$

$$r_{o2} = \frac{50 + 1.4}{10^{-4}} = 514\text{k}\Omega \quad | \quad r_{o4} = \frac{50 + 11.3}{10^{-4}} = 613\text{k}\Omega \quad | \quad r_{\pi3} = \frac{100(0.025)}{(12\text{V}/10\text{k}\Omega)} = 2.08\text{k}\Omega$$

$$T = (4 \times 10^{-3})(280\text{k}\Omega) \frac{(101)10\text{k}\Omega}{280\text{k}\Omega + 2.08\text{k}\Omega + 101(10\text{k}\Omega)} = 876 \quad (58.9 \text{ dB})$$

5.) Problem 18.59 of the text.

$$(a) \quad A(s) = \frac{2 \times 10^{14} \pi^2}{\left(1 + \frac{s}{2\pi \times 10^3}\right) \left(1 + \frac{s}{2\pi \times 10^5}\right)} = \frac{5 \times 10^5}{\left(1 + \frac{s}{2\pi \times 10^3}\right) \left(1 + \frac{s}{2\pi \times 10^5}\right)}$$

$A(s)$ represents a low - pass amplifier with two widely - spaced poles

Open - loop: $A_o = 5 \times 10^5 = 114\text{dB}$ | $f_L = 0$ | $f_H \cong f_1 = 1000 \text{ Hz}$

(b) A common mistake would be the following :

$$\text{Closed - loop: } f_H = 1000\text{Hz} [1 + 5 \times 10^5 (0.01)] = 5\text{MHz}$$

Oops! - This exceeds $f_2 = 100 \text{ kHz}$! This is a two - pole low - pass amplifier.

$$A_v(s) = \frac{2 \times 10^{14} \pi^2}{\left(1 + \frac{s}{2\pi \times 10^3}\right) \left(1 + \frac{s}{2\pi \times 10^5}\right) (0.01)} = \frac{2 \times 10^{14} \pi^2}{s^2 + 1.01(2\pi \times 10^5)s + 2 \times 10^{12} \pi^2}$$

Using dominant - root factorization : $f_1 = 101 \text{ kHz}$, $f_2 = 4.95 \text{ MHz}$

So the closed - loop values are $f_H = 101 \text{ kHz}$ and $f_L = 0$.