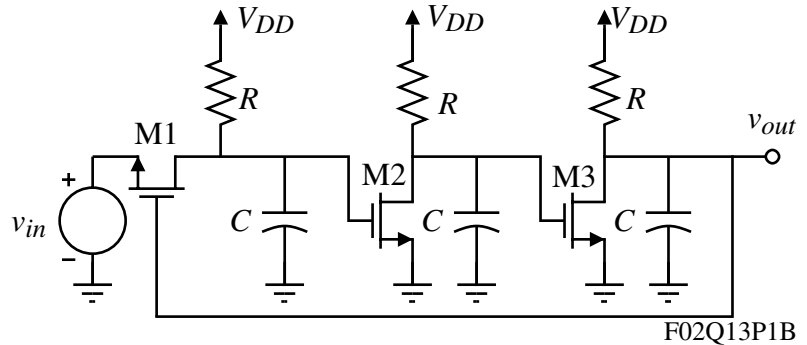



**Homework Assignment No. 14 - Solutions**

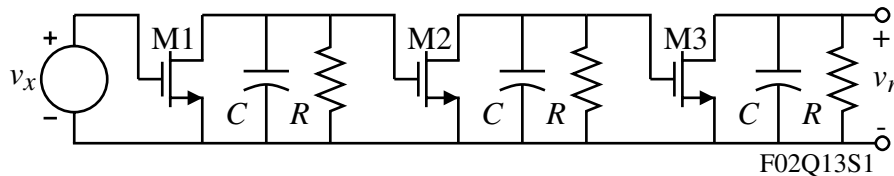1.) Find the loop gain of the amplifier shown. Assume that  $g_m = 1\text{mS}$  and  $r_{ds} = \infty$  for all MOSFETs and that  $R = 10\text{k}\Omega$  and  $C = 100\text{nF}$ .

Solution



Use the model shown to find the loop gain.



This circuit consists of three identical stages with each transfer function given as

$$A(s) = \frac{-g_m R}{sRC + 1}$$

Therefore,

$$T(s) = -\frac{v_r}{v_x} = -\left(\frac{-g_m R}{sRC + 1}\right)^3 = -\left(\frac{-10}{\frac{s}{10^3} + 1}\right)^3 = \frac{1000}{\left(\frac{s}{10^3} + 1\right)^3} \rightarrow \boxed{T(s) = \frac{1000}{\left(\frac{s}{10^3} + 1\right)^3}}$$

2.) Problem 18.71 (18.49) of the text.

$$(a) T = A\beta = \frac{2 \times 10^{14} \pi^2}{(s + 2 \times 10^3 \pi)(s + 2 \times 10^5 \pi)} \left(\frac{1}{5}\right) \quad | \quad \text{Yes, it is a second-order system and will}$$

have some phase margin, although  $\Phi_M$  may be vanishingly small.

$$(b) \text{ For } \omega \gg 2\pi \times 10^5, \quad |T(j\omega)| \approx \frac{4 \times 10^{13} \pi^2}{\omega^2} \quad \text{and } |T(j\omega)| = 1 \text{ for } \omega = 1.987 \times 10^7 \frac{\text{rad}}{\text{s}}$$

$$\angle T(j1.987 \times 10^7) = -\tan^{-1} \frac{1.987 \times 10^7}{2000\pi} - \tan^{-1} \frac{1.987 \times 10^7}{2 \times 10^5 \pi} = 178.2^\circ \rightarrow \Phi_M = 1.83^\circ \quad | \quad \text{A very small phase margin.}$$

3.) Problem 18.86 (18.61) of the text.


$$A_{v1} = \frac{V_{o1}}{V_{o2}} = -\frac{1}{sRC} \quad V_{o2} = \left(1 + \frac{2R}{2R}\right)V_+ = 2V_+$$

$$(V_+ - V_{o1})\frac{G}{2} + sCV_+ + (V_+ - V_{o2})G_F = 0 \quad \text{Combining these yields}$$

$$A_{v2} = \frac{V_{o2}}{V_{o1}} = \frac{G}{sC + \left(\frac{G}{2} - G_F\right)} \quad \text{and} \quad T(s) = A_{v1}A_{v2} = \frac{1}{sRC \left(sRC + \frac{1}{2} - \frac{R}{R_F}\right)}$$


$$\angle T(j\omega_o) = 0 \rightarrow R_F = 2R \quad \text{and} \quad |T(j\omega_o)| = 1 \rightarrow \omega_o = \frac{1}{RC}$$

4.) Problem 18.88 (18.63) of the text.

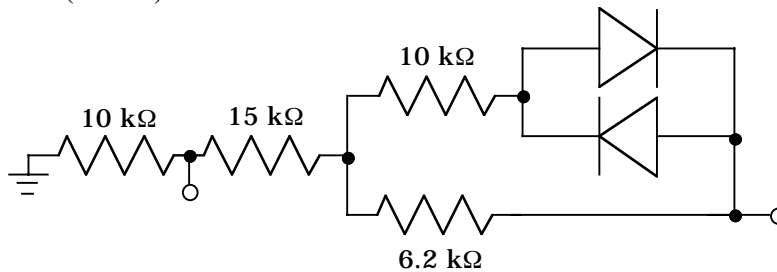

$$f_o = \frac{1}{2\pi(5k\Omega)(500pF)} = 63.7 \text{ kHz} \quad |v_o| = \frac{3(0.7V)}{\left(2 - \frac{15k\Omega}{10k\Omega}\right)\left(1 + \frac{10k\Omega}{6.2k\Omega}\right) - \frac{10k\Omega}{10k\Omega}} = 6.85 \text{ V}$$

5.) Problem 18.95 (18.70) of the text.

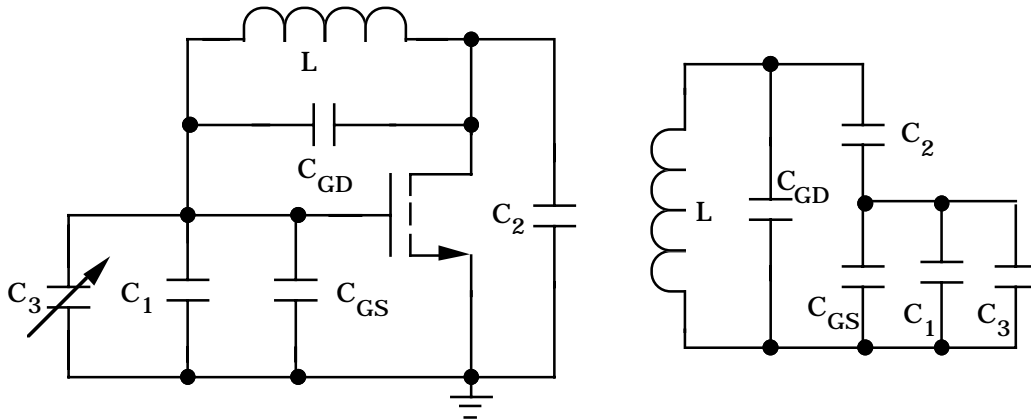

$$C_{TC} = C_{GD} + \frac{1}{\frac{1}{C_2} + \frac{1}{C_1 + C_3 + C_{GS}}} = 4pF + \frac{1}{\frac{1}{50pF} + \frac{1}{50pF + 0 + 10pF}} = 31.27pF$$

$$f_o = \frac{1}{2\pi\sqrt{LC_{TC}}} = \frac{1}{2\pi\sqrt{(10^{-5}H)(31.27 \times 10^{-12}F)}} = 9.00MHz$$

$$g_m r_o \geq \frac{C_1 + C_3 + C_{GS}}{C_2} = \frac{50pF + 0 + 10pF}{50pF} = 1.20 \quad \text{which is easily met.}$$