

Quiz #1 - Friday, Aug. 27, 9am - 9:25amToday's Lecture

- MOSFET Example 1
- MOSFET Example 2
- MOSFET Capacitances
- BJT introduction
- BJT Example 1
- BJT Example 2


Homework due in class or by 4pm to Marge Boehme  
VanLeer E274.

Nola Li 9-12 Thurs.

MOSFET Example 1

Find the dc operating point for the NMOS transistor shown


assuming  $K'_N = 25 \mu\text{A}/\text{V}^2$ ,  $\frac{W}{L} = 10$ ,  $V_{TN} = 1\text{V}$  and  $\lambda = 0$ .

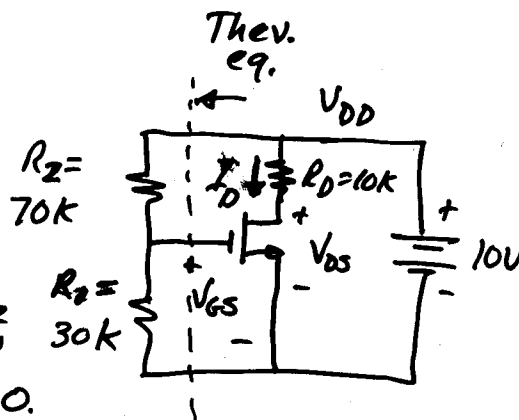Solution

Assume the MOSFET is saturated

$$I_D = \frac{K'_N}{2} \frac{W}{L} (V_{GS} - V_{TN})^2$$

Thev. eq. at GS -

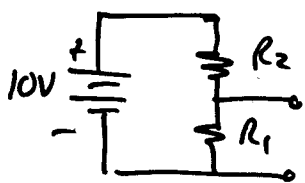


$$V_{GG} = 10 \frac{30\text{k}}{100\text{k}} = 3\text{V}$$

$$R_G = 30\text{k} \parallel 100\text{k} = 21\text{k}$$

$$V_{DS} = 10\text{V} - I_D R_D = 10\text{V} - 5\text{V} = 5\text{V}$$

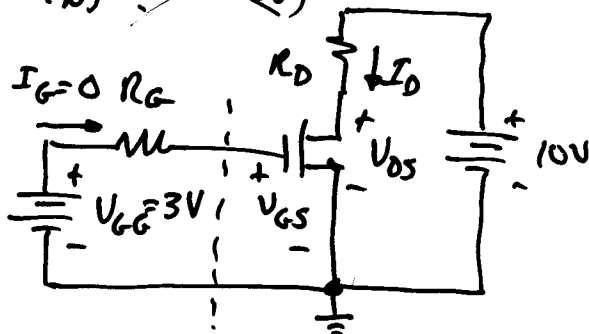The MOSFET is sat. if  $V_{DS} \geq V_{GS} - V_T \rightarrow 5\text{V} \geq 2$  Yes




$$\therefore V_{GS} = 3\text{V} \rightarrow I_D = \frac{25 \mu\text{A}}{2} \text{V}^2 (3-1)^2$$

$$I_D = 500 \mu\text{A}$$


MOSFET Example 2

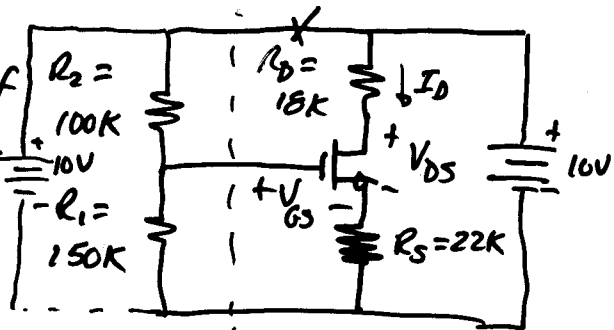Using the parameters of Ex. 1, find the Q point.



Solution

Simplify by Thev. concept -

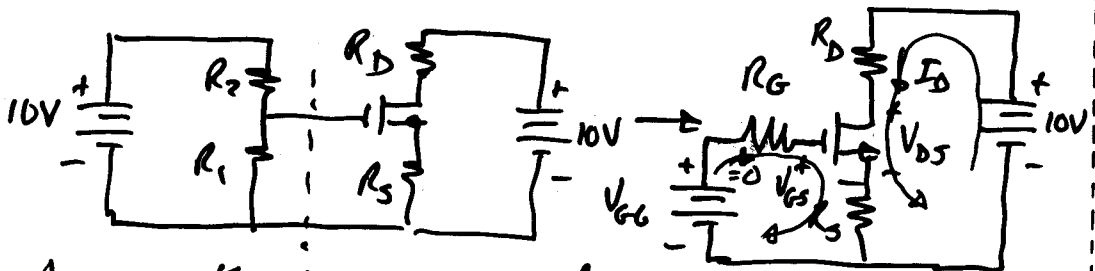

Assume the MOSFET is saturated -

GS-loop:


$$V_{GG} = V_{GS} + I_D R_S \quad \& \quad I_D = \frac{k_n'}{2} \frac{W}{L} (V_{GS} - V_{TN})^2$$

$$V_{GG} = V_{GS} + \frac{k_n' R_S W}{2 L} (V_{GS} - V_{TN})^2$$

Quadratic:  $V_{GS}^2 - 1.636 V_{GS} - 1.182 = 0$

$$V_{GS} = 0.8182 \pm 1.361 = \underline{\underline{2.179V}}$$

Graphical viewpoint -

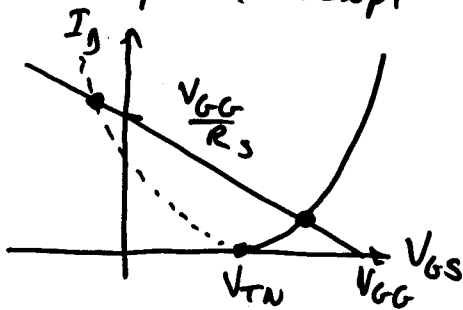

$$I_D = \frac{250}{2} (2.179 - 1)^2 = \underline{\underline{174 \mu A}}$$


$$V_{DS} = 10V - I_D (R_D + R_S) = 10V - 0.174(40K)$$

$$V_{DS} = 10 - 6.96 = \underline{\underline{3.04V}}$$

$$V_{GS} - V_T = 2.179V - 1 = 1.179V$$

∴ MOSFET is sat.

MOSFET Capacitances

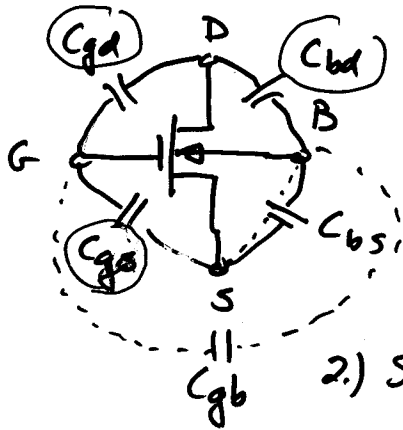

Assume  $V_{DS} = 0$  and  $C_{gb} \approx 0$

1.) Active, linear, triode, ohmic  
 $N_{DS} < N_{GS} - V_{TN}$


$$C_{gs} = C_{ox}W + \frac{1}{2}C_{ox}WL = C_{gd}, C_{bd}$$

2.) Saturation  $N_{DS} > N_{GS} - V_{TN}$

$$C_{gs} = C_{ox}W + \frac{2}{3}C_{ox}WL, C_{gd} = C_{ox}W, C_{bd}$$

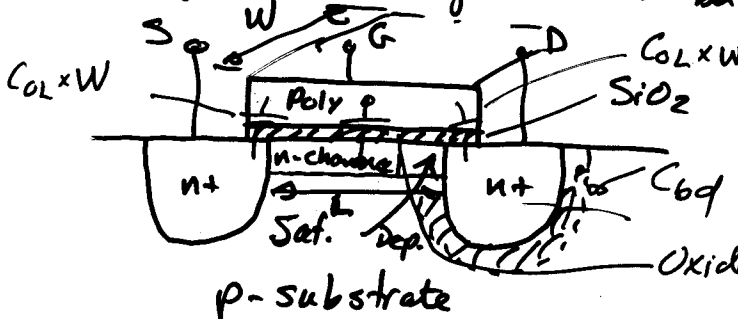3.) Cutoff  $N_{GS} < V_T$


$$C_{gs} = C_{ox}W, C_{gd} = C_{ox}W, C_{bd}, C_{gb} = C_{ox}WL$$



$$C_{ox} = \frac{\epsilon}{A \cdot \text{area}^2} = 1 \text{ fF}/\mu\text{m}^2$$

$$C_{bd} = \frac{C_{bdo}}{\sqrt{1 - \frac{N_{bd}}{\Phi_B}}}$$

Bipolar Junction Transistor

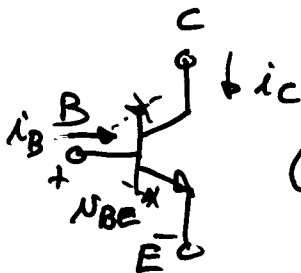

Regions of operation -


Region	BE	BC
Forward active	Fwd.	Rev.
Saturation	Fwd	Fwd
Reverse active	Rev.	Fwd.
Cutoff	Rev.	Rev.

Models -


Equations - Forward active region.

$$\left. \begin{aligned} i_C &= \beta_F i_B \\ i_B &= \frac{I_S}{\beta_F} \left( \exp \frac{V_{BE}}{nV_T} \right) \end{aligned} \right\} i_C = I_S \exp \left( \frac{V_{BE}}{nV_T} \right)$$

Schematic -

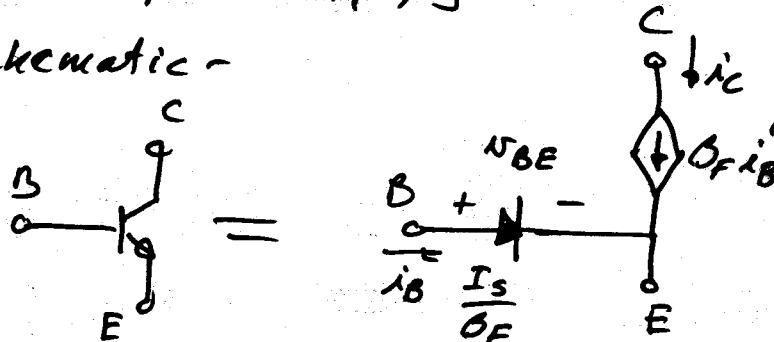


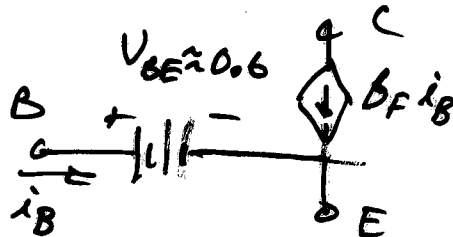If  $i_B$  is mostly determined externally, then



BJT Example 1

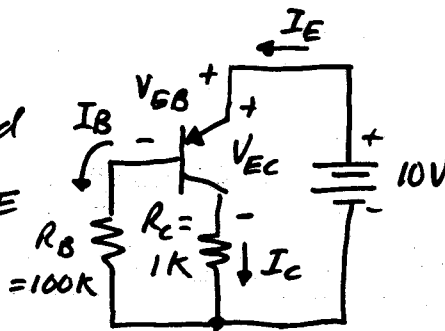If  $\beta_F = 50$ , find  $I_C$ ,  $V_{EC}$ ,  $V_{EB}$ ,  $I_E$  and  $I_B$



Voltage loop:  $10V = V_{EB} + I_B R_B \rightarrow I_B = \frac{10V - V_{EB}}{R_B}$

Since we know that  $10V \gg V_{EB}$  we can use the model where  $V_{EB} \approx 0.7V$ .

$\therefore I_B = \frac{10 - 0.7}{100k} = \underline{93\mu A}$       $I_C = \beta_F I_B = \underline{4.65mA}$

$I_E = I_B + I_C = \underline{4.74mA}$  ,  $V_{EB} \approx 0.7V$  ,  $V_C = I_C R_C = 4.65V$   
 $V_{EC} = V_E - V_C = \underline{5.35V}$

BJT Example 2


Find the quiescent point  
if  $\beta_F = 100$  and  $V_{BEQ} = 0.65V$ .

Solution

$$1.) V_{TH} = V_{BB} = 15V \frac{146}{315+146} = 4.72V$$

$$2.) R_{TH} = R_B = 315K // 146K = 100K$$

∴ The circuit can be  
rewritten as,

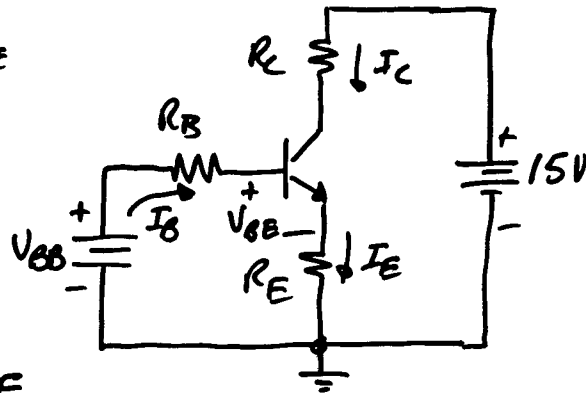

3.) Loop eq. around BE

$$V_{BB} = I_B R_B + V_{BE} + I_E R_E = V_{BE} + I_B R_B + (1 + \beta_F) I_B R_E$$

$$\therefore I_B = \frac{V_{BB} - V_{BE}}{R_B + (1 + \beta_F) R_E} = \frac{4.72 - 0.65}{100K + (101)1K} = \underline{\underline{20\mu A}}$$

$$4.) I_C = 100 I_B = \underline{\underline{2mA}}$$

$$5.) I_E = I_C + I_B = \underline{\underline{2.02mA}}$$

$$6.) V_{CE} = 15V - I_C R_C - I_E R_E = 15 - (2)(4) - (2.02)(1)$$

$$\underline{\underline{V_{CE} = 4.88V}}$$