

Homework Assign. 1 due in class today or by 4pm
 (turn homework after 12noon to Marge Boehme, VL E278)
 TA office hours - Nola Li <gttg019w@mail.gatech.edu>
 Monday 10-11 and Thursday 9-11, Room C448 VL


Amplifiers

- Linearity
- Linear amplifier
- decibels
- power flow
- Voltage transfer curve
- Distortion

CHAPTER 10 - ANALOG SYSTEMS

(A systems viewpoint of an amplifier)

I) Linearity

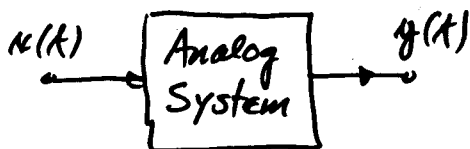

Analog is the study of signals which are continuous in amplitude and may or may not be continuous in time.

A system is linear iff


$$x_1(t) \rightarrow y_1(t)$$

$$x_2(t) \rightarrow y_2(t)$$


and

$$x_1(t) + x_2(t) \rightarrow y_1(t) + y_2(t)$$

for all $x(t)$.

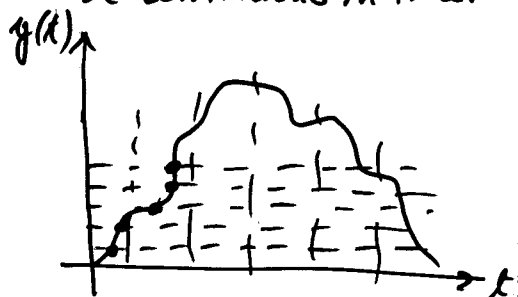

II. Linear Amplifier

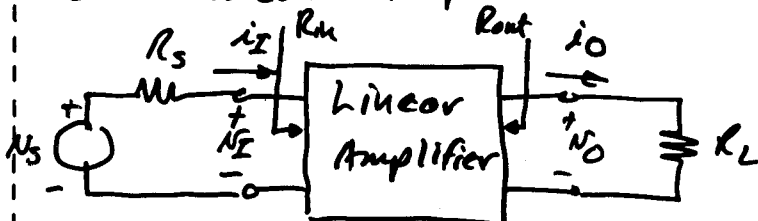

1.) Voltage gain



$$A_N = \frac{v_o}{v_i} \quad (R_s = 0) \quad \text{unloaded}$$

$$A_V = A_N \frac{R_{in}}{R_{in} + R_s} \quad (\text{loaded amplifier}) \quad R_{out} \ll R_L$$

2.) Current gain

$$A_I = \frac{i_o}{i_I} = \frac{N_o/R_L}{\frac{N_s}{R_{in} + R_s}} = \left(\frac{R_{in} + R_s}{R_L} \right) A_V$$

3.) R_{in} and R_{out}

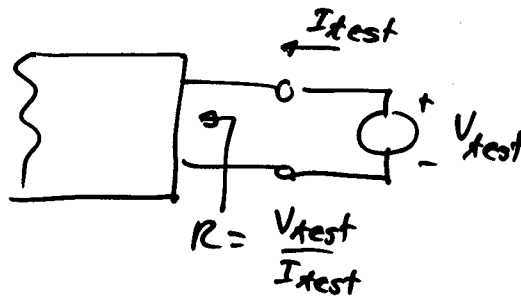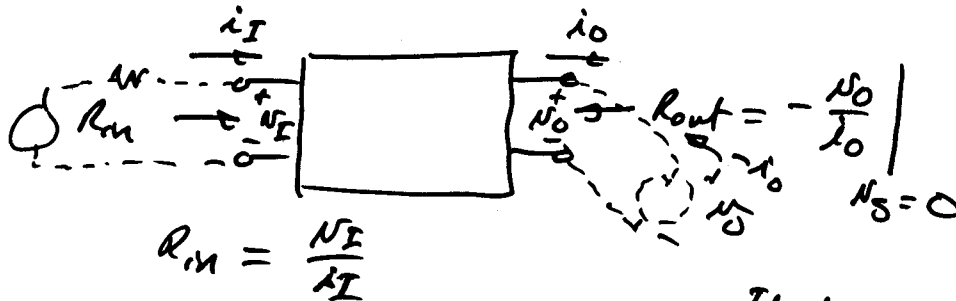

4.) Power gain

$$A_p = A_V A_I$$

III Decibels

Definitions:

$$\left. \begin{array}{l} \text{If } R_s = R_L \\ \text{Then } A_p = A_V^2 = A_I^2 \end{array} \right\} \begin{array}{l} A_p(\text{dB}) \equiv 10 \log_{10}(A_p) \\ A_V(\text{dB}) \equiv 20 \log_{10}(A_V) \\ A_I(\text{dB}) \equiv 20 \log_{10}(A_I) \end{array}$$


For A doubling in $A_p \Rightarrow 3 \text{ dB increase}$

A " " " $A_V(A_I) \Rightarrow 6 \text{ dB increase}$

A decade increase in $A_p \Rightarrow 10 \text{ dB increase}$

A " " " " $A_V(A_I) \Rightarrow 20 \text{ dB increase}$

IV. Power flow in amplifiers

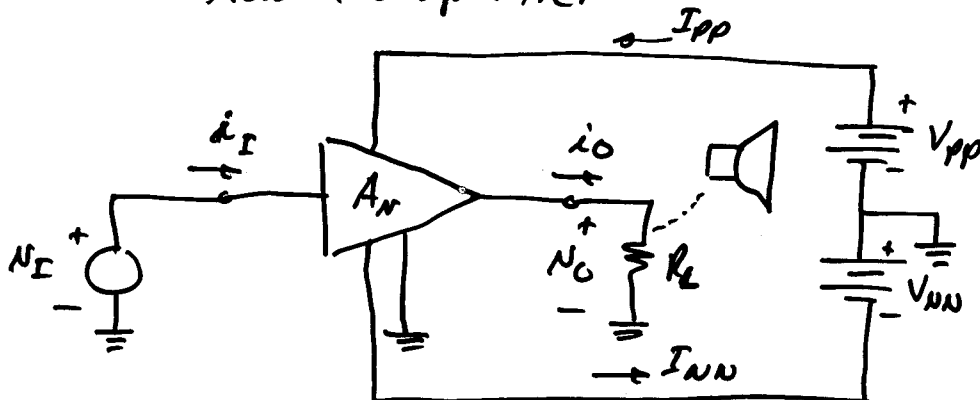

What power exists in this circuit?

- 1.) DC power is the power delivered from the batteries to the amplifier.

$$P_{DC} = V_{PP} I_{PP} + V_{NN} I_{NN}$$

- 2.) Input power from N_I or the source

$$P_{IN} = N_I i_I \text{ (typically small)}$$

- 3.) Power to the load R_L

$$P_{out} = i_O N_O = \frac{N_O^2}{R_L} = i_O^2 R_L$$

- 4.) Power loss in the amplifier

$$P_{DISS}$$

Power conservation:

$$P_{DC} + P_{IN} = P_{out} + P_{DISS}$$

Efficiency:


$$M = \frac{P_{out}}{P_{DC} + P_{IN}} \approx \frac{P_{out}}{P_{DC}} \quad (P_{IN} \ll P_{DC})$$

$0\% M < 100\%$ → Depends on signal level

Typically $M \propto$ signal level

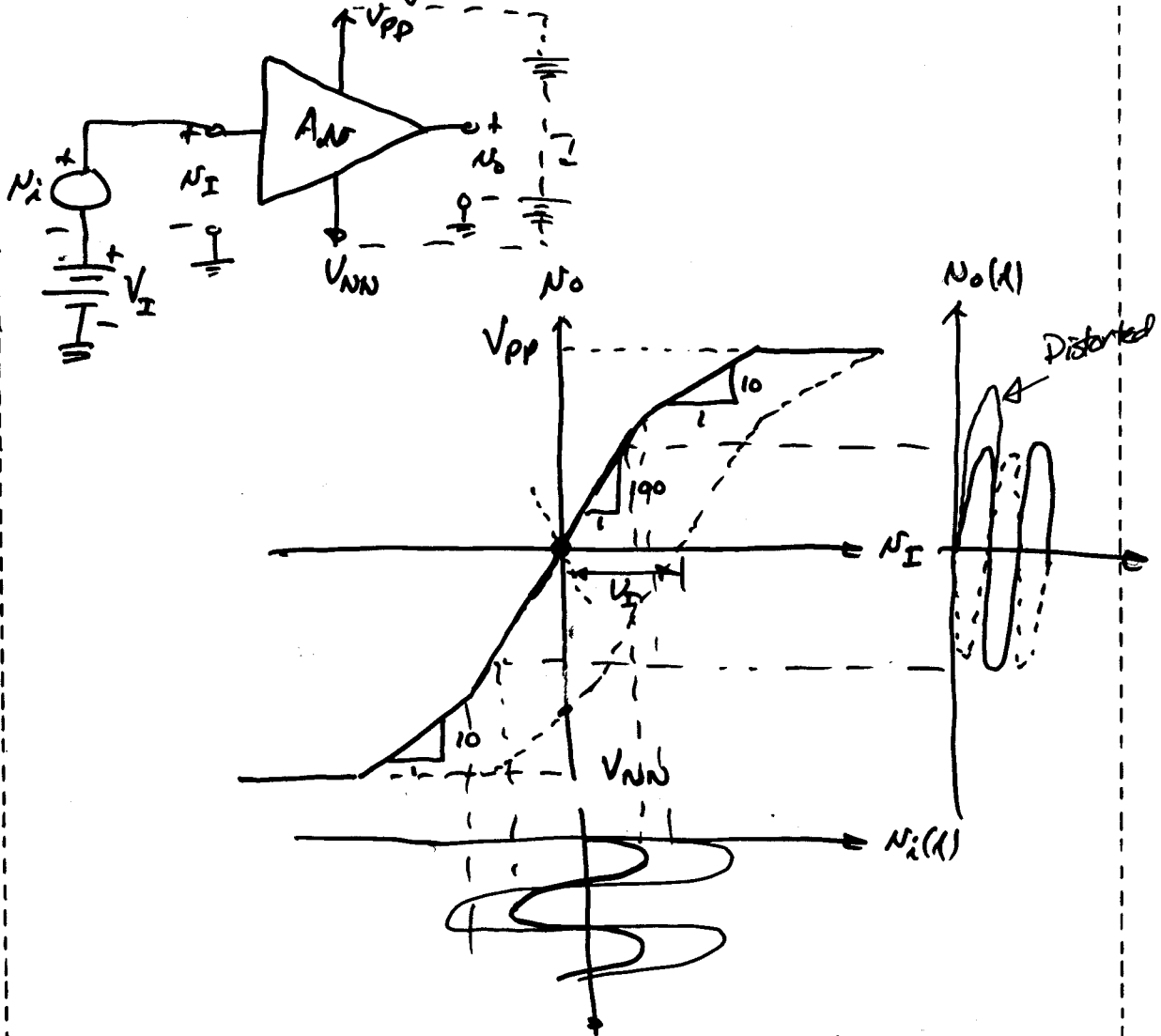II. Voltage Transfer Curve

Output voltage vs. input voltage of an amplifier



Small signal gain = Slope of VTC

$$= \left. \frac{\partial N_o}{\partial N_i} \right|_Q$$

Distortion -

Apply a pure sinusoidal voltage at input of freq = ω . Look for the harmonics at the output

$$N_{out} = a_1 \sin \omega t + a_2 \sin 2\omega t + a_3 \sin 3\omega t + \dots$$

$$THD = \frac{1}{a_1} \sqrt{a_2^2 + a_3^2 + a_4^2 + \dots}$$