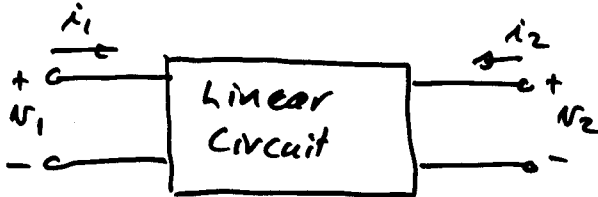


Today's Lecture

- Two-port parameters (10.5)
- Amplifiers (10.6)
- Frequency response (10.7)

Quiz #1 on Friday
Aug. 27, 2004
9 - 9:25am

Dr. Susanta Sengupta - 8/27

Two Port Parameters (10.5)

$$y_1 = f_1(x_1, x_2)$$

$$y_2 = f_2(x_1, x_2)$$

1.) y -parameters

$$i_1 = y_{11} V_1 + y_{12} V_2$$

$$V_2 = y_{21} V_1 + y_{22} V_2$$

$$y_{11} = \left. \frac{i_1}{V_1} \right|_{V_2=0}$$

$$y_{21} = \left. \frac{V_2}{V_1} \right|_{V_2=0}$$

$$y_{12} = \left. \frac{i_1}{V_2} \right|_{V_1=0}$$

$$y_{22} = \left. \frac{V_2}{V_2} \right|_{V_1=0}$$

2.) h -parameters

$$V_1 = h_{11} i_1 + h_{12} V_2$$

$$i_2 = h_{21} i_1 + h_{22} V_2$$

$$h_{11} = \left. \frac{V_1}{i_1} \right|_{V_2=0}$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{i_1=0}$$

$$h_{21} = \left. \frac{i_2}{i_1} \right|_{V_2=0}$$

$$h_{22} = \left. \frac{i_2}{V_2} \right|_{i_1=0}$$

3.) y -parameters

$$i_1 = y_{11} V_1 + y_{12} V_2$$

$$i_2 = y_{21} V_1 + y_{22} V_2$$



4.) z -parameters

$$V_1 = z_{11} i_1 + z_{12} i_2$$

$$V_2 = z_{21} i_1 + z_{22} i_2$$

Example

Voltage amplifier:

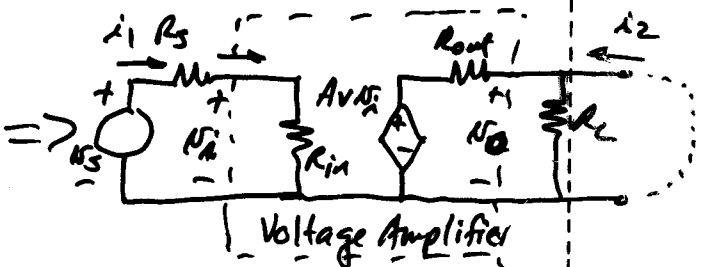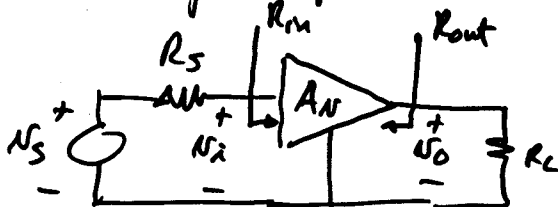


Example - Cont'd

$$N_0 = A_v N_i \frac{R_L}{R_{out} + R_L} = A_v \left(\frac{R_L}{R_{out} + R_L} \right) \left(\frac{R_{in}}{R_{in} + R_s} \right) N_s$$

$$\frac{N_0}{N_s} = A_v = \frac{R_L R_{in} A_v}{(R_{out} + R_L)(R_{in} + R_s)} = g_{v1}$$

Find the g-parameters if $N_i = N_s$ & $N_0 = N_2$

$$g_{11} = \left. \frac{i_1}{N_1} \right|_{i_2=0} = \frac{\text{Response}}{\text{Excitation}} \Bigg|_{\text{Condition}}$$

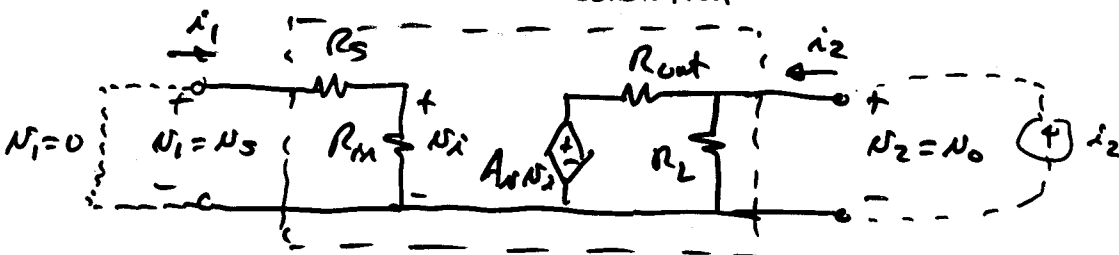

$$g_{11} = \left. \frac{i_1}{N_1} \right|_{i_2=0} = \frac{1}{R_s + R_m}$$

$$g_{21} = \left. \frac{N_2}{N_1} \right|_{i_2=0} = \frac{A_v R_L R_m}{(R_{out} + R_L)(R_s + R_{in})}$$

$$g_{12} = \left. \frac{i_1}{i_2} \right|_{N_1=0} = 0$$

$$g_{22} = \left. \frac{N_2}{i_2} \right|_{N_1=0 \rightarrow N_i=0} = R_L \parallel R_{out}$$


The 2-port parameters are useful for taking a more complicated ckt. and simplifying.



The schematic model for the 2-port parameters


$$i_1 = g_{11} N_1 + g_{12} i_2$$

$$N_2 = g_{21} N_1 + g_{22} i_2$$

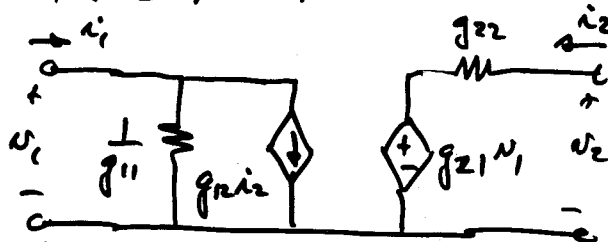

Amplifiers

	Type of Amplifier			
	Current	Transconductance	Trans-resistance	Voltage
Input variable	I	V	I	V
Output variable	I	I	V	V

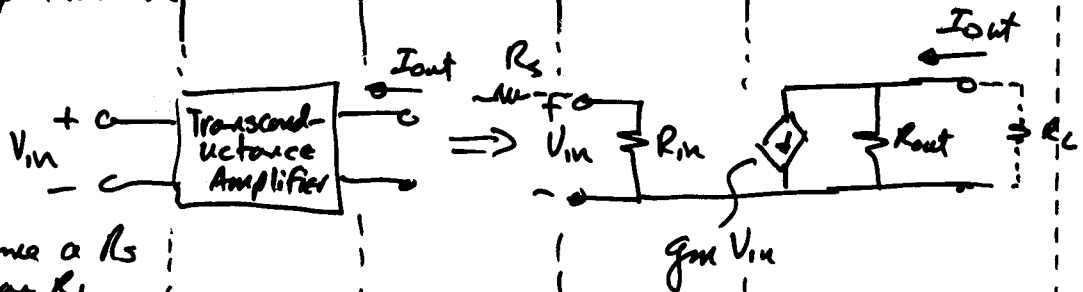

Ideal cond. at input

$R_{in} \ll R_s$

$R_{in} \gg R_s$

$R_{in} \ll R_s$

$R_{in} \gg R_s$

Ideal condition at the output


$R_{out} \gg R_L$

$R_{out} \gg R_L$


$R_{out} \ll R_L$

$R_{out} \ll R_L$


Current Amplifier

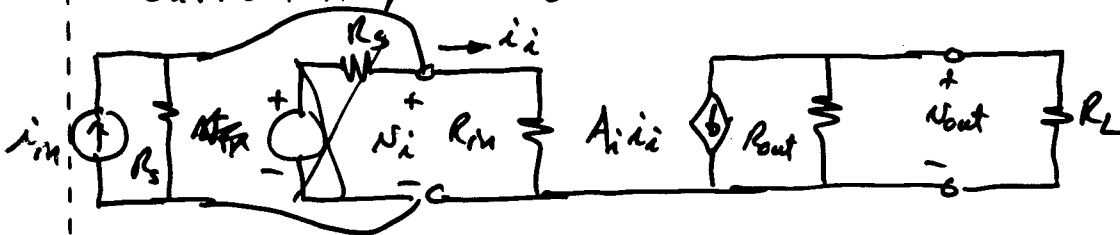

Frequency Response

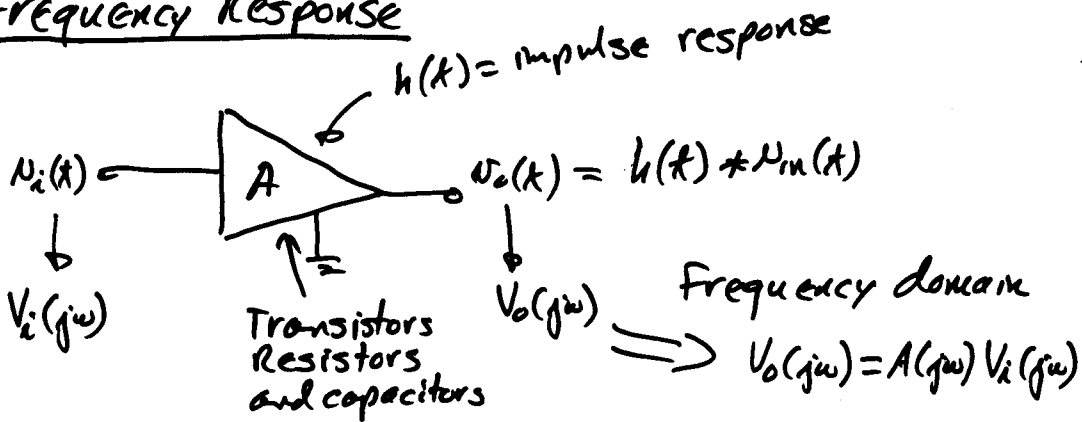

Frequency Domain Analysis of Amplifiers

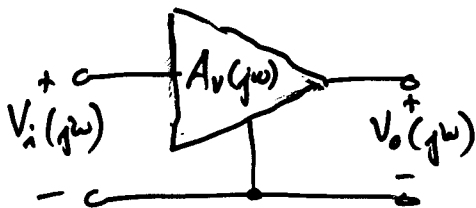

$A_v(j\omega) \leftrightarrow A_v(s)$

$s = \text{Complex freq. variable}$

$s = \sigma + j\omega$

Typically the amplifier can be described in the s-domain as,

$$A_v(s) = \frac{a_n s^n + \dots + a_1 s + a_0}{b_n s^n + \dots + b_1 s + b_0} \quad \text{where } n \geq m$$

$$= K \frac{(s+z_1)(s+z_2)\dots(s+z_m)}{(s+p_1)(s+p_2)\dots(s+p_n)}$$

Zeros: Values of s where $A_v(s) = 0$, i.e., $s = -z_1, -z_2, \dots$


Poles: " " " " $A_v(s) = \infty$, i.e., $s = -p_1, -p_2, \dots$

$$A_v(s) = \frac{100s(s+1)}{(s+10)(s+100)}$$

zeros at $s=0$ and $s=-1$

poles at $s=-10$ and $s=-100$

Complex frequency plane

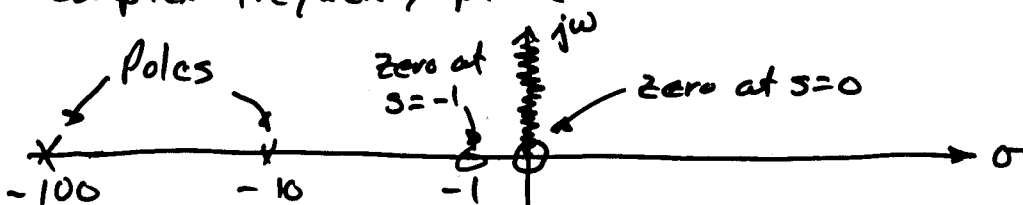

Approach to freq. response -

1.) Find $A(s)$

2.) $s \rightarrow j\omega \rightarrow A(j\omega)$

3.) Find \angle plot $|A(j\omega)|$

4.) Find ϕ plot $\text{Arg}[A(j\omega)]$

$20 \log_{10} |A(j\omega)|$ } -3dB bandwidth