

Quiz Solution on web site (Great average 9.1/10)

Quiz 2 on Friday, Sept. 3, 2004

I. Bandpass frequency response

II. Intro to op amps

III. Op amp circuits

I. Bandpass Frequency Response

$$A_V(s) = \frac{A_0 s \omega_H}{(s + \omega_L)(s + \omega_H)} \quad \omega_H \gg \omega_L$$

$$\lim_{s \rightarrow 0} A_V(s) = 0$$

$$\lim_{s \rightarrow \infty} A_V(s) = 0$$

$$s = j\omega \rightarrow A_V(j\omega) = \frac{A_0 j\omega \omega_H}{(j\omega + \omega_L)(j\omega + \omega_H)}$$

$$A_V(j\omega) = \frac{A_0 j \frac{\omega}{\omega_L}}{(1 + j \frac{\omega}{\omega_L})(1 + j \frac{\omega}{\omega_H})} \quad (1 + j\omega)$$

Make a Bode plot (asymptotic plot) of  $|A_V(j\omega)|$  and  $\text{Arg}[A_V(j\omega)]$ .

$$|A_V(j\omega)| = \frac{A_0 \left(\frac{\omega}{\omega_L}\right)}{\sqrt{1 + \left(\frac{\omega}{\omega_L}\right)^2} \sqrt{1 + \left(\frac{\omega}{\omega_H}\right)^2}}$$

$$\text{Arg}[A_V(j\omega)] = (\pm 180^\circ) + \tan^{-1}(\infty) - \tan^{-1}\left(\frac{\omega}{\omega_L}\right) - \tan^{-1}\left(\frac{\omega}{\omega_H}\right)$$


Mixes preceding the transfer funct.

Aside:

$$|A| = \frac{1}{\sqrt{1+x^2}}$$

$$x = \frac{\omega}{\omega_L}$$

$$\pm \tan^{-1}(x)$$

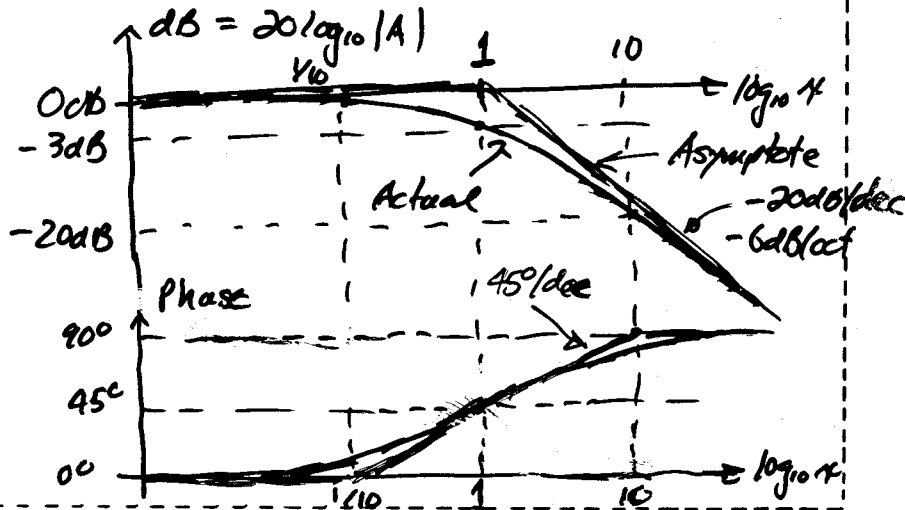


Continuing -

$$A_v(j\omega) = \frac{jA_0 \left(\frac{\omega}{\omega_L}\right)}{(1 + j\frac{\omega}{\omega_L})(1 + j\frac{\omega}{\omega_H})}$$

$$|A_v(j\omega)| = \frac{A_0 \frac{\omega}{\omega_L}}{\sqrt{1 + \left(\frac{\omega}{\omega_L}\right)^2} \sqrt{1 + \left(\frac{\omega}{\omega_H}\right)^2}}$$

$$20 \log_{10} |A_v(j\omega)| = \cancel{\pm 180^\circ} + 20 \log_{10}(A_0) + 20 \log_{10}\left(\frac{\omega}{\omega_L}\right)$$

$$|A_v(j\omega)|_{dB} = -20 \log_{10} \sqrt{1 + \left(\frac{\omega}{\omega_L}\right)^2} - 20 \log_{10} \sqrt{1 + \left(\frac{\omega}{\omega_H}\right)^2}$$

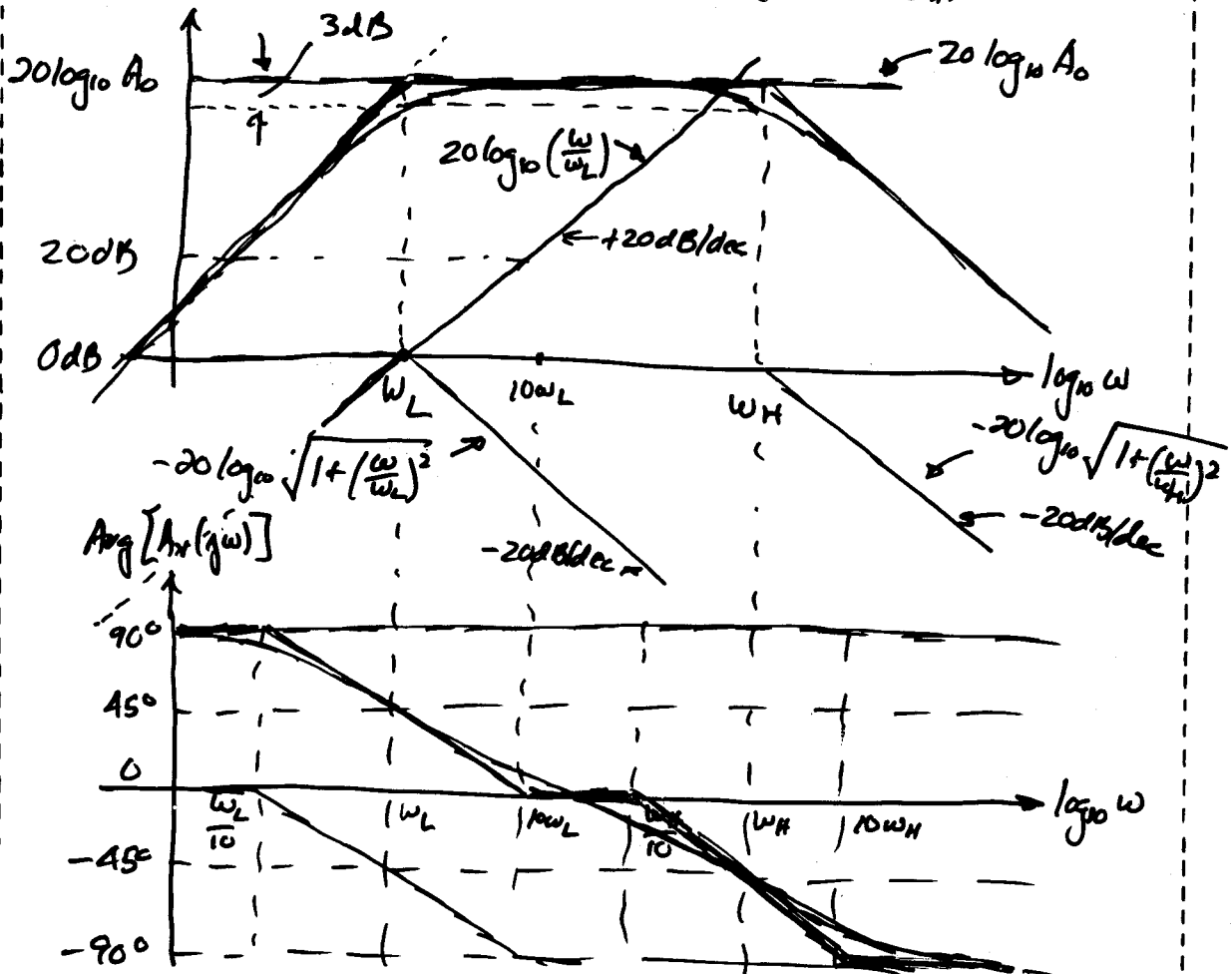


$$\text{Arg}[A_v(j\omega)] = \cancel{\pm 180^\circ} + 90^\circ - \tan^{-1}\left(\frac{\omega}{\omega_L}\right) - \tan^{-1}\left(\frac{\omega}{\omega_H}\right)$$

Work as many Bode plot probs as you can.

## II. Op Amps


### 1.) Differential Amplifier

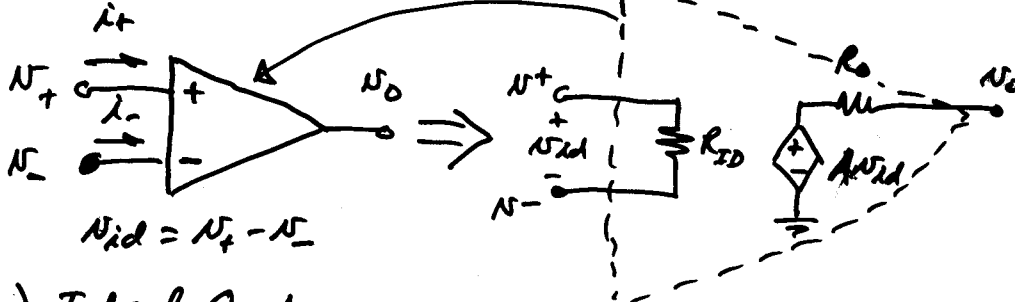

### 2.) Ideal Op Amp Requirements -


a.)  $A \rightarrow \infty$  ← KEY

b.)  $i_+ = i_- = 0$

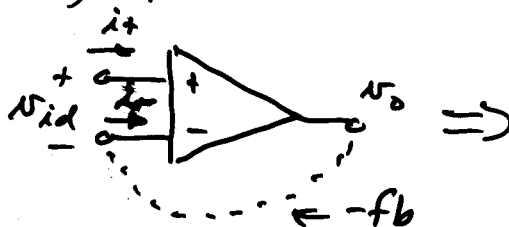

If  $A \rightarrow \infty$  and if there is some form of negative feedback, then  $V_{id} \approx 0$  and  $i_+ = i_- \approx 0$

### 3.) Inverting Amplifier

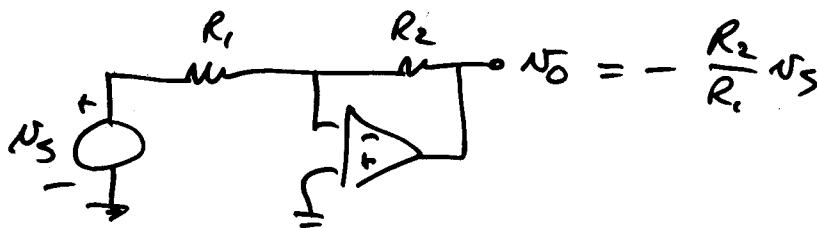

### 4.) Non inverting Amp.

