


Quiz 2 - Friday, Sept. 3

Topics: Two port parameters, s-domain analysis, Bode plots


IDEAL OP AMP CIRCUITS ($A_{vd} = A_o \rightarrow \infty$)

Nonideal aspects of an op amp

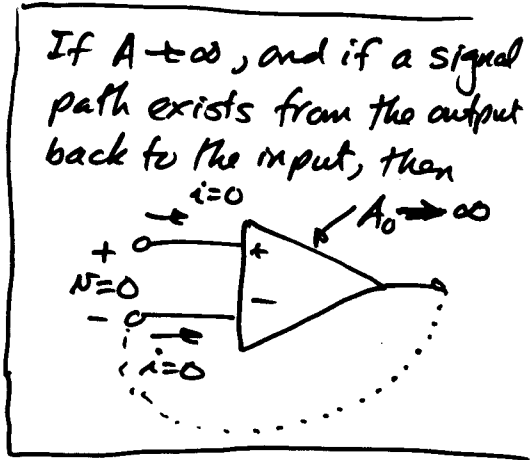- 1.) $A_v \neq \infty$
- 2.) $BW \neq \infty$
- 3.) $R_{id} \neq \infty$ and $R_o \neq 0$



1.) Inverting Amplifier

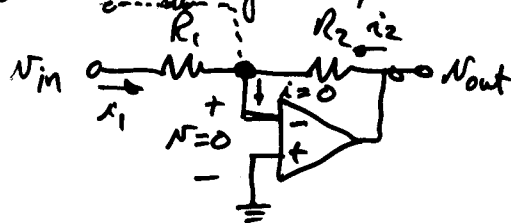


$$i_1 = \frac{N_{in} - N}{R_1} = \frac{N_{in} - 0}{R_1} = \frac{N_{in}}{R_1} \rightarrow R_{in} = \frac{N_i}{i_i} = R_1$$

$$i_2 = \frac{N_{out} - N}{R_2} = \frac{N_{out} - 0}{R_2} = \frac{N_{out}}{R_2}$$

$$i_1 + i_2 + i = 0 \rightarrow i_1 + i_2 + 0 = 0 \rightarrow i_1 = -i_2$$



$$\frac{N_{in}}{R_1} = -\frac{N_{out}}{R_2} \rightarrow \boxed{\frac{N_{out}}{N_{in}} = -\frac{R_2}{R_1} = -\frac{Z_2(s)}{Z_1(s)}}$$

2.) Noninverting Amplifier

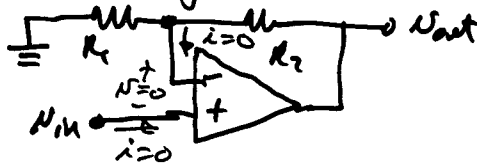


$$N = N_{in} - \frac{R_1}{R_1 + R_2} N_{out} = 0$$
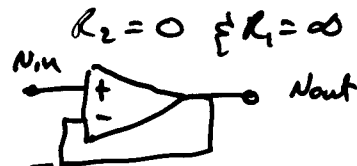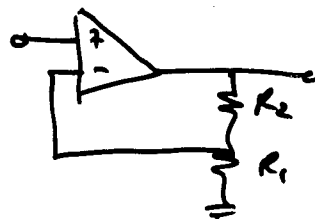
$$\boxed{\frac{N_{out}}{N_{in}} = \frac{R_1 + R_2}{R_1} = \frac{Z_1 + Z_2}{Z_1}}$$



"Buffer" \rightarrow $\frac{N_{out}}{N_{in}} = 1$

3.) Difference Amplifier

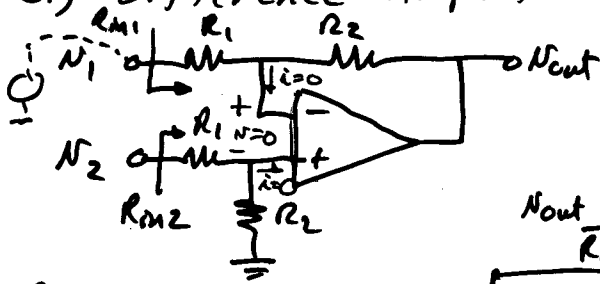


$$V = \left(N_{out} \frac{R_1}{R_1 + R_2} + \frac{R_2}{R_1 R_2} N_1 \right) - \frac{R_2}{R_1 R_2} N_2 = 0$$

$$N_{out} \frac{R_1}{R_1 + R_2} = \frac{R_2}{R_1 R_2} N_2 - \frac{R_2}{R_1 R_2} N_1$$


$R_{in1} = R_1$
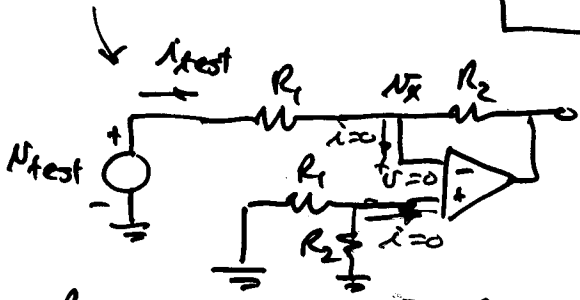
$$\therefore V_{out} = \frac{R_2}{R_1} (N_2 - N_1)$$



$$i_{test} = \frac{N_{test} - N_x}{R_1} = \frac{N_{test}}{R_1}$$

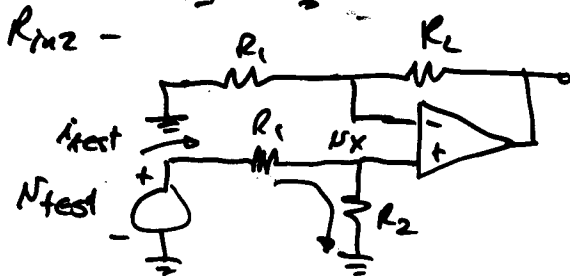
$$R_{in1} = \frac{N_{test}}{i_{test}} = R_1$$



$$N_{test} = i_{test} (R_1 + R_2)$$

$$\therefore R_{in2} = R_1 + R_2$$

4.) Instrumentation Amplifier

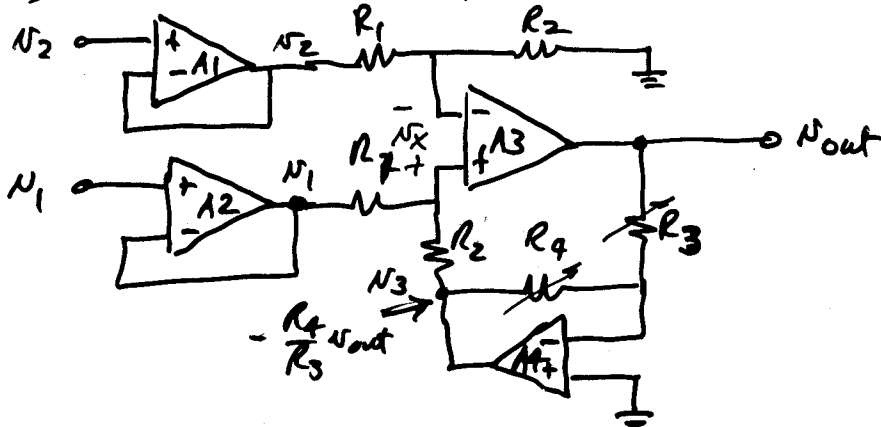

$$N_x = N_1 \frac{R_2}{R_1 + R_2} + N_3 \frac{R_1}{R_1 + R_2} - N_2 \frac{R_2}{R_1 + R_2} = 0$$


$$N_3 \frac{R_1}{R_1 + R_2} = \frac{R_2}{R_1 + R_2} N_2 - \frac{R_2}{R_1 + R_2} N_1 = \frac{R_2}{R_1 + R_2} (N_2 - N_1)$$

Cont'd


$$N_3 = \frac{R_2}{R_1} (N_2 - N_1) \rightarrow N_{out} = -\frac{R_4}{R_3} N_3 = -\frac{R_4}{R_3} \frac{R_2}{R_1} (N_2 - N_1)$$

$$N_{out} = + \frac{R_2 R_4}{R_1 R_3} (N_1 - N_2) = K(N_1 - N_2)$$

5) For you. Find R_{in} .

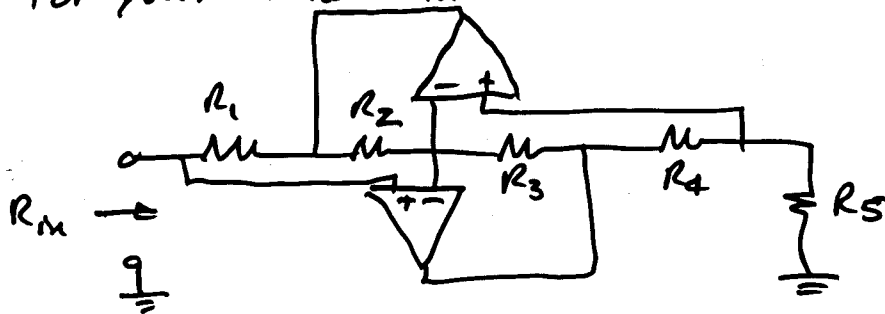


6.) Integrator DC problems

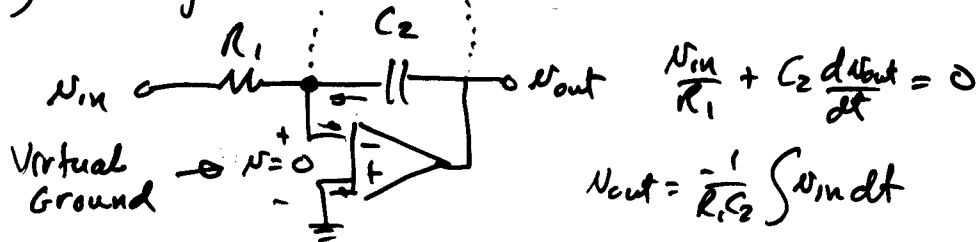

$$\frac{N_{in}}{R_1} + C_2 \frac{dV_{out}}{dt} = 0$$

$$V_{out} = -\frac{1}{R_1 C_2} \int N_{in} dt$$

7.) Low pass filter

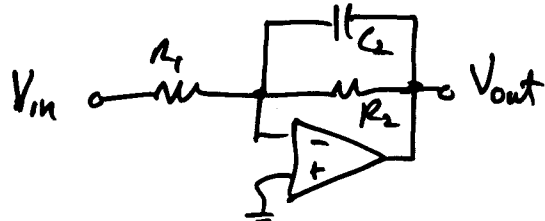

$$Z_2(s) = \frac{R_2 \frac{1}{sC_2}}{R_2 + \frac{1}{sC_2}} = \frac{R_2}{sR_2C_2 + 1}$$


$$Z_1(s) = R_1$$

$$\frac{V_{out}(s)}{V_{in}(s)} = -\frac{Z_2(s)}{Z_1(s)} = -\frac{R_2}{R_1} \left(\frac{1}{sR_2C_2 + 1} \right)$$

If $\omega_H = \frac{1}{R_2 C_2}$

then

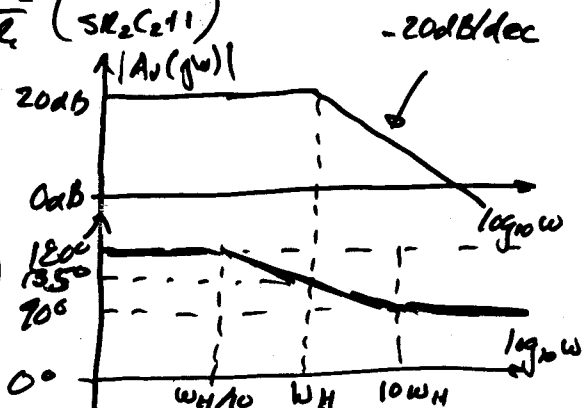
$$\frac{V_{out}(s)}{V_{in}(s)} = A_V(s) = -\frac{R_2}{R_1} \left(\frac{1}{\frac{s}{\omega_H} + 1} \right)$$



NONIDEAL OP AMPS

- 1.) $A_0 \neq \infty$
 - 2.) $BW \neq \infty$
- } 3050
- 3.) Resistances not ideal


Model for an op amp?

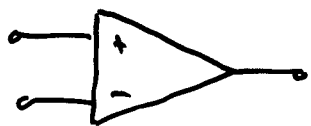

$A_v(s) = ?$

1.) $A_v(s) = A_0$

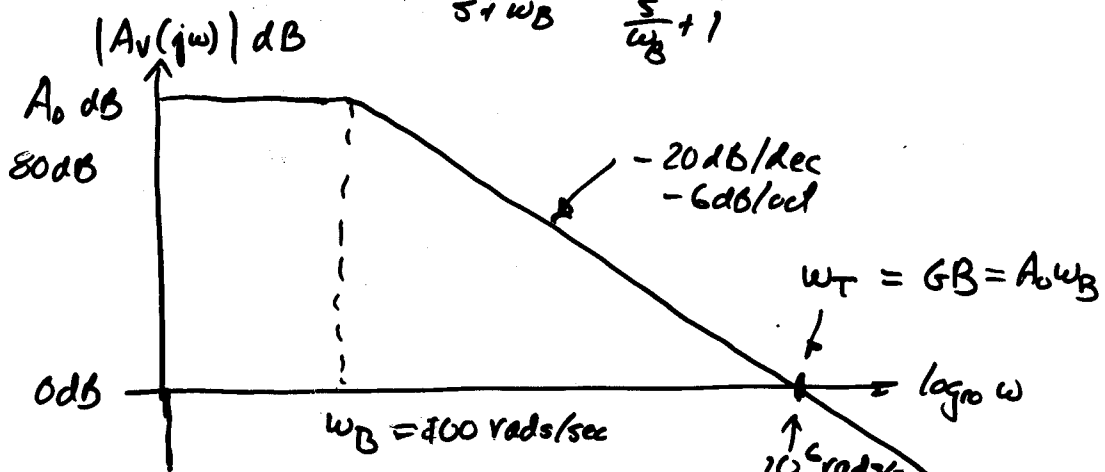2.) $A_v(s) = A_0 \frac{\omega_B}{s + \omega_B} = \frac{A_0}{\frac{s}{\omega_B} + 1}$



$\omega_T = GB =$ unity gain frequency (Gain-bandwidth)

- 1.) The noninverting amplifier when $A_v(s) = \frac{A_0}{\frac{s}{\omega_B} + 1}$
- (To be continued)