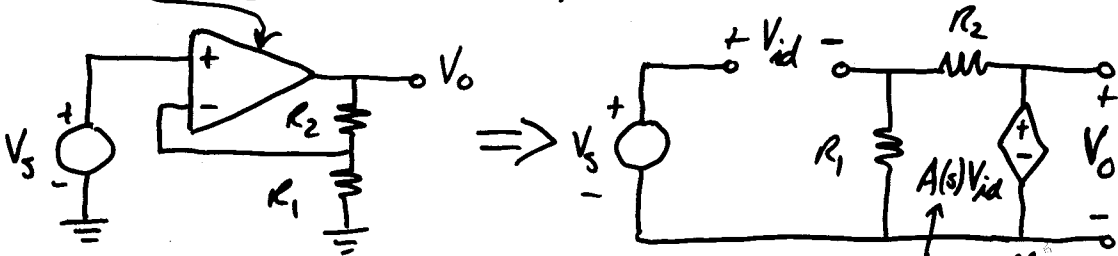



Frequency Response of the Non-Inverting Amplifier

$$A(s) = \frac{A_0}{\frac{s}{\omega_B} + 1} \leftarrow \text{op amp differential voltage gain}$$

$\frac{s}{\omega_B} + 1 \leftarrow A_0 \neq \infty \ \& \ \omega_B \neq \infty$



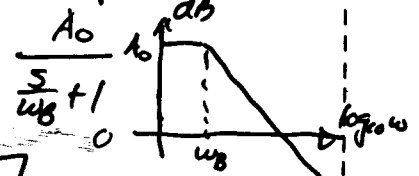Ideally $\frac{V_o}{V_s} = \frac{R_1 + R_2}{R_1}$




$$V_o(s) = A_v(s) V_{id} = A_v(s) \left[V_s - \frac{R_1}{R_1 + R_2} V_o \right]$$

$$V_o \left[1 + \frac{A_v(s) R_1}{R_1 + R_2} \right] = A_v(s) V_s \Rightarrow \frac{V_o(s)}{V_s(s)} = \frac{A_v(s)}{1 + \frac{A_v(s) R_1}{R_1 + R_2}}$$

$$A_v(s) = \frac{V_o(s)}{V_s(s)} = \frac{1}{\frac{1}{A_v(s)} + \frac{R_1}{R_1 + R_2}} = \frac{1}{\frac{s}{\omega_B} + 1 + \frac{R_1}{R_1 + R_2}} = \frac{A_0}{\frac{s}{\omega_B} + 1 + \frac{A_0 R_1}{R_1 + R_2}}$$

Let $\beta \equiv \frac{R_1}{R_1 + R_2}$ (feedback factor)
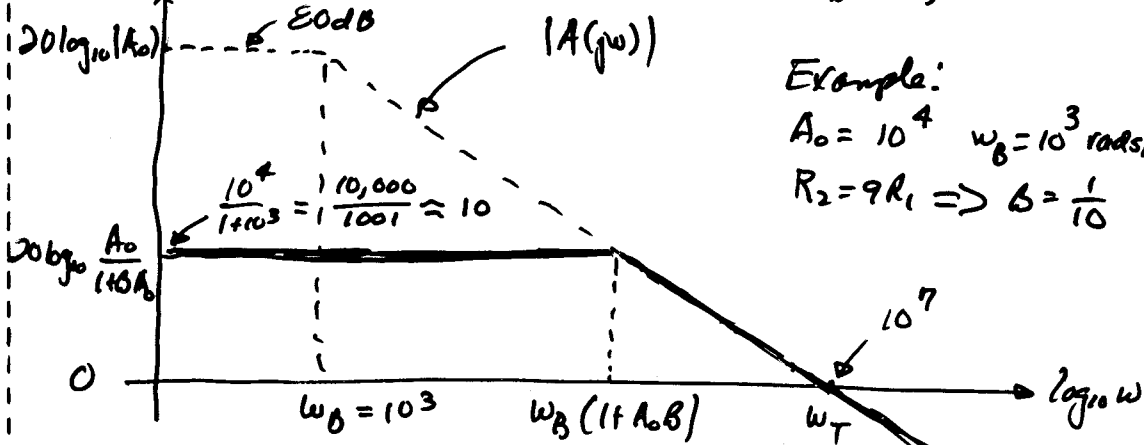
$$A_v(s) = \frac{A_0}{\frac{s}{\omega_B} + (1 + A_0 \beta)} = \left(\frac{A_0}{1 + A_0 \beta} \right) \left(\frac{1}{\frac{s}{\omega_B (1 + A_0 \beta)} + 1} \right)$$




Example:

$$A_0 = 10^4 \quad \omega_B = 10^3 \text{ rad/s}$$

$$R_2 = 9R_1 \Rightarrow \beta = \frac{1}{10}$$

INVERTING AMPLIFIER FREQUENCY RESPONSE

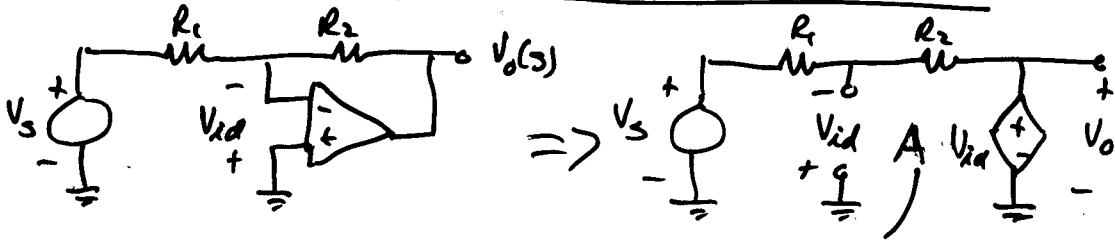


$$V_o = A V_{id} = -A \left[\frac{R_2}{R_1 + R_2} V_s + \frac{R_1}{R_1 + R_2} V_o \right] = -\frac{A R_2}{R_1 + R_2} V_s - \frac{A R_1}{R_1 + R_2} V_o$$

$$V_o (1 + AB) = -\frac{R_2}{R_1} AB V_s \quad \frac{V_o}{V_s} = \left(-\frac{R_2}{R_1}\right) \frac{AB}{1 + AB}$$

$$\frac{V_o(s)}{V_s(s)} = A_v(s) = -\left(\frac{R_2}{R_1}\right) \frac{B}{\frac{1}{A} + B}$$

Finally,

$$|A_v(j\omega)|_{dB} \quad A_v(s) = \left(-\frac{R_2}{R_1}\right) \left(\frac{A_0 B}{1 + A_0 B}\right) \left(\frac{1}{\frac{s}{\omega_B(1 + A_0 B)} + 1}\right)$$

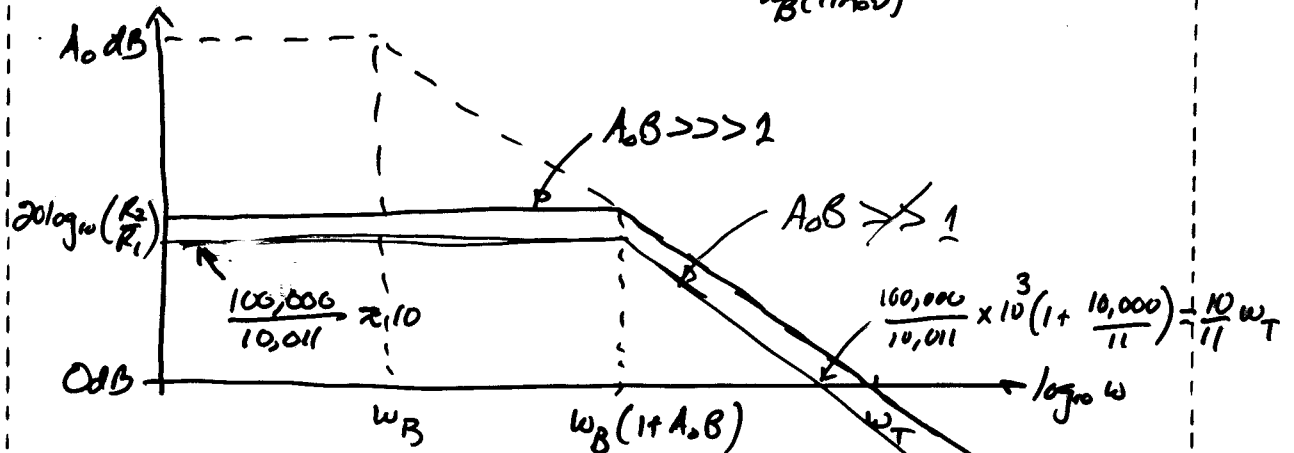

$$A_0 = 10^4, \omega_B = 10^3, R_2 = 10 R_1 \rightarrow B = \frac{1}{11}$$

$$\frac{A_0 B}{1 + A_0 B} = \frac{10^4 / 11}{1 + 10^4 / 11} = \frac{10^4}{11 + 10^4} = \frac{10,000}{10,011}$$