

Op Amp Frequency Response - Summary



$$\frac{V_{out}(s)}{V_{in}(s)} = A_v(s) = K \left(\frac{1}{\frac{s}{\omega_B(1+A_0B)} + 1} \right); \quad K = \frac{A_0}{1+A_0B} \text{ for NInv.}$$

$$K = \left(-\frac{R_2}{R_1} \right) \frac{A_0}{1+A_0B} \text{ for Inv.}$$

$\omega_H \leftarrow -3\text{dB frequency}$

Example

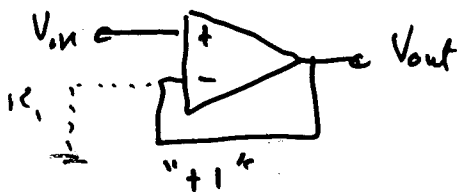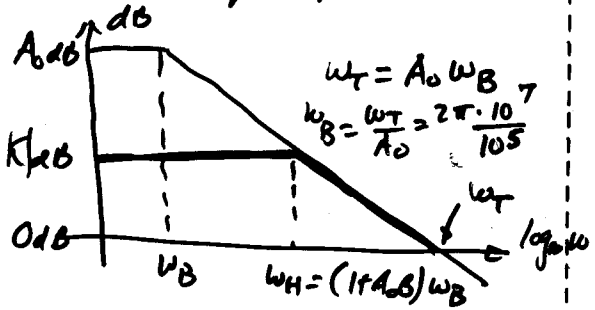
1.) An op amp with $A_0 = 100000$, $f_T = 10\text{MHz}$ is used to build a voltage amplifier having a gain of +1 and a gain of -1. Find ω_H .



$$B = \frac{R_1}{R_1 + R_2} = \frac{\infty}{\infty + 0} = \mathbf{1}$$

$$\therefore \omega_H = 200\pi (1 + 10^5 \cdot 1)$$
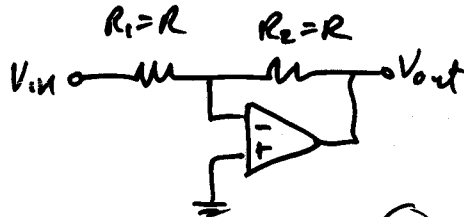
$$\approx 2\pi \times 10^7 \rightarrow \underline{\underline{10\text{MHz}}}$$



$$B = \frac{R_1}{R_1 + R_2} = \frac{R}{R + R} = \mathbf{\left(\frac{1}{2}\right)}$$

$$\omega_H = 200\pi (1 + 10^5 \cdot \frac{1}{2}) \approx \pi \times 10^7$$

$$\underline{\underline{f_H \approx 5\text{MHz}}}$$

2.) Repeat 1.) but let the amplifiers have a gain of ± 100

$$B = \frac{R_1}{R_1 + R_2} = \frac{R_1}{R_1 + 99R_1} = \mathbf{\left(\frac{1}{100}\right)}$$


$$\omega_H = 200\pi (1 + \frac{10^5}{10^2})$$

$$\approx 2\pi \times 10^5 \rightarrow \underline{\underline{100\text{kHz}}}$$

$$B = \frac{R_1}{R_1 + R_2} = \frac{R_1}{R_1 + 100R_1} = \mathbf{\left(\frac{1}{101}\right)}$$

$$\omega_H = 200\pi (1 + \frac{10^5}{101}) \approx \underline{\underline{99\text{kHz}}}$$

N-Cascade Amplifiers (Identical)


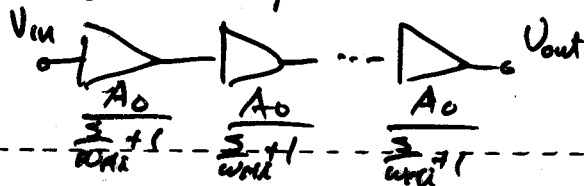


$$\frac{V_{out}}{V_{in}} = \left(\frac{A_0}{\frac{s}{\omega_{Hi}} + 1} \right)^n \quad \text{For } n=3$$

$$\omega_H = \omega_{Hi} \sqrt{2^{1/n} - 1} \quad \omega_H = 0.51\omega_{Hi}$$

CHAPTER 13 - TRANSISTOR AMPLIFIERS

1.) BJT Amplifier

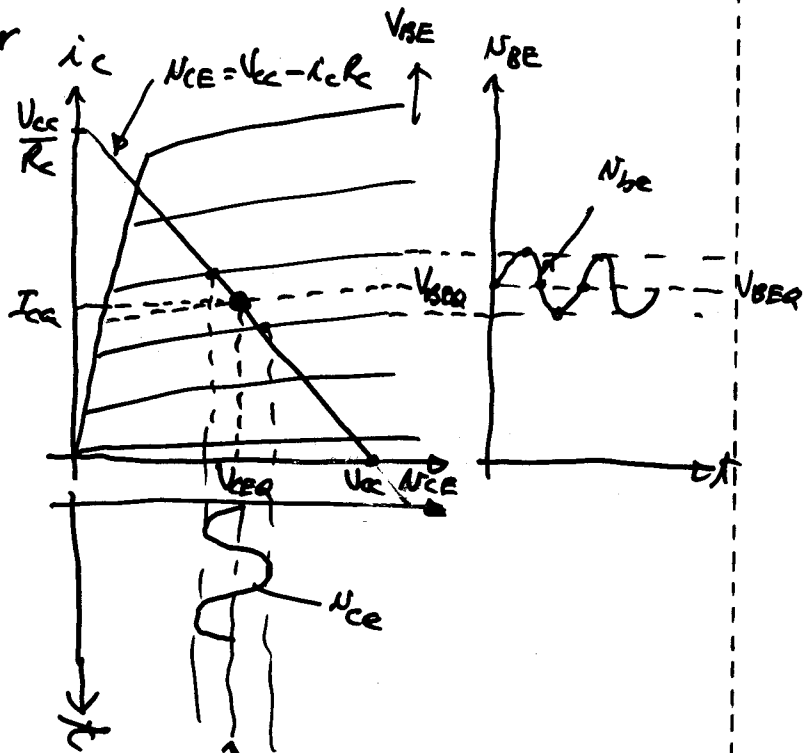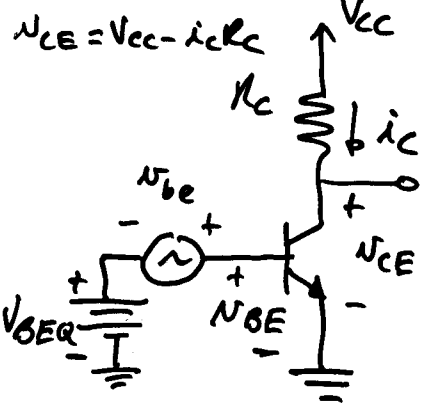

Mathematically -


$$N_{CE} = V_{CC} - I_C R_C = V_{CC} - R_C \left[I_S \exp\left(\frac{V_{BE}}{V_T}\right) \right]$$

$$\left. \frac{\partial N_{CE}}{\partial V_{BE}} \right|_Q = \text{gain} = -\frac{R_C I_S}{V_T} \exp\left(\frac{V_{BEQ}}{V_T}\right) = -\frac{R_C I_{CQ}}{V_T}$$

Suppose, $R_C = 10K$, $I_{CQ} = 1mA$ & $V_T = 25mV$

$$\left. \frac{\partial N_{CE}}{\partial V_{BE}} \right|_Q = \text{voltage gain} = -\frac{10^4 \cdot 10^{-3}}{25 \times 10^{-3}} = -\frac{10,000}{25} = \underline{\underline{-400V}}$$

2.) MOSFET Amplifiers

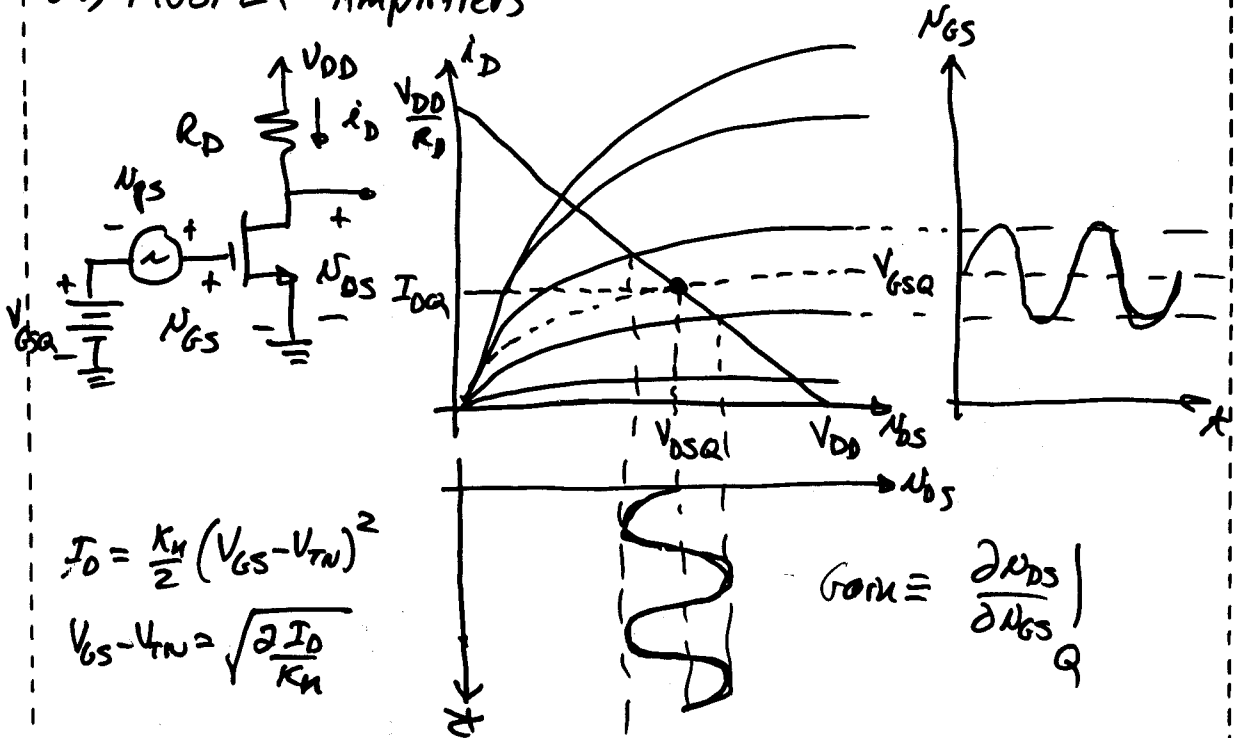

$$I_D = \frac{K_n}{2} (V_{GS} - V_{TN})^2$$

$$V_{GS} - V_{TN} = \sqrt{\frac{2I_D}{K_n}}$$

$$g_m = \left. \frac{\partial I_D}{\partial V_{GS}} \right|_Q$$

$$V_{DS} \approx V_{DD} - R_D \left[\frac{K_n}{2} (V_{GS} - V_{TN})^2 \right] \leftarrow \text{Assumes } V_{DS} > V_{GS} - V_{TN}$$

$$\left. \frac{\partial V_{DS}}{\partial V_{GS}} \right|_Q = -R_D K_n (V_{GS} - V_{TN}) = -R_D K_n \sqrt{\frac{2I_{DQ}}{K_n}} = -R_D \sqrt{K_n I_{DQ}^2}$$

Assume $K_n = 250 \frac{\mu A}{V^2}$, $I_D = 1 \text{ mA}$, and $R_D = 10 \text{ K}$

$$\text{Voltage gain} = \left. \frac{\partial V_{DS}}{\partial V_{GS}} \right|_Q = -10^4 \sqrt{250 \cdot 1000 \cdot 10^{-6}}$$


$$= \underline{\underline{-7.07 \frac{V}{V}}}$$

MOSFET gain \ll BJT gain

3) Coupling and Bypass Capacitors

How do you separate ac and dc signals?

Example -

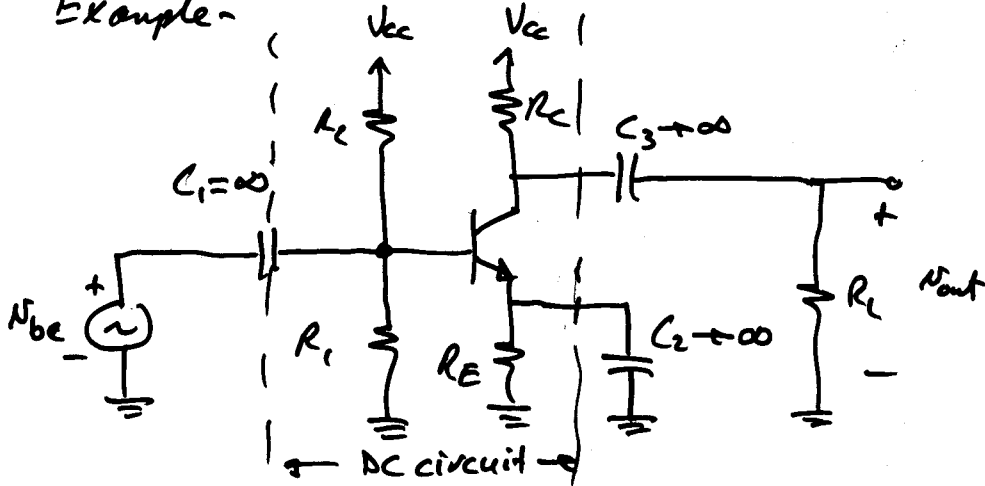

C_1 & C_3 are coupling capacitors

C_2 is a bypass capacitor

On p. 580 \rightarrow 586 (AC ckt. & DC ckt.)