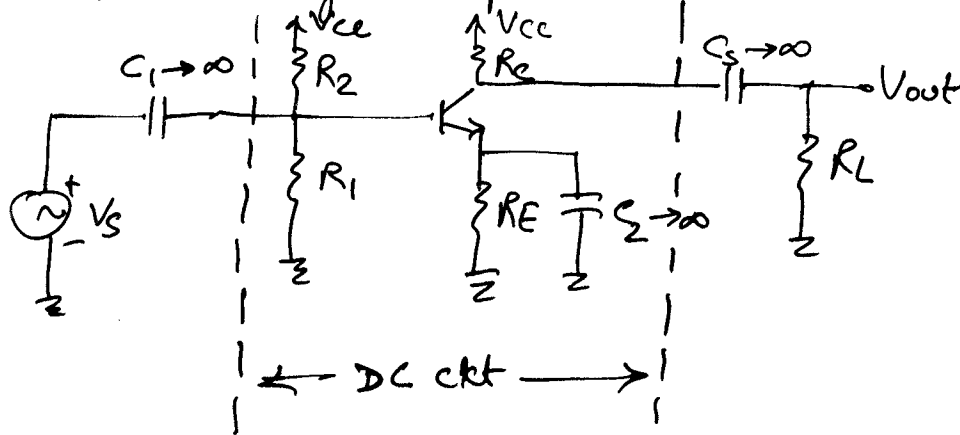



### 3) Coupling and Bypass Capacitors

How do you separate the ac and dc signals?




AC ckt.

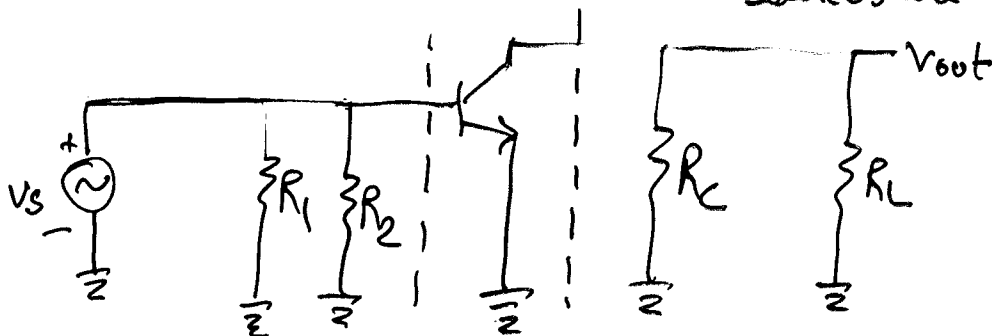1. All  $\infty$  caps are shorted
2. All dc voltages are shorted
3. All dc current sources are opened



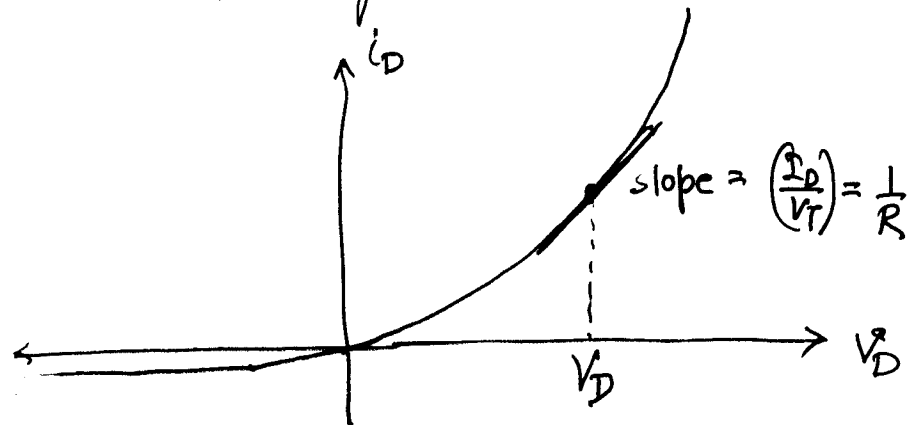4) Diode small-signal model  $\rightarrow$  ac model



Large signal:  $i_D = I_S \left[ \exp\left(\frac{v_D}{V_T}\right) - 1 \right]$

$$i_d + I_D \begin{matrix} \text{(ss)} & \text{(dc)} \end{matrix} = I_S \left[ \exp\left(\frac{v_d + v_D}{V_T}\right) - 1 \right]$$

$$= I_S \left[ \exp\left(\frac{v_d}{V_T}\right) \cdot \exp\left(\frac{v_D}{V_T}\right) - 1 \right]$$

When  $v_d \ll V_T$ , then  $\exp\left(\frac{v_d}{V_T}\right) \approx 1 + \frac{v_d}{V_T} + \frac{1}{2} \left(\frac{v_d}{V_T}\right)^2 + \dots$

$$i_d + I_D = I_S \left[ \exp\left(\frac{v_D}{V_T}\right) \left(1 + \frac{v_d}{V_T}\right) - 1 \right]$$


$$i_d + I_D = \underbrace{I_S \left[ \exp\left(\frac{v_D}{V_T}\right) - 1 \right]}_{I_D} + \left[ I_S \exp\left(\frac{v_D}{V_T}\right) \right] \left(\frac{v_d}{V_T}\right)$$

$$\text{SS} \rightarrow i_d = \left[ I_S \exp\left(\frac{v_D}{V_T}\right) \right] \left(\frac{v_d}{V_T}\right) \approx \left(\frac{I_D + I_S}{V_T}\right) v_d \approx \left(\frac{I_D}{V_T}\right) v_d$$

$$i_d \approx \left(\frac{I_D}{V_T}\right) v_d$$

Small-signal BJT model

CE BJT

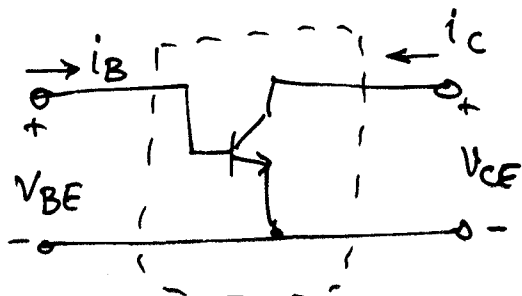

Forward active

- BE is forward biased

- CB is reversed biased

Large-signal

$$\begin{cases} i_c = I_s \left[ \exp\left(\frac{V_{BE}}{V_T}\right) \right] \left[ 1 + \frac{V_{CE}}{V_A} \right] \\ i_b = \frac{I_s}{\beta_F} \left[ \exp\left(\frac{V_{BE}}{V_T}\right) \right] \end{cases}$$

↓  
Linearize

$$i_c = K_1 V_{BE} + K_2 V_{CE}$$

$$i_b = K_3 V_{BE}$$

$$K_1 = \left. \frac{i_c}{V_{BE}} \right|_{V_{CE}=0} = \left. \frac{\partial i_c}{\partial V_{BE}} \right|_{V_{CE}=0} = \left( \frac{I_c}{V_T} \right) = g_m$$

$$K_2 = \left. \frac{i_c}{V_{CE}} \right|_{V_{BE}=0} = \left. \frac{\partial i_c}{\partial V_{CE}} \right|_{V_{BE}=0} = \frac{I_c}{(V_A + V_{CE})} \approx \frac{I_c}{V_A} \equiv g_o$$

$$K_3 = \left. \frac{i_b}{V_{BE}} \right|_0 = \left. \frac{\partial i_b}{\partial V_{BE}} \right|_0 = \frac{I_c}{\beta_F V_T} = g_{\pi} = \frac{1}{r_{\pi}}$$

$$i_c = g_m V_{BE} + g_o V_{CE}$$

$$i_b = g_{\pi} V_{BE}$$

