

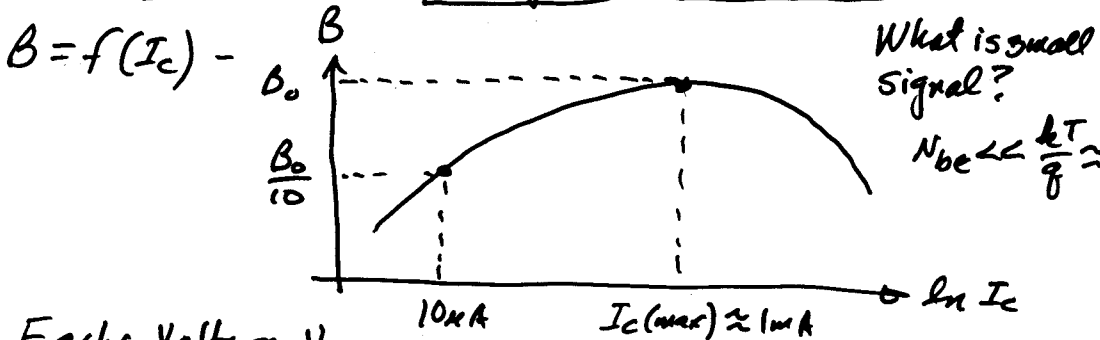


Small Signal Model for the BJT

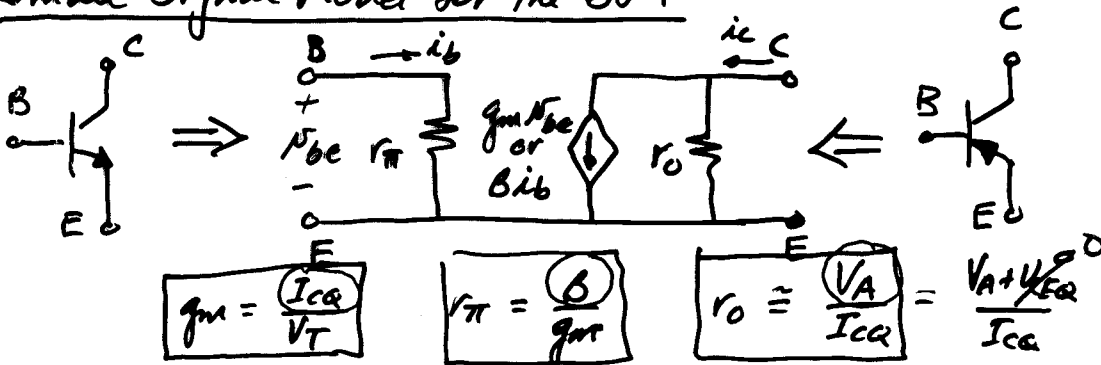


Early Voltage, V_A -

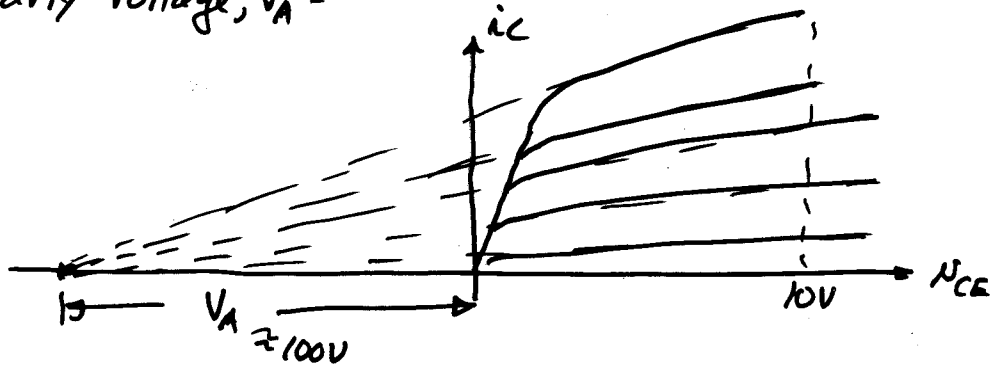

BJT Common-Emitter Amplifier Example


Find the small-signal input resistance, R_{in} , the output resistance, R_{out} , and $\frac{R_{out}}{R_{in}}$ where $I_{CQ} = 1mA$, $\beta_0 = 100$ and $V_A = 100V$. Assume $R_1 || R_2 = R_B = 20K$

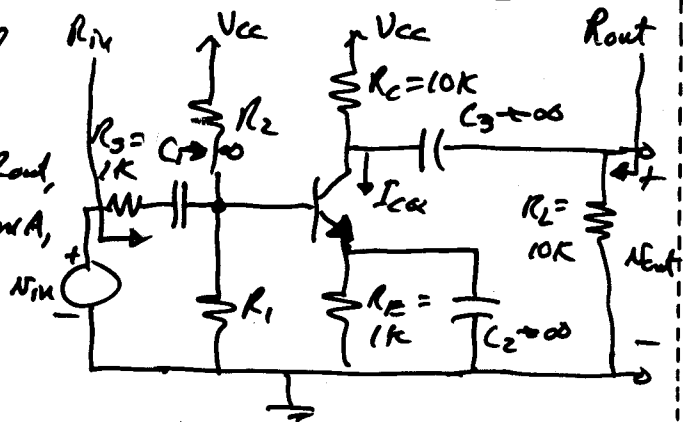


1.) AC equiv. ckt.

$C \rightarrow \infty \Rightarrow$ short
 $V_{cc} \Rightarrow$ short

$\oplus \Rightarrow$ opens

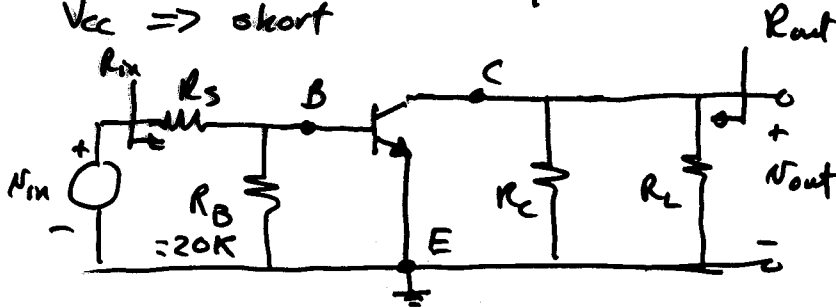

2.) AC or SS model:

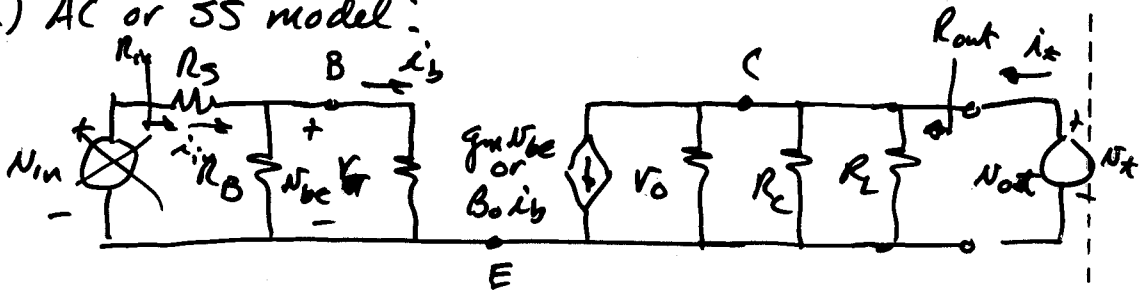

$$R_{in} = R_s + R_B \parallel r_{\pi}$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{1 \text{ mA}}{25 \text{ mV}} = \frac{1}{25} \text{ S}$$

$$R_{out} = r_o \parallel R_L \parallel R_C$$

$$r_{\pi} = \frac{\beta_0}{g_m} = 25 \times 100 = 2.5 \text{ k}\Omega$$

$$r_o \approx \frac{V_A}{I_{CQ}} = \frac{100 \text{ V}}{1 \text{ mA}} = 100 \text{ k}\Omega$$

$$\circ c R_{in} = 1 \text{ k} + 20 \text{ k} \parallel 2.5 \text{ k} = \underline{\underline{3.22 \text{ k}}}$$


$$R_{out} = 100 \text{ k} \parallel 10 \text{ k} \parallel 10 \text{ k} = \underline{\underline{4.7 \text{ k}}}$$

$$\frac{v_{out}}{v_{in}} = \left(\frac{v_{out}}{i_b} \right) \left(\frac{i_b}{v_{in}} \right) = (-\beta_0 R_{out}) \left(\frac{R_B}{r_{\pi} + R_B} \right) \left(\frac{1}{R_{in}} \right)$$

$$i_{in} = \frac{v_{in}}{R_{in}} \rightarrow i_b = i_{in} \frac{R_B}{r_{\pi} + R_B} = \frac{R_B}{r_{\pi} + R_B} \frac{v_{in}}{R_{in}}$$

$$\frac{v_{out}}{v_{in}} = \frac{-\beta_0 R_{out} R_B}{(r_{\pi} + R_B) [R_s + R_B \parallel r_{\pi}]} = \frac{-100 (4.7 \text{ k}) (20 \text{ k})}{(2.5 \text{ k}) (3.22 \text{ k})} = \underline{\underline{-131 \text{ V/V}}}$$

MOSFET Small Signal Model

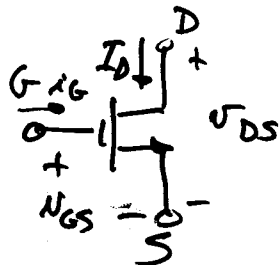

Assume saturation -

$$i_D = \frac{K_n}{2} (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS})$$

$i_G = 0$
Linearize $i_D = f(V_{GS}, V_{DS})$

$$i_d = k_1 v_{gs} + k_2 v_{ds}$$

$$k_1 = \left. \frac{\partial i_D}{\partial V_{GS}} \right|_Q = K_n (V_{GS} - V_{TN}) (1 + \lambda V_{DS}) \approx K_n (V_{GS} - V_{TN})$$

where $\lambda V_{DS} \ll 1$

$$k_1 = g_m = \frac{K_n (V_{GS} - V_T)}{2} = \sqrt{2 K_n I_D}$$


$$(V_{GS} - V_{TN})^2 \approx \frac{2 I_D}{K_n} \rightarrow (V_{GS} - V_T) = \sqrt{\frac{2 I_D}{K_n}}$$

$$k_2 = \left. \frac{\partial i_D}{\partial V_{DS}} \right|_Q = \frac{K_n}{2} (V_{GS} - V_{TN})^2 \lambda = ?$$

$$k_2 = \frac{K_n}{2} (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS}) \frac{\lambda}{1 + \lambda V_{DS}} = \frac{\lambda I_D}{1 + \lambda V_{DS}}$$

$$k_2 \approx \lambda I_D = \frac{1}{r_d} = g_d$$

Small signal MOS model -

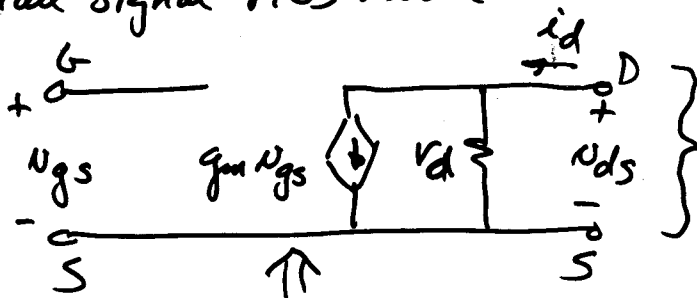


$$i_d = g_m v_{gs} + \frac{v_{ds}}{r_d}$$



Same for PMOS or NMOS

Comments on MOS SS model -

λ interpretation -

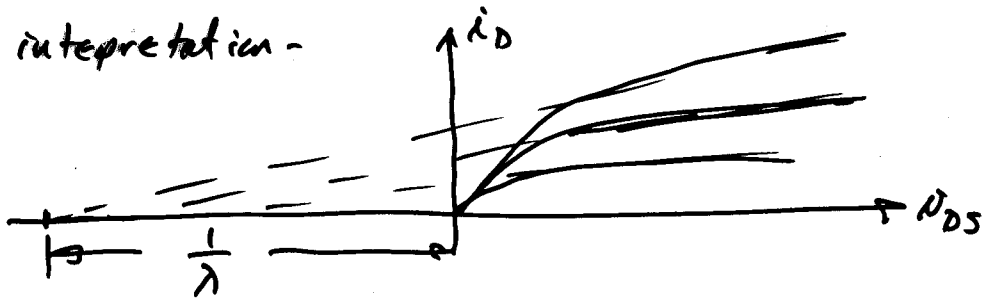

Bulk nodes -

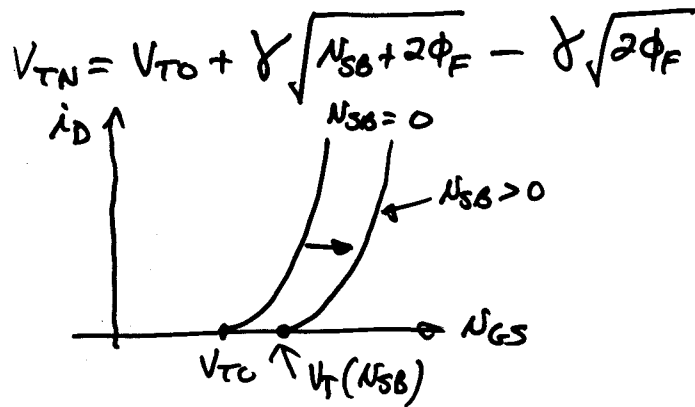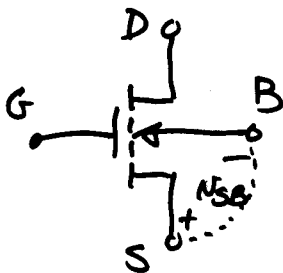

$$i_D = g_m V_{GS} + g_d V_{DS} + k_3 N_{SB}$$

$$k_3 \equiv \left. \frac{\partial i_D}{\partial N_{SB}} \right|_Q = g_{mb} = \frac{\gamma K_n (V_{GS} - V_{T0})}{2 \sqrt{V_{SB} + 2\phi_F}} = M g_m$$

$$M = \frac{\gamma}{2 \sqrt{V_{SB} + 2\phi_F}}$$

