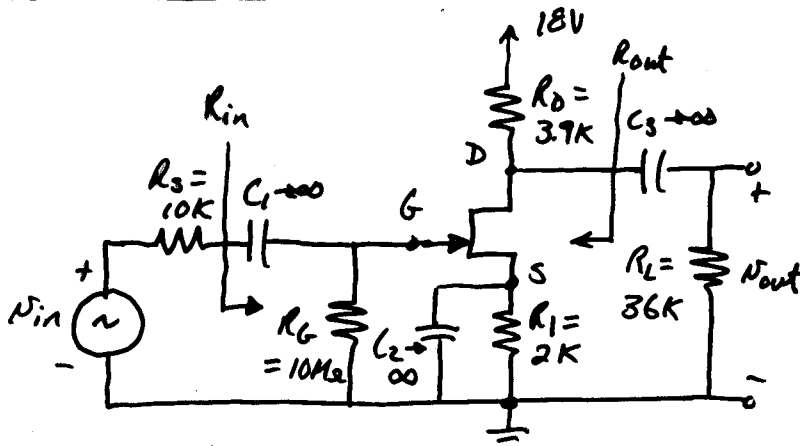


JFET Amplifier Example




If $I_{DSS} = 5\text{mA}$,
 $V_p = -5\text{V}$ and
 $\lambda = \frac{1}{50\text{V}}$, find
 R_{in} , R_{out} and
 $\frac{N_{out}}{N_{in}}$

a.) Q-point

1st eq. $V_{GS} + I_D R_1 = 0$

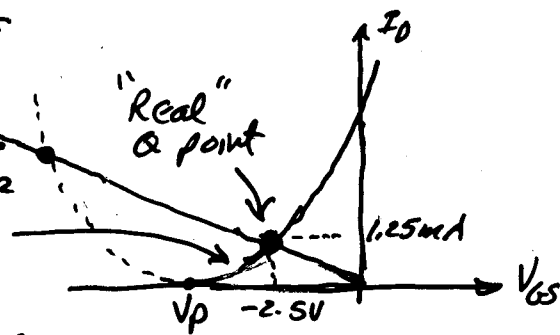2nd eq. $I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2$



$\therefore V_{GS} + R_1 I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2 = 0$

which gives $V_{GS}^2 + 12.5V_{GS} + 25 = 0 \rightarrow V_{GS} = -6.25 \pm 3.75$

$\therefore V_{GS} = -2.5\text{V}$ $I_D = 1.25\text{mA}$ $\nless V_{DS} = 10.6\text{V}$


b.) S.S. model parameters

$$g_m = \frac{2}{|V_p|} \sqrt{I_{DSS} I_D (1 + \lambda V_{DS})} = \frac{2}{5} \sqrt{(5\text{mA})(1.25\text{mA}) \left(1 + \frac{10.6}{50}\right)}$$

$$= 1.1\text{mS}$$

$$r_{ds} = r_o = \frac{1}{\lambda + \frac{V_{DS}}{V_p}} = \frac{50 + 10.6}{1.25\text{mA}} = 48.5\text{k}\Omega$$

c.) S.S. model

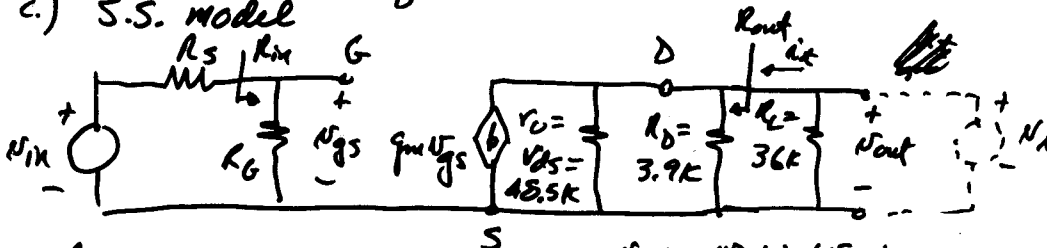

$R_{in} = R_G = 10\text{M}\Omega$

$R_{out} = \frac{v_x}{i_x} = r_{ds} \parallel R_D = 3.6\text{k}\Omega$

$\frac{N_{out}}{N_{in}} = \left(\frac{N_{out}}{N_{GS}}\right) \left(\frac{N_{GS}}{N_{in}}\right)$

$= (-g_m r_{ds} \parallel R_D \parallel R_L) \left(\frac{R_G}{R_s \parallel R_G}\right) = -3.6 \frac{V}{V}$

Summary of Chapt. 13 -

Table 13.6

| | Common-emitter Amplifier | Common-source Amplifier |
|-----------------------------|--|---|
| Voltage Gain | $-\frac{\beta_0 R_c}{r_{\pi} + R_{th}} \left(\frac{R_c}{R_B + R_S} \right)$ $\approx -g_m R_c$ | $(-g_m R_c) \left(\frac{R_G}{R_S + R_G} \right)$ $\approx -g_m R_c$ |
| Rule of thumb voltage gains | $\approx -10 V_{cc}$ | $\approx -V_{DD}$ |
| A_m | $r_{\pi} \parallel R_B$ | $\infty \parallel R_G$ |
| R_{out} | $= R_c \parallel r_o \approx R_c$ | $R_D \parallel r_{ds} \approx R_D$ |



Rules of thumb -

BJT: $-g_m R_c = -\frac{I_c}{V_T} R_c = -\frac{(I_c R_c)}{V_T} \approx -\frac{V_{cc}}{3V_T}$
 $= -\frac{40}{3} V_{cc} \approx -10 V_{cc}$

FET: $-g_m R_D = \frac{-I_D R_D}{V_{GS} - V_T} \approx -\frac{V_{DD}}{3} \frac{2}{V_{GS} - V_T} \approx -V_{DD}$

CHAPTER 14 - TRANSISTOR AMPLIFIERS IN GENERAL

Classes of Amplifiers

1. Common emitter / common source (CE/CS)
- 2.) Common base / common gate (CB/CG)
- 3.) Common collector / common drain (CC/CD)
- 4.) Common nothing


Another classification of amplifiers is:

Inverting - CE, CS or common nothing

Noninverting - CC, CB, CD, CG


Common Nothing NMOS Amplifier (CS - Jaeger)

1.) Complete circuit

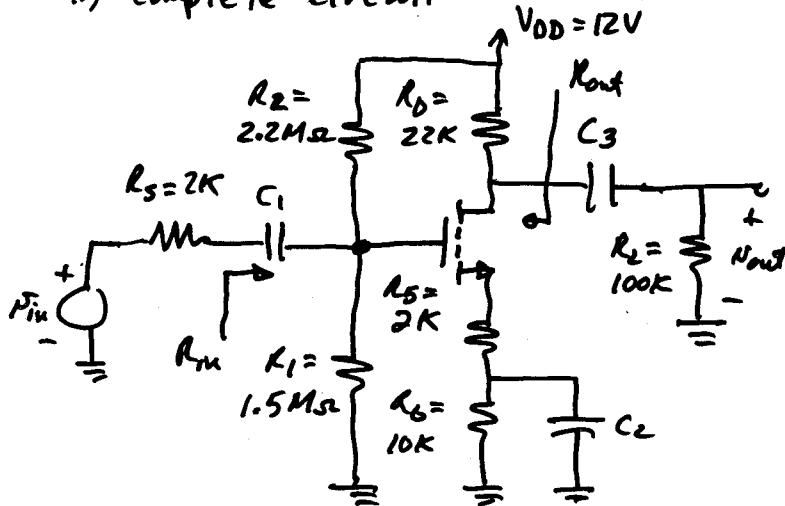


If $K_n = 0.5 \text{ mA/V}^2$,
 $V_{TN} = 1 \text{ V}$ and
 $\lambda = 0.02 \text{ V}^{-1}$
 Do your thing.

2.) AC circuit

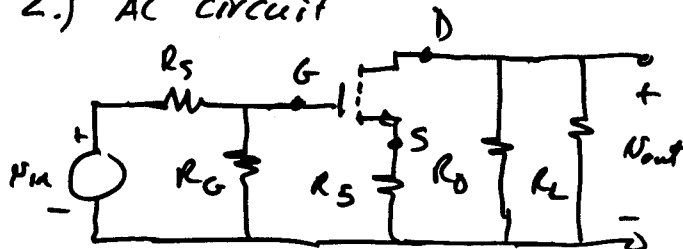

$$R_G = R_1 || R_2$$

3.) AC or SS circuit -

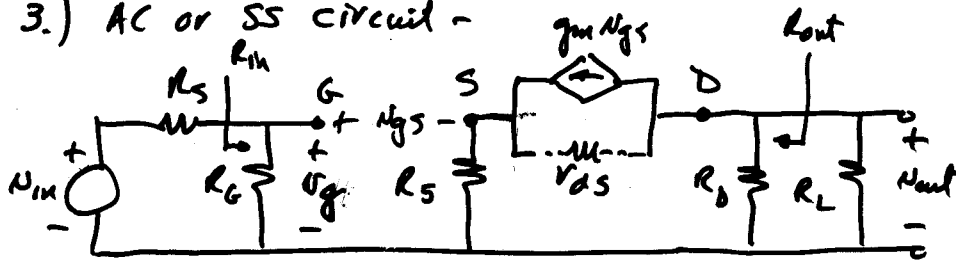

4.) Find $\frac{N_{out}}{N_{in}}$, R_{in} & R_{out}

$$\frac{N_{out}}{N_{in}} = \left(\frac{N_{out}}{N_{gs}}\right) \left(\frac{N_{gs}}{N_g}\right) \left(\frac{N_g}{N_{in}}\right)$$

Assume that r_{ds} can be neglected.