

Quiz #4 - CE and/or CS amplifier ($R_{in}, R_{out}, \frac{N_{out}}{N_{in}}, \frac{i_{out}}{i_{in}}$)


Common Nothing NMOS (Inverting) Amplifier - Cont'd

If $K_n = 0.5 \text{ mA/V}^2$,

$V_{TN} = 1\text{V}$ and
 $\lambda = \frac{1}{50\text{V}}$, find

R_{in}, R_{out} , and
 $\frac{N_{out}}{N_{in}}$ also $\frac{i_{out}}{i_{in}}$.

Note: I changed R_{in} definition

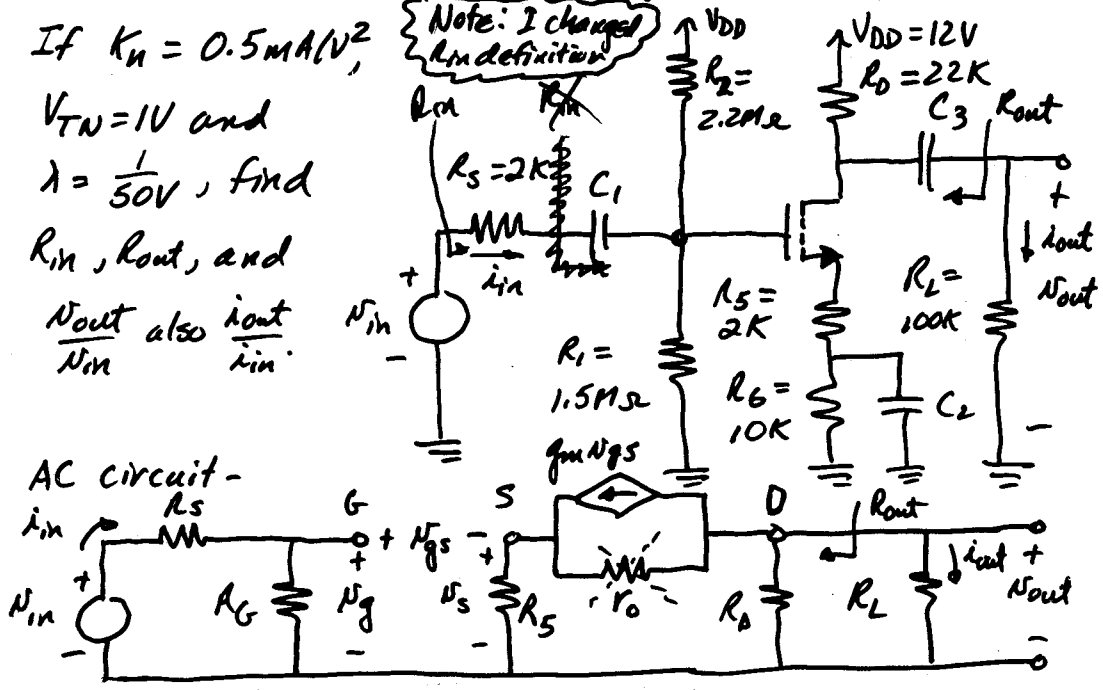

$$R_G = R_1 || R_2 = 0.892 \text{ M}\Omega$$

ASSUME we can neglect r_o .

- r_o is large other external resistors are small
- Lot of work for no effort.

$$\frac{N_{out}}{N_{in}} = \left(\frac{N_{out}}{N_{gs}} \right) \left(\frac{N_{gs}}{N_g} \right) \left(\frac{N_g}{N_{in}} \right)$$

$$\frac{N_{out}}{N_{gs}} = -g_m (R_D || R_L)$$


"Nab trick" $\rightarrow N_{ab} = N_a - N_b \rightarrow N_{gs} = N_g - N_s$

$$N_{gs} = N_g - g_m N_{gs} R_s \rightarrow N_{gs} (1 + g_m R_s) = N_g$$

$$\frac{N_{gs}}{N_g} = \frac{1}{1 + g_m R_s}$$

$$\therefore \frac{N_{out}}{N_{in}} = \left[-g_m (R_D || R_L) \right] \left[\frac{1}{1 + g_m R_s} \right] \left[\frac{R_L}{R_s + R_G} \right]$$
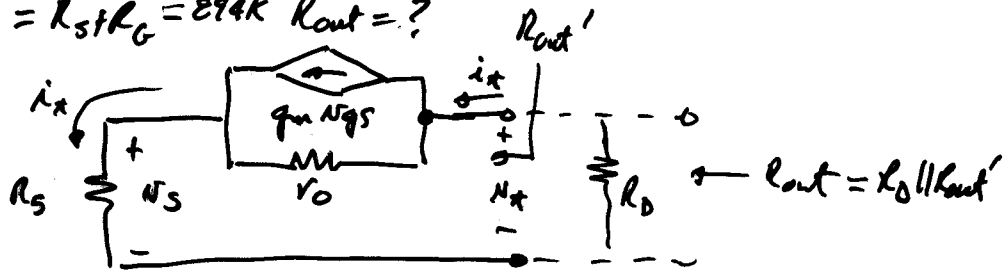
$$R_{in} = R_s \parallel R_G = 894K \quad R_{out} = ?$$



a.) $r_o = \infty$

$$i_x = g_m v_{gs} = g_m (v_g - v_s) = -g_m v_s$$

$$v_s = i_x R_s$$

$$R_{out}' = \frac{v_x}{i_x} \quad \text{If we apply } v_x, i_x = 0 \Rightarrow R_{out}' = \infty$$

$$\therefore R_{out} = R_D = 22k\Omega$$

b.) $r_o \neq \infty$

$$v_x = r_o [i_x - g_m v_{gs}] + i_x R_s$$

$$v_{gs} = v_g - v_s = -v_s = -i_x R_s$$

$$\therefore v_x = r_o i_x - g_m r_o (-i_x R_s) + i_x R_s$$

$$\frac{v_x}{i_x} = r_o + R_s + g_m r_o R_s = 223k + 2k + (509)(0.223)2k = 452k$$

$$R_{out} = R_D \parallel [r_o + R_s + g_m r_o R_s] = 22k \parallel 452k = 20.98k$$

Assume $I_{DS} = 241\mu A \rightarrow V_{GS} = 1.982V \quad \& \quad V_{DS} = 3.81V$


$$g_m = \sqrt{2K_n I_{DS} (1 + \lambda V_{DS})} = \sqrt{2 \cdot 500 \cdot 241 (1 + \frac{3.81}{50})} = 509\mu S$$

$$r_o = \frac{1}{\lambda + \lambda V_{DS}} = \frac{50 + 3.81}{0.241mA} = 223k\Omega$$


$$\frac{v_{out}}{v_{in}} = \frac{(-509\mu S)(22k \parallel 100k)}{1 + (509\mu S)(2k)} \left(\frac{892}{894} \right) = -4.54V/V$$

$$\frac{i_{out}}{i_{in}} = \frac{v_{out}/R_L}{v_{in}/R_{in}} = \left(\frac{v_{out}}{v_{in}} \right) \left(\frac{R_{in}}{R_L} \right) = -4.54 \left(\frac{894k}{100k} \right) \approx -40 \frac{A}{A}$$



Inverting CE Amplifier

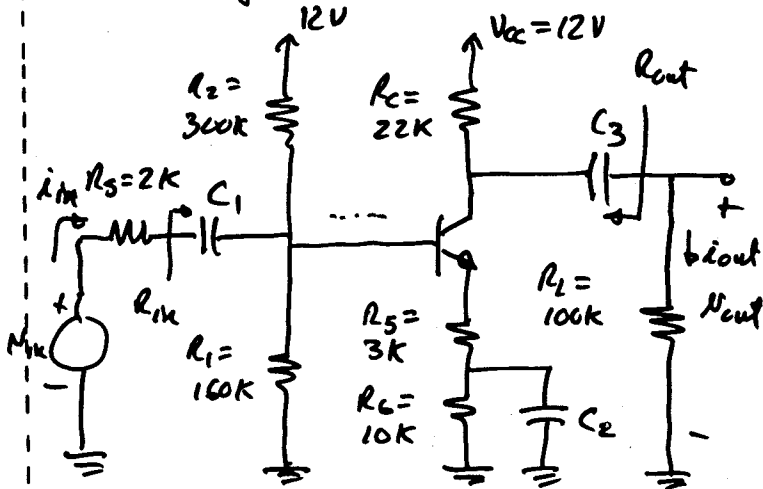

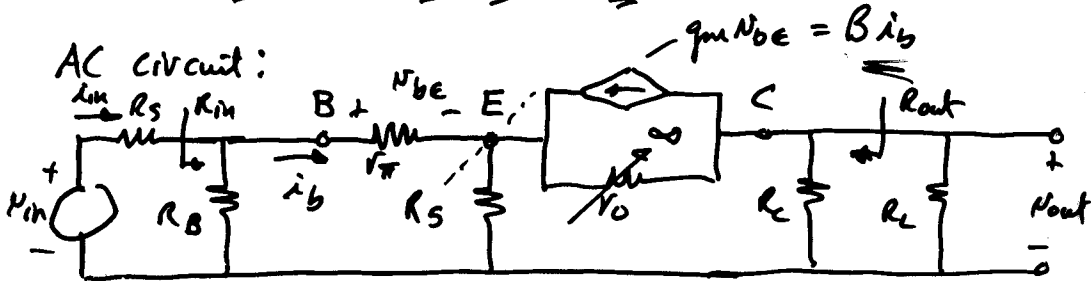
$\beta_F = \beta_o = 100$
 $V_A = 50V$
 Room temperature
 Find $\frac{v_{out}}{v_{in}}$, R_{in} , R_{out}
 if $I_{CQ} = 245\mu A$
 $V_{CEQ} = 3.64V$



$R_B = R_1 || R_2 = 104k\Omega$
 $g_m = \frac{I_{CQ}}{V_T} = \frac{245\mu A}{25mV} \approx 10mS$
 $r_{\pi} = \frac{\beta}{g_m} = \frac{100 \cdot 25mS}{245\mu A} = 10.2k\Omega$

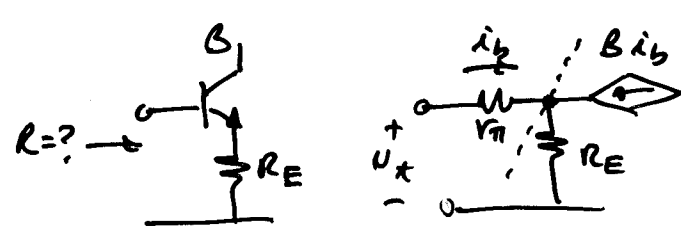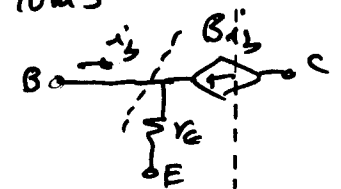

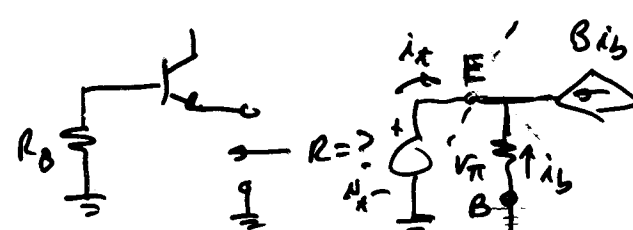$v_x = i_b r_{\pi} + (1+\beta) i_b R_E$
 $\frac{v_x}{i_b} = r_{\pi} + (1+\beta) R_E$



$v_x = -i_x (r_{\pi} + R_B)$
 $i_x = -i_b (1+\beta)$
 $v_x = + \frac{r_{\pi} + R_B}{1+\beta} i_x$
 $\therefore R = \frac{r_{\pi} + R_B}{1+\beta}$

$$\infty \quad R_{in} = R_B \parallel [r_{\pi} + (1+\beta)R_E]$$

$$R_{out} = R_C$$

$$\begin{aligned} \frac{N_{out}}{N_{in}} &= \left(\frac{N_{out}}{I_b}\right) \left(\frac{I_b}{I_m}\right) \left(\frac{I_m}{N_{in}}\right) \\ &= [-\beta(R_C \parallel R_L)] \left[\frac{R_B}{R_B + r_{\pi} + (1+\beta)R_E}\right] \left[\frac{1}{R_{in} + R_S}\right] \end{aligned}$$

$$R_{in} = 104k \parallel [10.2k + (100)3k] = 104k \parallel 313k = \underline{\underline{78.3k\Omega}}$$

$$R_{out} = \underline{\underline{22k\Omega}}$$

$$\frac{N_{out}}{N_{in}} = [-100 \cdot 22k \parallel 100k] \left[\frac{104k}{104k + 313k}\right] \left[\frac{1}{80.3k}\right] = -\underline{\underline{5.61 \frac{V}{V}}}$$



$$\text{gain} \rightarrow -\frac{R_C}{R_E} = -\frac{22k}{3k} = -7 \frac{V}{V}$$