


Jaeger: Overall voltage gain (N_{out}/N_{in}) vs. terminal voltage gain (N_{out}/N_b or N_{out}/N_g).

$$\frac{N_{out}}{N_{in}} = \left(\frac{N_{out}}{N_b}\right) \left(\frac{N_b}{N_{in}}\right) \text{ or } \left(\frac{N_{out}}{N_g}\right) \left(\frac{N_g}{N_{in}}\right)$$

Common drain amplifier



Find R_{in} , R_{out} ,
and N_{out}/N_{in}

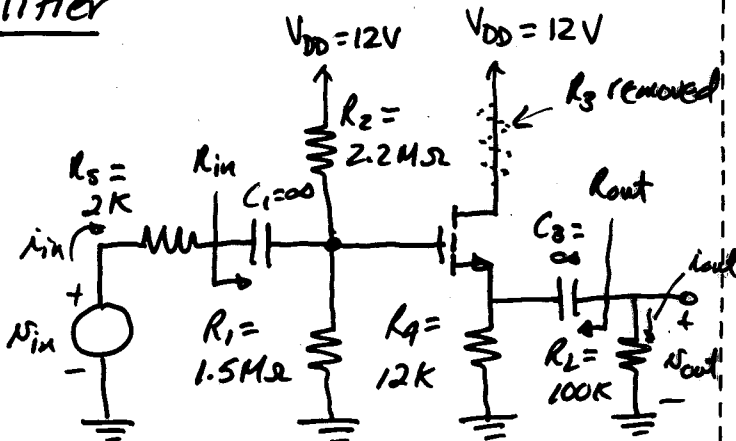given $k_n = 0.5 \text{ mA/V}^2$,
 $V_{TN} = 1 \text{ V}$, $\lambda = 0.02 \text{ V}^{-1}$,
 $I_{DQ} = 241 \mu\text{A}$ and
 $V_{DSQ} = 3.8 \text{ V}$




Small-signal model:
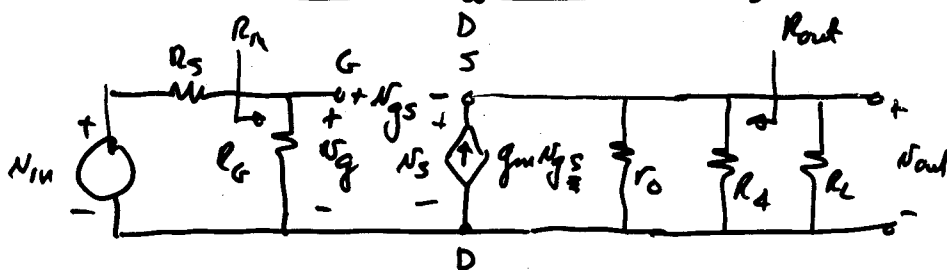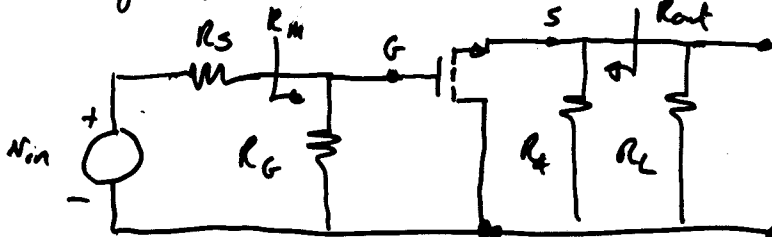
$$g_m = \sqrt{2k_n I_{DQ} (1 + \lambda V_{DSQ})} = 509 \mu\text{S} \quad \text{and} \quad r_o = \frac{1}{\lambda} \frac{V_{DSQ}}{I_{DQ}} = 223 \text{ k}\Omega$$


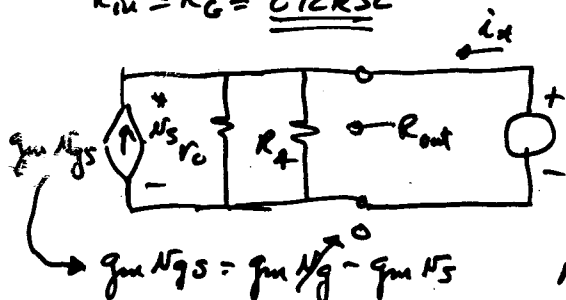
$$R_{in} = R_G = \underline{872 \text{ k}\Omega}$$



$$\Rightarrow R_{out} = \frac{N_x}{i_x}$$

$$i_x = \frac{N_x}{R_4} + \frac{N_x}{r_o} + g_m N_x$$

$$R_{out} = r_o \parallel R_4 \parallel \frac{1}{g_m} = 223 \text{ k}\Omega \parallel 12 \text{ k}\Omega \parallel \frac{1 \text{ k}\Omega}{0.509}$$

$$= \underline{1.96 \text{ k}\Omega} = 1.675 \text{ k}\Omega$$

$$\frac{N_{out}}{N_{in}} = \left(\frac{N_{out}}{N_{gs}} \right) \left(\frac{N_{gs}}{N_g} \right) \left(\frac{N_g}{N_{in}} \right)$$

$$N_{gs} = N_g - N_s$$

Ignoring r_o ,

$$= \left[\frac{g_m (R_4 \parallel R_L)}{1 + g_m (R_4 \parallel R_L)} \right] \left[\frac{R_g}{R_s + R_g} \right] \left[\frac{N_g}{N_{in}} \right]$$

$$N_s = g_m (R_4 \parallel R_L) N_{gs}$$


$$N_{gs} = N_g - g_m (R_4 \parallel R_L) N_{gs}$$

$$N_{gs} [1 + g_m (R_4 \parallel R_L)] = N_g$$

$$\frac{N_{out}}{N_{in}} = \left(\frac{R_g}{R_s + R_g} \right) \left[\frac{g_m (R_4 \parallel R_L)}{1 + g_m (R_4 \parallel R_L)} \right] = \left(\frac{892}{892} \right) \left[\frac{5.45}{1 + 30.5} \right]$$

$$= \underline{\underline{0.966}} \text{ V/V}$$

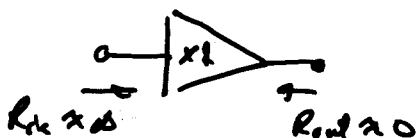The common drain is called source follower or a buffer.



Check out the current gain of this circuit $\left(\frac{i_{out}}{i_{in}} \right)$

It should be very larger than 1

$$\frac{i_{out}}{i_{in}} = \frac{N_{out}/R_L}{N_{in}/R_{in}} = \left(\frac{N_{out}}{N_{in}} \right) \frac{R_{in}}{R_L} \approx 1 \times \frac{894}{100} = 8.94 \text{ A/A}$$