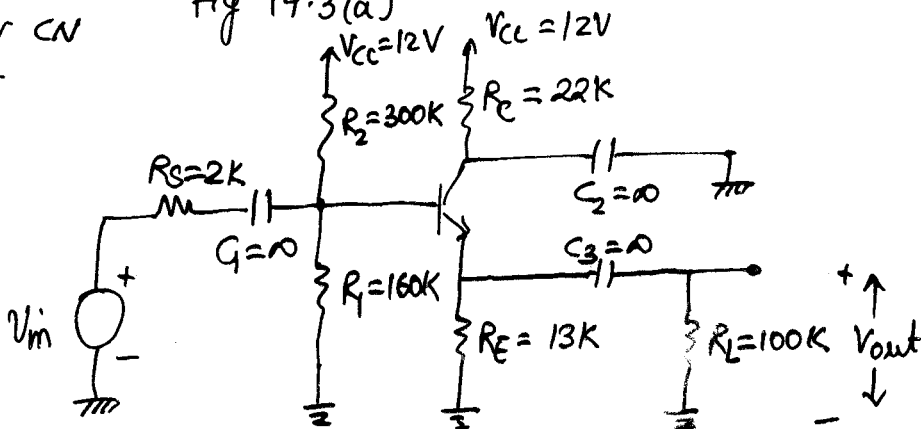


Common Collector (Emitter follower)


Quiz 5
1. CC/CD or CN
2. BJT/FET

Fig 14.3(a)



Assume: $\beta_F = 100$, $V_A = 50V$, Q point: $\{ I_C = 245 \mu A \}$
 $\{ V_{CE} = 3.64 V \}$


Small-signal model

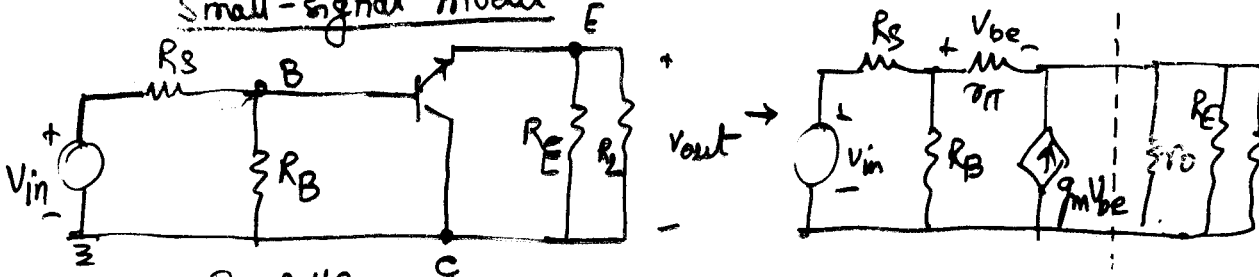

$R_B = R_1 || R_2$

$R_B = R_1 || R_2 = 104.35K\Omega$, $g_m = \frac{I_C}{V_T} = 9.8 mS$

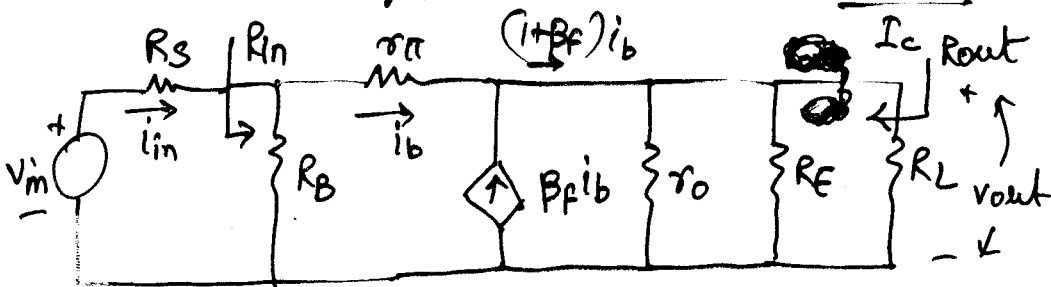$r_{\pi} = \frac{\beta_F}{g_m} = 10.2K\Omega$, $r_o = \frac{V_A + V_{CE}}{I_C} = 219K\Omega$



1. $R_{in} = ??$

$$R_{in} = R_B \parallel \{ r_{\pi} + (1 + \beta_F)(r_o \parallel R_E \parallel R_L) \}$$

$$= 104.35k \parallel \{ 10.2k\Omega + 101(17.3k) \} = 98.5k\Omega$$

2. $\left(\frac{V_{out}}{V_{in}}\right) = ??$


$$\left(\frac{V_{out}}{V_{in}}\right) = \left(\frac{V_{out}}{i_b}\right) \left(\frac{i_b}{i_{in}}\right) \left(\frac{i_{in}}{V_{in}}\right)$$

$$= \left\{ (1 + \beta_F)(r_o \parallel R_E \parallel R_L) \right\} \left\{ \frac{R_B}{R_B + r_{\pi} + (1 + \beta_F)(r_o \parallel R_E \parallel R_L)} \right\} \left\{ \frac{1}{R_S + R_{in}} \right\}$$

$$= \left\{ (101)(17.3k) \right\} \left\{ \frac{104.35k}{104.35k + 170k} \right\} \left\{ \frac{1}{2k + 98.5k} \right\}$$

$$= 0.963 \text{ v/v}$$

3. $R_{out} = ?? \Rightarrow V_{in} = 0$

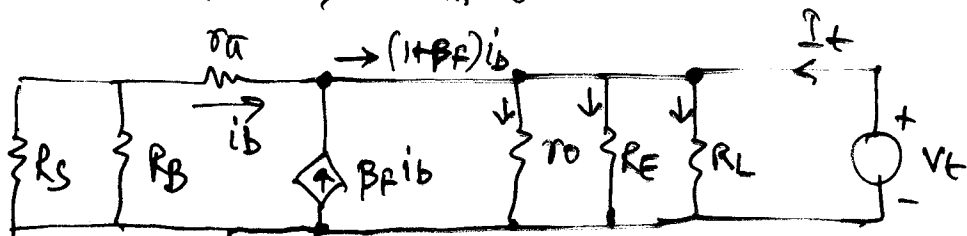


$$R_{out} = \frac{V_t}{I_t}$$

$$\sum i = 0 \Rightarrow V_t \left(\frac{1}{R_E} + \frac{1}{R_L} + \frac{1}{r_o} \right) - (1 + \beta_F) i_b = 0 \quad I_t$$

$$i_b = \frac{-V_t}{\{ r_{\pi} + (R_S \parallel R_B) \}}$$



$$R_{out} = \frac{V_t}{I_t} = \frac{1}{\left[\left(\frac{1}{r_o} + \frac{1}{R_E} + \frac{1}{R_C} \right) + \frac{(1+\beta_F)}{\{r_{\pi} + (R_S \parallel R_B)\}} \right]} = 119.6 \Omega$$

Common Base amplifier

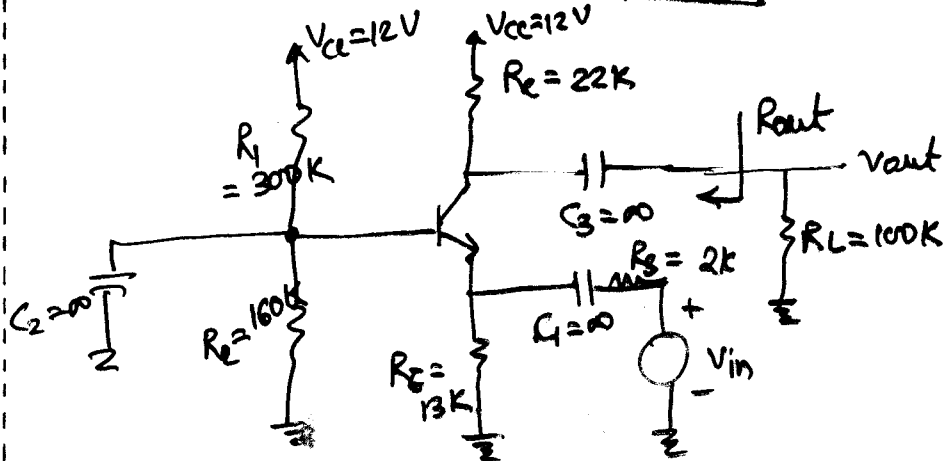


$\beta_F = 100$
 $V_A = 50V$
 $I_C = 245 \mu A$
 $V_{CE} = 3.4V$

Small-signal model

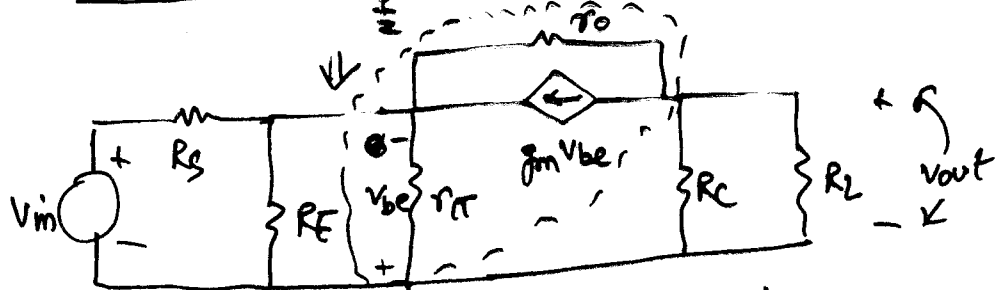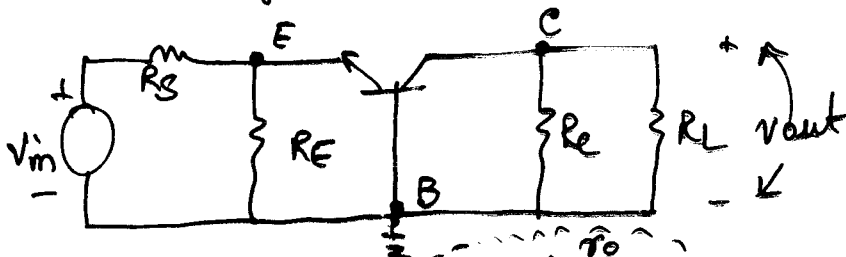


$r_o \rightarrow$ neglect

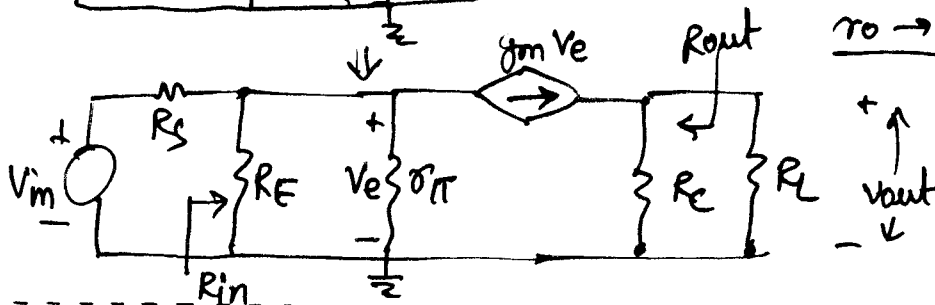

$$g_m = \frac{I_c}{V_t} = \frac{245 \mu A}{25 mV} = 9.8 mS$$

$$r_o = \frac{V_A}{I_c} = 204 k\Omega, \quad r_{\pi} = \frac{\beta_F}{g_m} = 10.2 k\Omega.$$

① $R_{in} = ??$

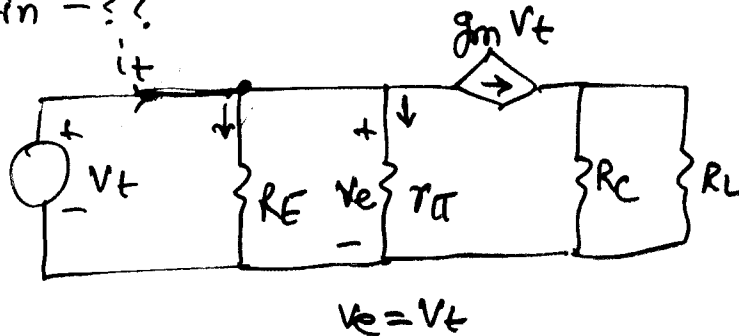

$$R_{in} = \frac{V_t}{i_t}$$

$$i_t = \frac{V_t}{R_E} + \frac{V_t}{r_{\pi}} + g_m V_t$$

$$= V_t \left(\frac{1}{R_E} + \frac{1}{r_{\pi}} + g_m \right)$$

$$= V_t \left(\frac{1}{R_E} + \frac{g_m}{\beta_F} + g_m \right)$$

$$i_t \approx V_t \left(\frac{1}{R_E} + g_m \right)$$

$$R_{in} \approx \frac{V_t}{i_t} \approx \frac{1}{\left(g_m + \frac{1}{R_E} \right)} \approx 101 \Omega$$

2. $\left(\frac{V_{out}}{V_{in}}\right) = ??$

$$\left(\frac{V_{out}}{V_{in}}\right) = \left(\frac{v_{out}}{v_e}\right) \left(\frac{v_e}{V_{in}}\right)$$

$$= \left\{ g_m (R_e \parallel R_L) \right\} \left\{ \frac{R_{in}}{R_{in} + R_s} \right\} = 8.48 \text{ V/V}$$

3. $R_{out} = ??$

