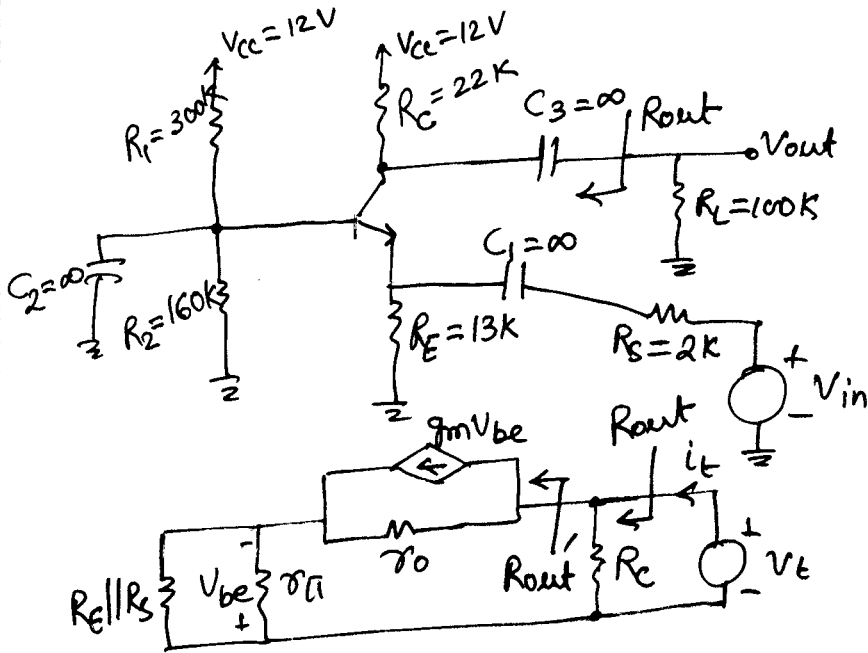


Common Base Amplifier (continued)

Output resistance




Case 1. When  $r_o \rightarrow \infty$

$$R_{out} = R_c$$

Case 2. When  $r_o$  is not neglected

$$R_{out} = (R_c \parallel R_{out}')$$

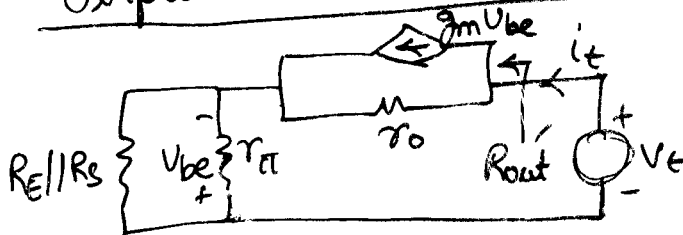Output resistance at drain ( $R_{out}'$ )



$$v_t = (i_t - g_m v_{be}) r_o - v_{be} = r_o i_t - v_{be} (1 + g_m r_o)$$

$$-v_{be} = i_t (r_{\pi} \parallel R_E \parallel R_S)$$

$$v_t = r_o i_t + i_t (r_{\pi} \parallel R_E \parallel R_S) (1 + g_m r_o)$$


$$R_{out}' = \frac{v_t}{i_t} = \left[ r_o + (r_{\pi} \parallel R_E \parallel R_S) (1 + g_m r_o) \right]$$

$$= 3.166 \text{ M}\Omega$$

$$R_{out} = (R_C \parallel R_{out}')$$

$$= (22\text{K} \parallel 3.166 \text{ M}\Omega) \cong 22\text{K}$$

Common gate amplifier


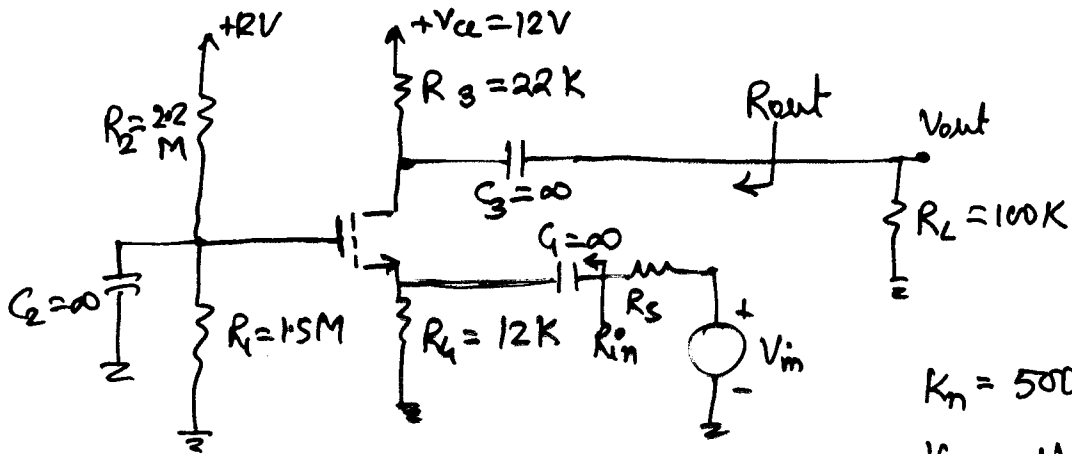


$K_n = 500 \mu A/V^2$   
 $V_{TN} = 1V$   
 $\lambda = 0.02 V^{-1}$

Q point  $\left\{ \begin{array}{l} I_{DS} = 241 \mu A \\ V_{DS} = 3.8V \end{array} \right\}$

$g_m = \sqrt{2K_n \cdot I_{DS} (1 + \lambda V_{DS})} = 509 \mu S$

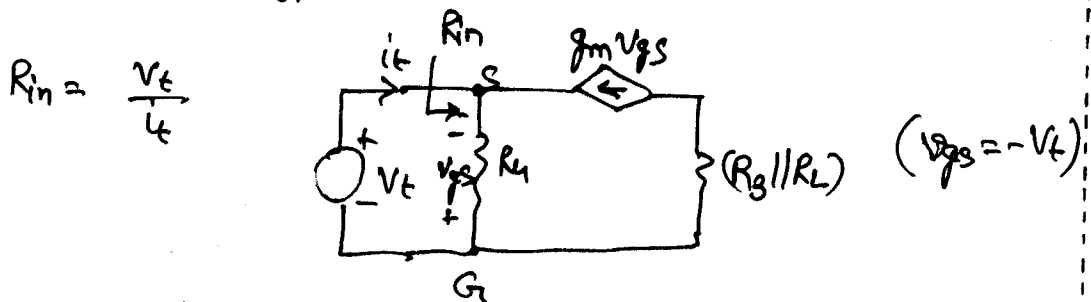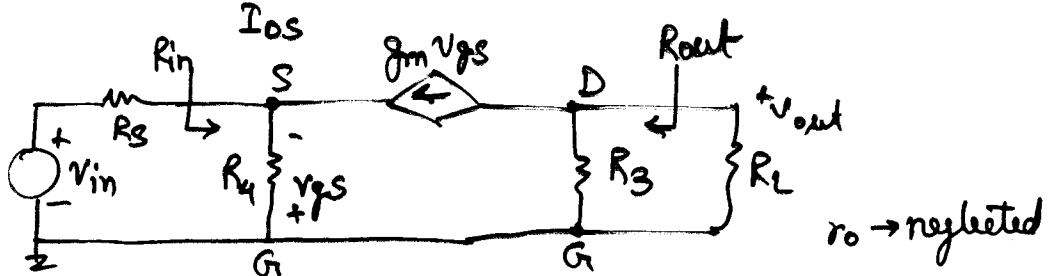$r_o = \frac{1/\lambda + V_{DS}}{I_{DS}} = 223 K\Omega$



$i_t = \frac{v_t}{R_4} + g_m v_{gs} = \frac{v_t}{R_4} + g_m \cdot v_t$

$R_{in} = \frac{v_t}{i_t} = \frac{R_4}{(1 + g_m R_4)} \approx \frac{1}{g_m} \approx 1.96 K\Omega$


$$\begin{aligned} \left( \frac{v_{out}}{v_{in}} \right) &= \left( \frac{v_{out}}{v_{gs}} \right) \left( \frac{v_{gs}}{v_{in}} \right) \\ &= \left[ -g_m (R_3 \parallel R_L) \right] \left[ \frac{-R_{in}}{R_{in} + R_s} \right] = 4.54 \text{ V/V} \end{aligned}$$

$$\underline{R_{out} = ??}$$

If  $r_o \rightarrow$  neglected,  $R_{out} = R_3 = 22\text{K}$

$$R_{out} = (R_3 \parallel R_{out}')$$

$R_{out}' =$  resistance at the drain

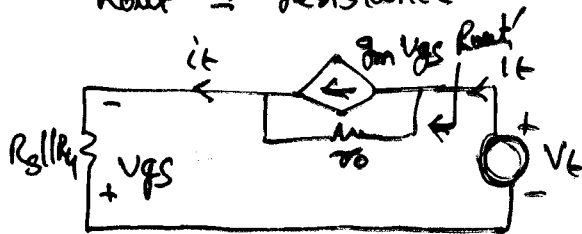

$$R_{out}' = \frac{v_t}{i_t}$$

$$v_t = (i_t - g_m v_{gs}) r_o - v_{gs} = i_t r_o - v_{gs} (1 + g_m r_o)$$

$$v_{gs} = \underline{\underline{-i_t (R_s \parallel R_4)}}$$

$$v_t = i_t r_o + i_t (1 + g_m r_o) (R_s \parallel R_4)$$

$$= i_t \left\{ r_o + (1 + g_m r_o) (R_s \parallel R_4) \right\}$$

$$R_{out}' = \frac{v_t}{i_t} = \left[ r_o + (1 + g_m r_o) (R_s \parallel R_4) \right] = 416 \text{ K}\Omega$$

$$R_{out} = (R_3 \parallel R_{out}') = (22\text{K} \parallel 416\text{K}\Omega)$$