
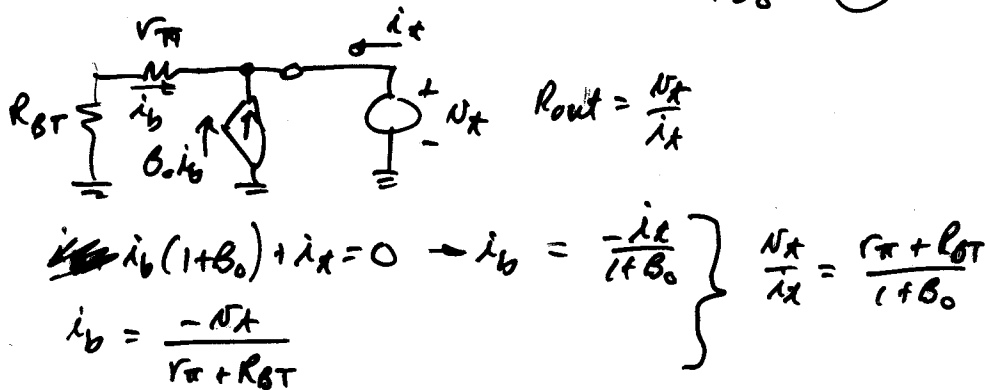



Comments on emitter follower output resistance:

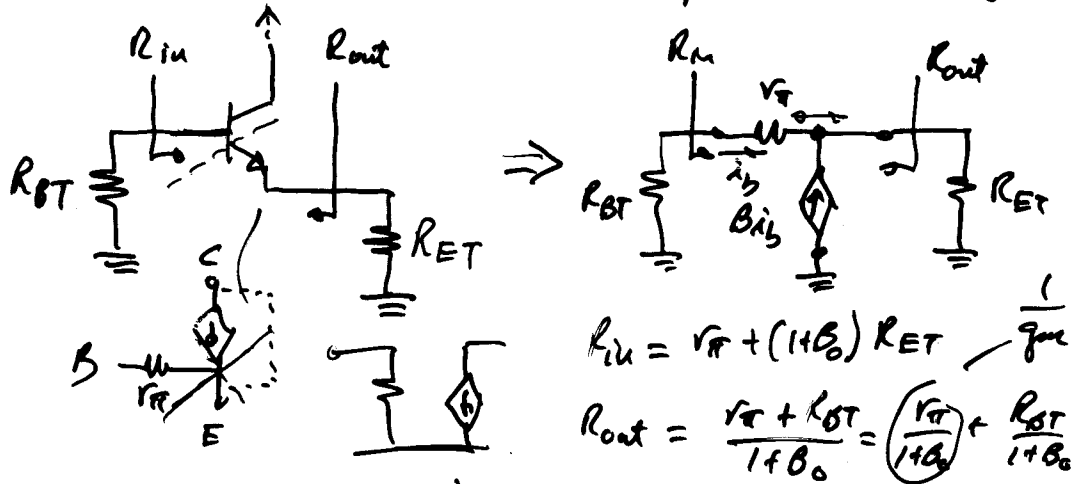

CHAPTER 15 - MULTISTAGE AMPLIFIERS

- Multistage Amps
  - Darlington
  - Cascode
- Diff. amps

Multistage Amplifier Example

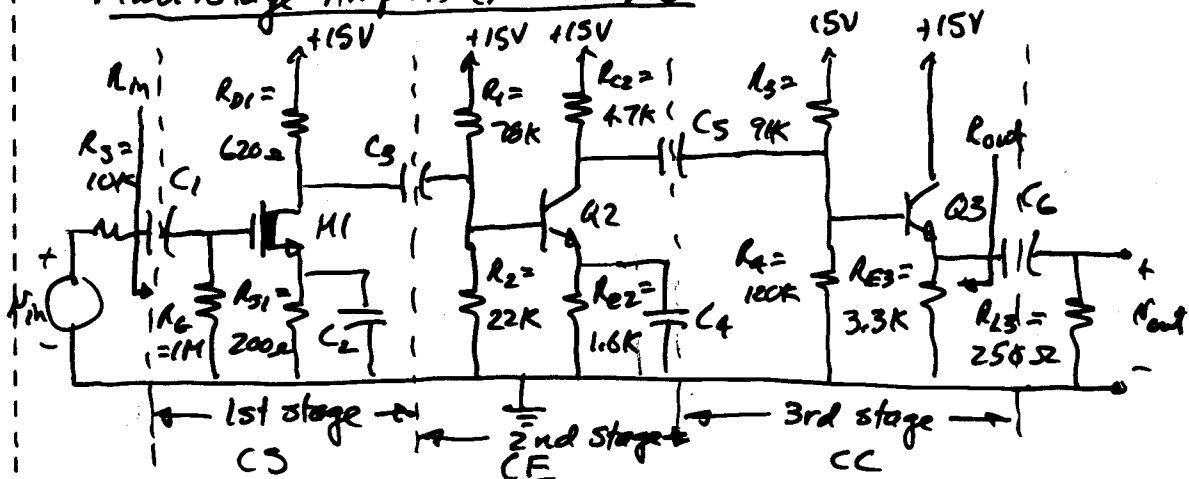

Transistor parameters:

M1:  $k_n = 10 \text{ mA/V}^2$ ,  $V_{TN} = -2 \text{ V}$ ,  $\lambda = 0.02 \text{ V}^{-1}$

Q2:  $\beta_o = \beta_F = 150$ ,  $V_A = 80 \text{ V}$  and  $V_{BEQ} = 0.6 \text{ V}$

Q3:  $\beta_o = \beta_F = 80$ ,  $V_A = 60 \text{ V}$  and  $V_{BEQ} = 0.6 \text{ V}$


Q-point and s.s. model parameters:

M1:  $I_{D1} = 5 \text{ mA}$ ,  $V_{D1} = 10.9 \text{ V} \rightarrow g_{m1} = 10 \text{ mS}$   $r_{o1} = 12.2 \text{ k}\Omega$


Q2:  $I_{C2} = 1.57 \text{ mA}$ ,  $V_{CE2} = 5.09 \text{ V} \rightarrow g_{m2} = 62.8 \text{ mS}$   
 $r_{\pi 2} = 2.39 \text{ k}\Omega$   
 $r_{o2} = 54.2 \text{ k}\Omega$

Q3:  $I_{C3} = 1.99 \text{ mA}$ ,  $V_{CE3} = 8.3 \text{ V} \rightarrow g_{m3} = 79.6 \text{ mS}$   
 $r_{\pi 3} = 1 \text{ k}\Omega$   
 $r_{o3} = 34.4 \text{ k}\Omega$

Simplified AC circuit:

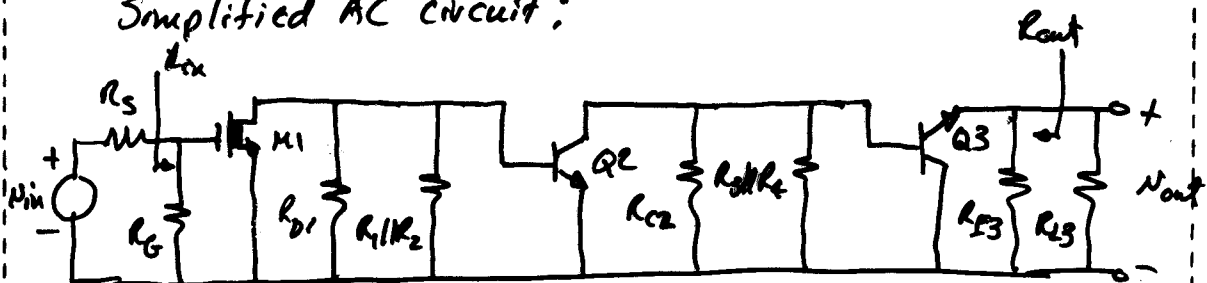

Small-signal circuit:

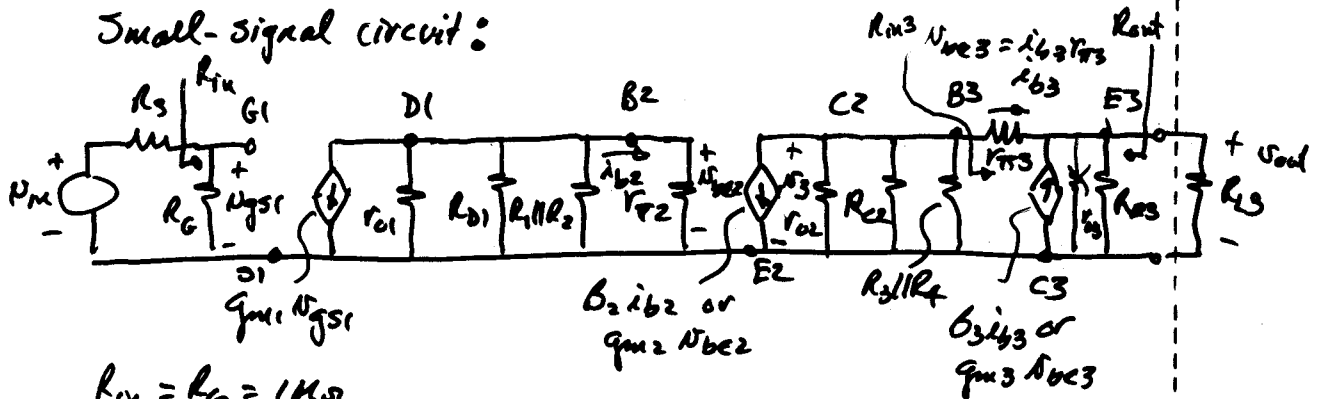

$R_{in} = R_G = 1 \text{ k}\Omega$

$$R_{out} = r_{o3} \parallel R_{E3} \parallel \left[ \frac{r_{\pi 3} + r_{o2} \parallel R_{C2} \parallel R_{B3} \parallel R_E}{1 + \beta_3} \right]$$

$$\approx 3.3 \text{ k}\Omega \parallel \left[ \frac{1 \text{ k}\Omega + 4.7 \text{ k}\Omega \parallel 51.75 \text{ k}\Omega \parallel 54.2 \text{ k}\Omega}{81} \right] = \underline{60.4 \Omega} \approx \frac{1}{g_{m3}}$$

$$\frac{N_{out}}{N_{in}} = \left( \frac{N_{out}}{N_{be3}} \right) \left( \frac{N_{be3}}{N_3} \right) \left( \frac{N_3}{N_{be2}} \right) \left( \frac{N_{be2}}{N_{gs1}} \right) \left( \frac{N_{gs1}}{N_{in}} \right)$$

$$N_{out} = i_{b3} (1 + \beta_3) [r_{o3} \parallel R_{E3} \parallel R_{L3}] \approx \frac{N_{be3}}{r_{\pi 3}} (1 + \beta_3) (R_{E3} \parallel R_{L3}) = 18.82 \text{ V}$$

$$\frac{N_{be3}}{N_3} = ?$$

$$R_{in3} = r_{\pi 3} + (1 + \beta_3) R_{E3} \parallel R_{L3}$$

$$i_{b3} = \frac{N_3}{R_{in3}} = \frac{N_{be3}}{r_{\pi 3}} \rightarrow \frac{N_{be3}}{N_3} = \frac{r_{\pi 3}}{R_{in3}}$$

$$\frac{N_{be3}}{N_3} = \frac{r_{\pi 3}}{R_{in3}} = \frac{1}{19.82}$$

$$\frac{N_3}{N_{be2}} = -g_{m2} (r_{o2} \parallel R_{C2} \parallel R_{in3} \parallel R_3 \parallel R_4) = -62.8 (3.322) = -208.6 \text{ V/V}$$

$$\frac{N_{be2}}{N_{gs1}} = -g_{m1} (r_{o1} \parallel R_{D1} \parallel R_L \parallel R_2 \parallel r_{o2}) = -4.786 \text{ V/V}$$

$$\frac{N_{gs1}}{N_{in}} = \frac{R_6}{R_5 \parallel R_6} = \frac{1}{1.01}$$

$$\frac{N_{out}}{N_{in}} = \underline{\underline{738.6 \text{ V/V}}}$$