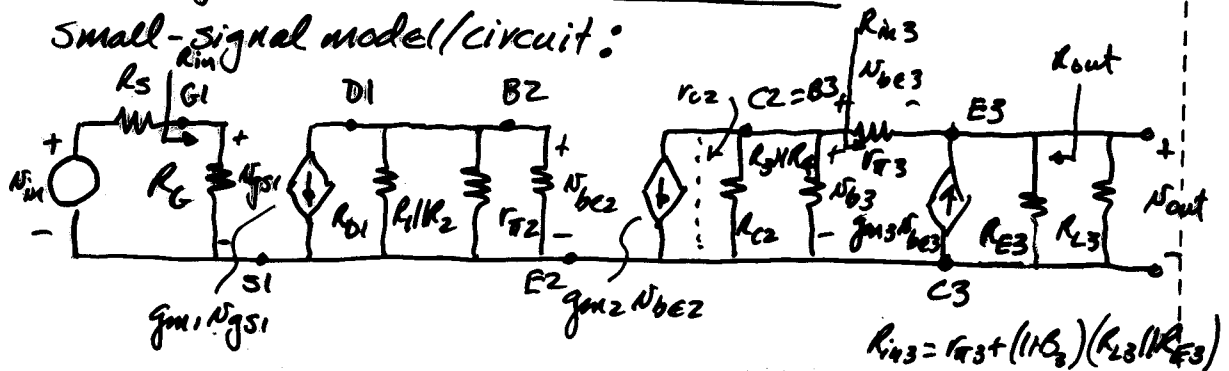


Multistage Amplifier Example - Cont'd

Small-signal model/circuit:



$$\frac{V_{out}}{V_{in}} = \left( \frac{V_{out}}{V_{be3}} \right) \left( \frac{V_{be3}}{V_{b3}} \right) \left( \frac{V_{b3}}{V_{be2}} \right) \left( \frac{V_{be2}}{V_{gs1}} \right) \left( \frac{V_{gs1}}{V_{in}} \right)$$

$$= \left[ \frac{(1483)(R_{E3} \parallel R_{L3})}{r_{\pi 3}} \right] \left[ \frac{r_{\pi 3}}{R_{in3}} \right] \left[ -g_{m2} (r_{o2} \parallel R_{c2} \parallel R_3 \parallel R_4 \parallel R_{in3}) \right]$$

$$\times \left[ -g_{m1} (r_{o1} \parallel R_{D1} \parallel R_1 \parallel R_2 \parallel r_{D2}) \right] \left[ \frac{R_G}{R_S \parallel R_G} \right]$$

$$\frac{V_{out}}{V_{in}} = (18.82) \left( \frac{1}{19.82} \right) (-208.6) (-4.786) \left( \frac{1}{1.01} \right) = \underline{\underline{938.6 \frac{V}{V}}}$$

Find the input signal to keep the amplifier in "small signal" operation:


For s.s. operation -

FET  $V_{gs} \leq 0.2 (V_{GS} - V_T)$

BJT  $V_{be} \leq 5mV$

Stage 1
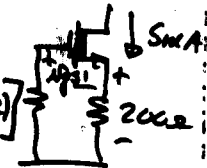
$$V_{gs1} \leq 0.2 (V_{GS1} - V_T) = 0.2 [-5mA \times 200\Omega - (-2)] = 0.2V$$



$$\therefore V_{in1(max)} = 1.01 \times 0.2V = \underline{\underline{0.2V}}$$


Stage 2

$$V_{be2} \leq 5mV \quad \left| \frac{V_{be2}}{V_{in}} \right| = 4.786 \rightarrow V_{in2(max)} = \frac{5mV}{4.786} = \underline{\underline{1.04mV}}$$

Stage 3


$$V_{be3} \leq 5mV \rightarrow V_{in3(max)} = \frac{5mV}{102.5mV} \left( \frac{V_{be3}}{V_{b3}} \right) \left( \frac{V_{b3}}{V_{be2}} \right) \left( \frac{V_{be2}}{V_{gs1}} \right) \left( \frac{V_{gs1}}{V_{in}} \right)$$
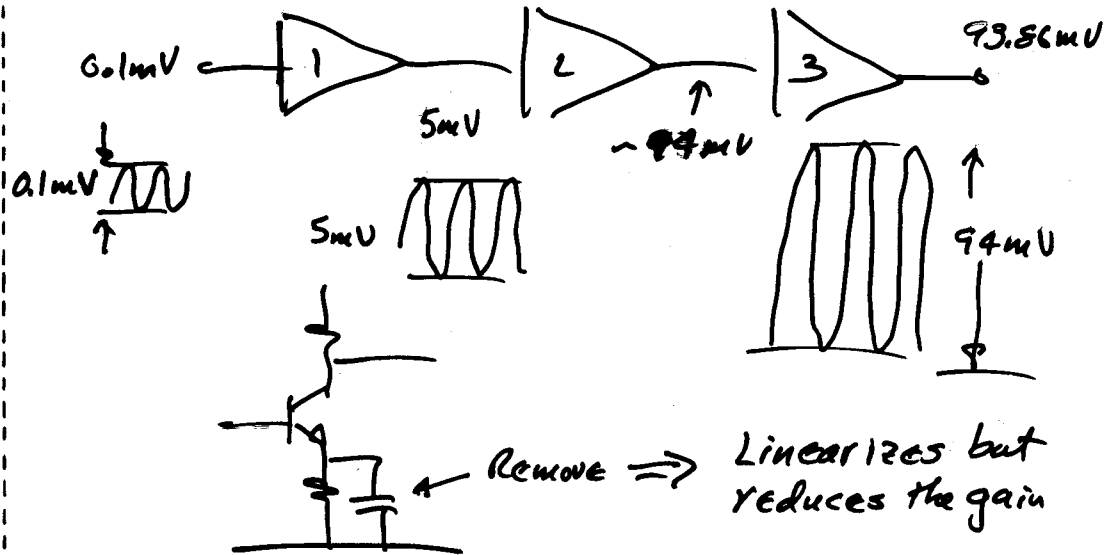
$$V_{in3(max)} = \frac{5mV}{(49.81)} = \underline{\underline{0.1mV}}$$



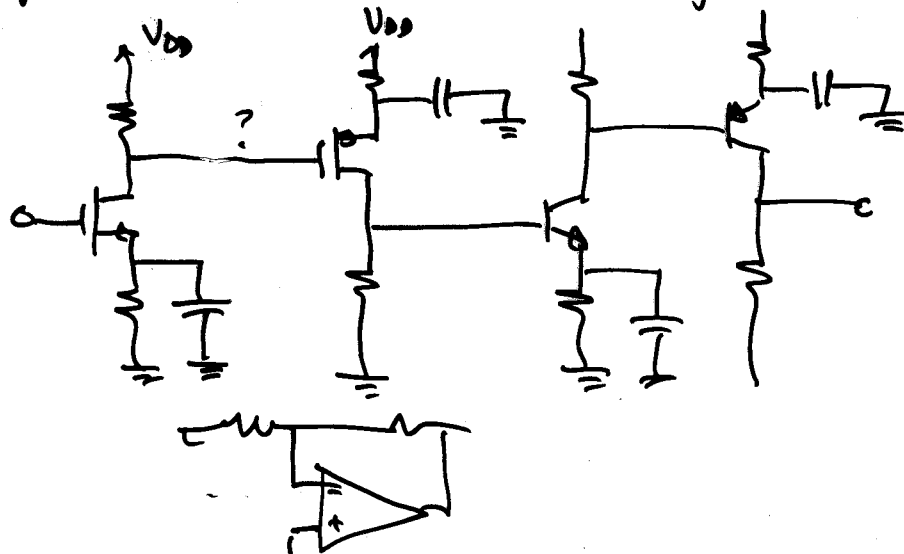
### Direct Coupled Amplifiers

Amplifiers that do not use coupling caps.



### Darlington Configuration

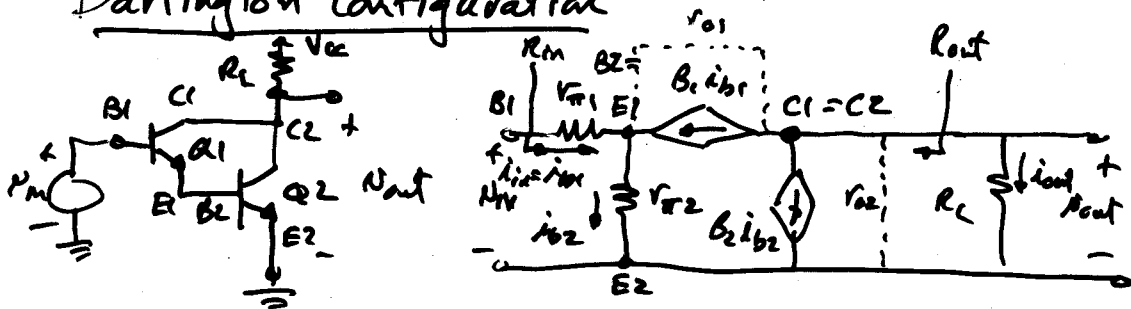

Find  $\frac{N_{out}}{N_{in}}$ ,  $R_{in}$  &  $R_{out}$  &  $\frac{i_{out}}{i_{in}}$

$R_{in} = r_{\pi 1} + (1 + \beta_1) r_{\pi 2}$        $R_{out} = \infty$  ( $r_{o2} = \infty$ )


$\frac{N_{out}}{N_{in}} = ?$        $\beta_1 i_{b1} + \beta_2 i_{b2} + \frac{N_{out}}{R_L} = 0$  }  $\beta_1 i_{b1} + \beta_2 (\beta_1 + 1) i_{b1} = -\frac{N_{out}}{R_L}$   
 Note that  $i_{b1} (1 + \beta_1) = i_{b2}$

$\frac{N_{out}}{i_{b1}} = -[\beta_1 + (1 + \beta_1) \beta_2] R_L$

$\frac{N_{out}}{N_{in}} = \left(\frac{N_{out}}{i_{b1}}\right) \left(\frac{i_{b1}}{N_{in}}\right) = \frac{-[\beta_1 + (1 + \beta_1) \beta_2] R_L}{r_{\pi 1} + (1 + \beta_1) r_{\pi 2}} \approx -\frac{(1 + \beta_1) \beta_2 R_L}{2 r_{\pi 1}}$


$\frac{i_{out}}{i_{in}} = \left(\frac{N_{out}}{R_L}\right) \left(\frac{R_{in}}{N_{in}}\right) = \frac{N_{out}}{N_{in}} \left(\frac{R_{in}}{R_L}\right) = -\frac{(1 + \beta_1) \beta_2 R_L}{R_{in}} \approx \frac{R_{in}}{R_L}$

Compare with CE:

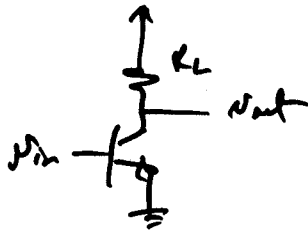

$\frac{N_{out}}{N_{in}} = \left(\frac{N_{out}}{i_b}\right) \left(\frac{i_b}{N_{in}}\right) = -\frac{\beta R_L}{r_{\pi}}$


Cascode Circuit -

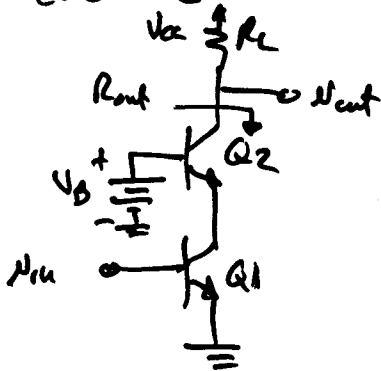

$\frac{N_{out}}{N_{in}} = -g_{m1} R_L = -\frac{\beta_1 R_L}{r_{\pi 1}}$

$R_{in} = r_{\pi 1}$

$R_{out} = r_{o1} \beta$

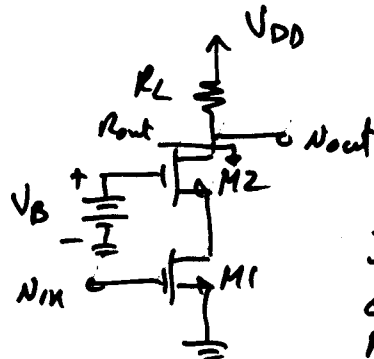

$-g_{m1} R_L$


$\infty$

$r_{o1} g_{m1} r_{o2}$

Increases the output resistance of a transistor above  $r_o$ .
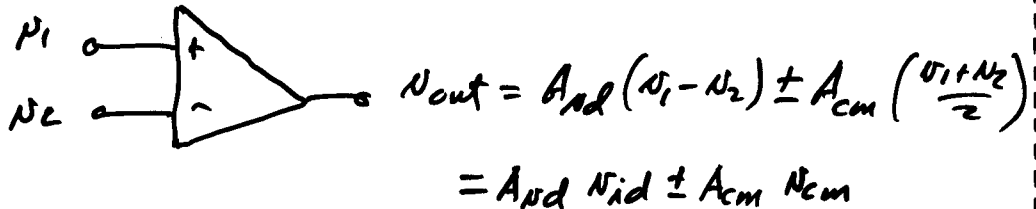
## Differential Amplifiers

Differential amplifiers are amplifiers that sense and amplify the difference between two voltages and reject the average of the voltages.



$$v_{out} = A_{diff}(v_1 - v_2) \pm A_{cm} \left( \frac{v_1 + v_2}{2} \right)$$

$$= A_{diff} v_{id} \pm A_{cm} v_{cm}$$

$$\therefore v_{id} \equiv v_1 - v_2 \quad \text{and} \quad v_{cm} \equiv \frac{v_1 + v_2}{2}$$

A "good" differential amplifier has  $|A_{diff}| \gg |A_{cm}|$ .