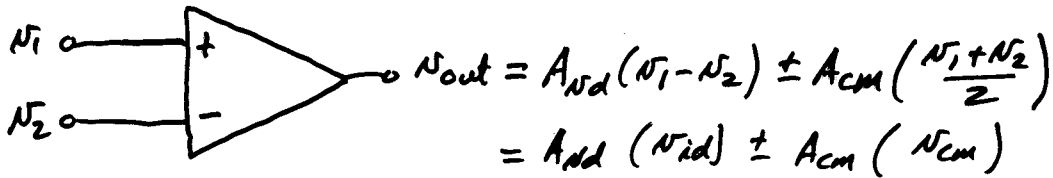


Differential Amplifiers



where, $V_{id} \equiv V_1 - V_2$ and $N_{cm} \equiv \frac{V_1 + V_2}{2}$

\uparrow Differential signal
 \uparrow Common (average) signal

A good differential amplifier rejects the average signal and amplifies the difference signal.


Note:

$$V_{id} = V_1 - V_2$$

$$2N_{cm} = V_1 + V_2$$

$$V_{id} + 2N_{cm} = 2V_1 \rightarrow V_1 = N_{cm} + \frac{V_{id}}{2}$$
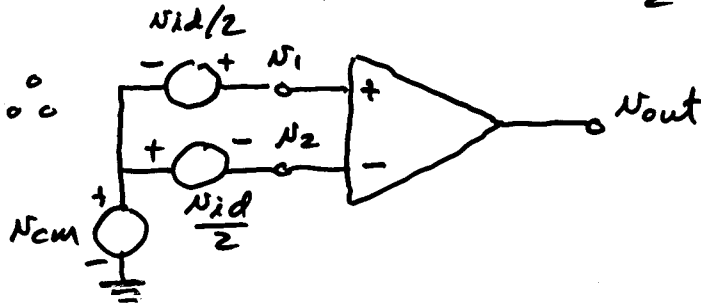
$$\text{Similarly, } V_2 = N_{cm} - \frac{V_{id}}{2}$$



Types of analysis:

1.) Differential mode ($N_{cm} = 0$)

2.) Common mode ($V_{id} = 0$)


Much easier than trying to do the whole analysis.

Common Mode Rejection Ratio (CMRR):


$$CMRR \equiv \frac{|A_{nd}|}{|A_{cm}|} \quad \text{Ideal} \rightarrow \infty$$

Differential Amplifier Circuits

BJT:

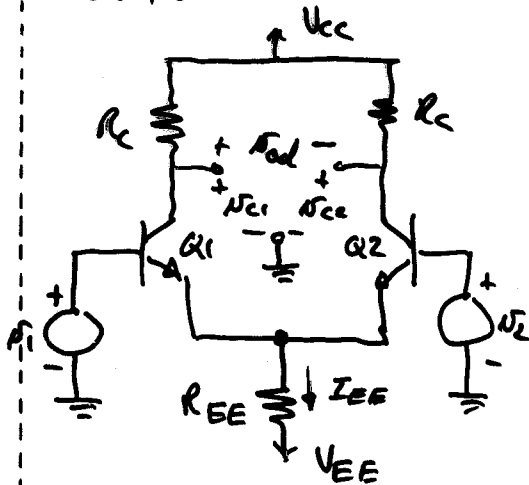

MOSFET:

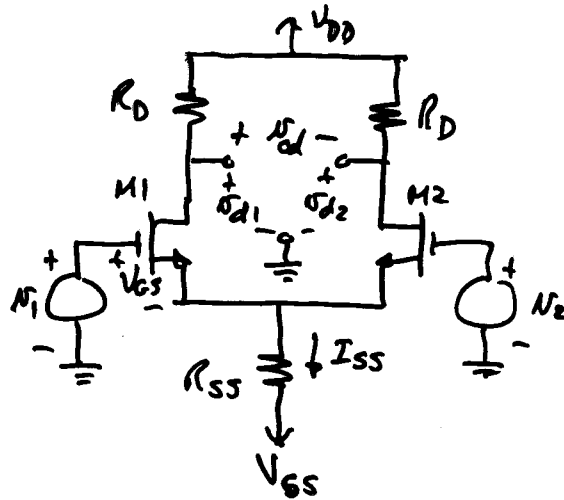DC Analysis (Assume $v_{d1} = v_{d2} = 0$)

$$I_{EE} = \frac{|V_{EE}| - V_{BE}}{R_{EE}}$$

$$I_{E1} = I_{E2} = \frac{I_{EE}}{2}$$

$$I_{C1} = I_{C2} = \alpha \frac{I_{EE}}{2}$$

Guessing V_{BE} gives
 I_{EE} .

$$I_{SS} = \frac{|V_{SS}| - V_{GS}}{R_{SS}}$$

$$I_{D1} = I_{D2} = \frac{I_{SS}}{2}$$

$$V_{DD} = 5, V_{SS} = -5V, R_{SS} = 10K, R_D = 10K$$

$$K_N = 1 \text{ mA/V}^2 \text{ \& } V_{TN} = 1V$$

$$|V_{SS}| = V_{GS} + I_{SS} R_{SS}$$

$$I_{SS} = 2I_D = 2 \frac{K_N}{2} (V_{GS} - V_T)^2$$

$$|V_{SS}| = V_{GS} + R_{SS} K_N (V_{GS} - V_T)^2$$

$$V_{GS}^2 - 1.9V_{GS} + 0.5 = 0$$




$$V_{GS} = 1.548V$$

$$\therefore I_{D5} = 171 \mu A$$

$$V_{DS} = 4.876V$$

\therefore saturated

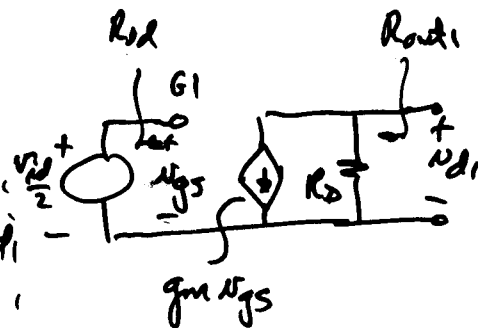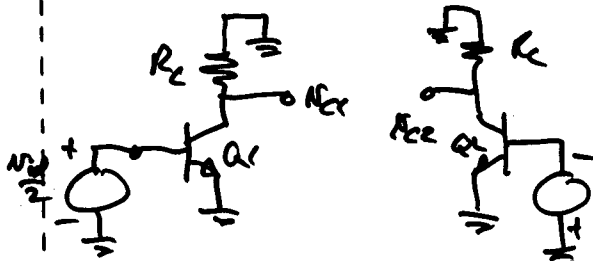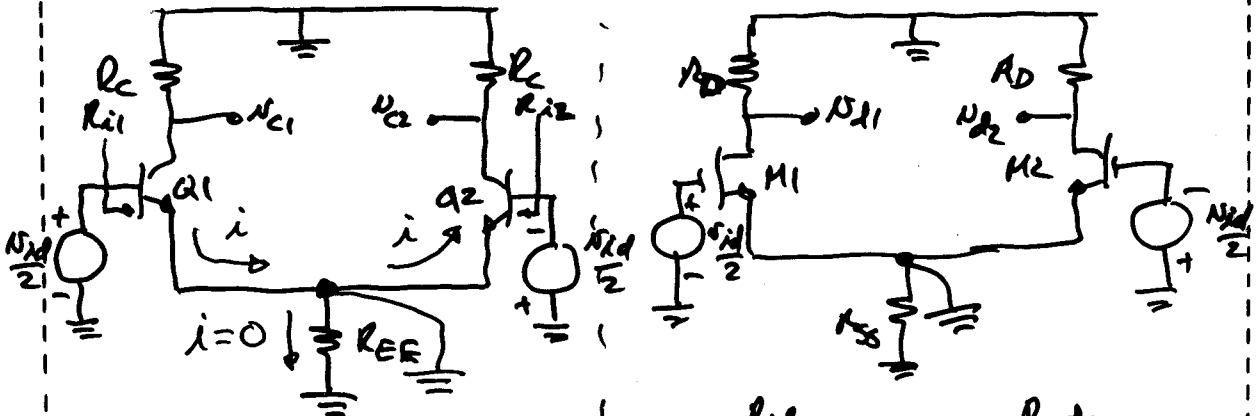Differential Mode Analysis (Small-signal)



$$\frac{N_{e1}}{N_{i1}} = -g_m R_c + \frac{N_{e1}}{N_{i2}} = -\frac{g_m R_c}{2}$$

$$\frac{N_{d1}}{N_{i2}} = \frac{1}{2} g_m R_D$$

$$R_{id1} = r_{\pi 1} \quad R_{id2} = r_{\pi 2}$$

$$R_{id1} = \infty \quad R_{out1} = R_D$$



$$R_{out1} = R_c \quad R_{out2} = R_c$$

$$R_{id} = \infty \quad R_{od} = 2R_D$$

$$R_{id} = 2r_{\pi}$$


$$R_{od} = 2R_c$$

Common Mode Analysis

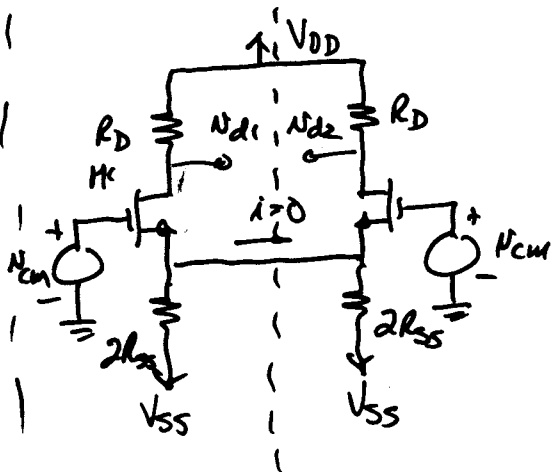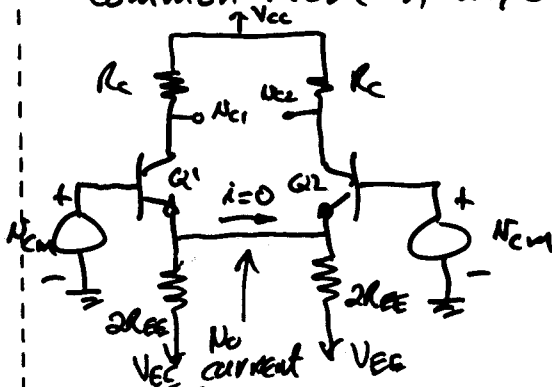


No current flows so you can "cut" the wire with no change.

Eq. ckt. for cm analysis:

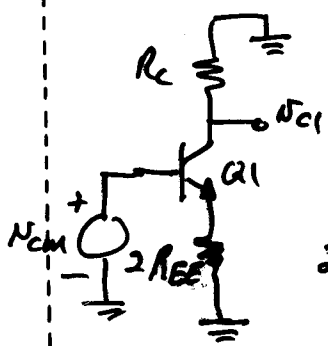

Analyze either one

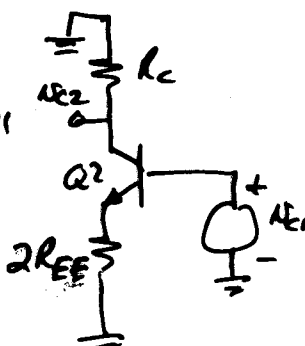

Analyze either one

Note: The cm analysis is essentially a common nothing circuit.