

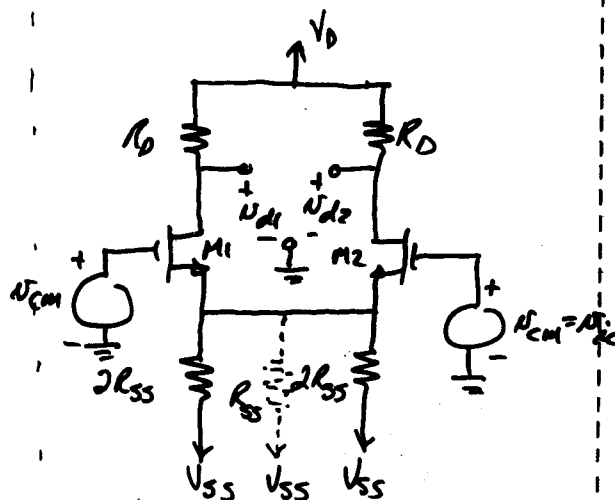
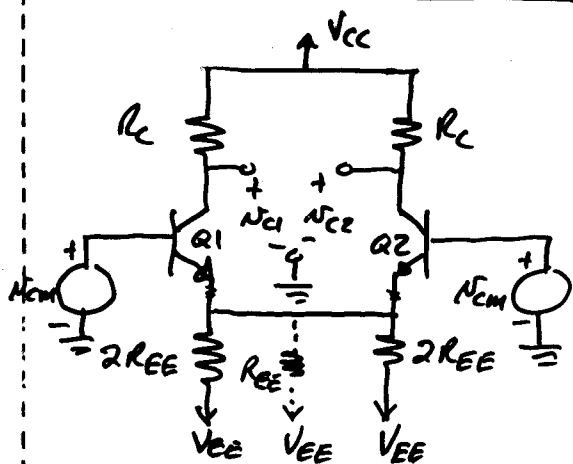


- Quiz #7 will cover differential amplifiers
- Dr. Sengupta will lecture on Friday (10/15)
- No quiz on 10/22 because of Fall break (10/18 & 10/19)
- As a result, there will be a quiz on 12/3 (last day of classes)



Common Mode Analysis

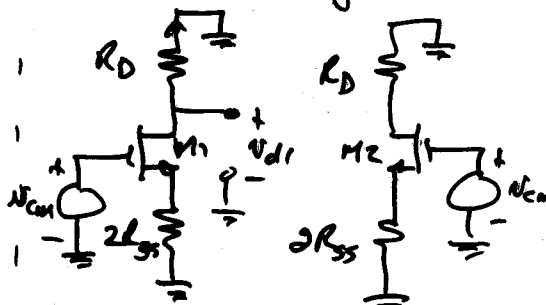

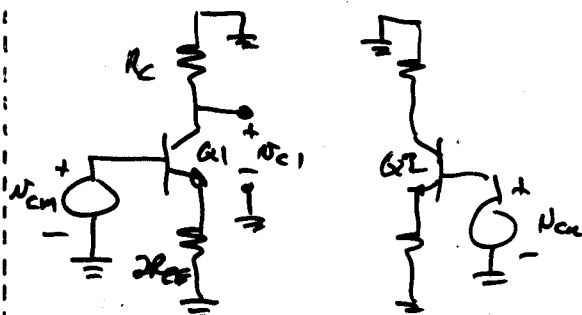Because no current flows in the wire between the emitters or collectors, we write the following:



S.S. model for the R.H. ckt -

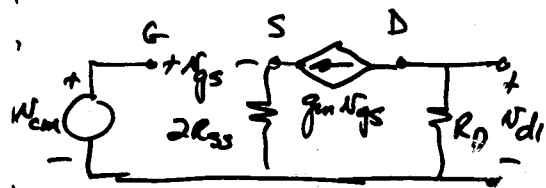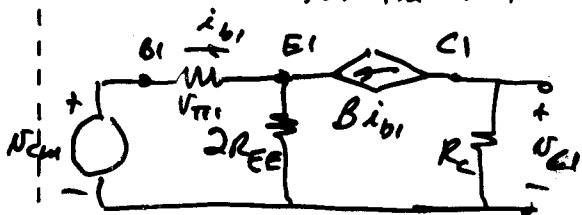

$$A_{cm} = \frac{V_{ce2}}{N_{cm}} = \frac{V_{ce1}}{N_{cm}} = \left(\frac{V_{ce1}}{i_{b1}} \right) \left(\frac{i_{b1}}{N_{cm}} \right) = \left(\frac{-\beta R_c}{r_{\pi 1} + (1+\beta)2R_{EE}} \right)$$

$$R_{oc} = R_c$$

$$R_{icm} = r_{\pi 1} + (1+\beta)2R_{EE}$$

$$\frac{V_{d1}}{N_{cm}} = \left(\frac{V_{d1}}{N_{gs}} \right) \left(\frac{N_{gs}}{N_{cm}} \right) = A_{cm}$$

$$N_{gs} = N_g - N_s = N_{cm} - g_m 2R_{SS} N_{gs}$$

$$\frac{V_{d1}}{N_{cm}} = (-g_m R_D) \left(\frac{1}{1 + 2g_m R_{SS}} \right)$$



CMRR (Common mode rejection ratio)

$$CMRR = \frac{|A_{od}|}{|A_{cm}|}$$



$$\beta = g_m r_{\pi}$$

$$\text{BJT: } CMRR = \frac{g_m R_C / 2}{\frac{\beta R_E}{r_{\pi} + (1+\beta)2R_{EE}}} = \frac{r_{\pi} + (1+\beta)2R_{EE}}{\beta/g_m = r_{\pi}} \approx \frac{(1+\beta)2R_{EE}}{r_{\pi}} \approx 2g_m R_{EE}$$


$$\text{FET: } CMRR = \frac{g_m R_D / 2}{\frac{g_m R_S}{1+g_m 2R_{SS}}} = \frac{1+g_m 2R_{SS}}{2} \approx g_m R_{SS}$$

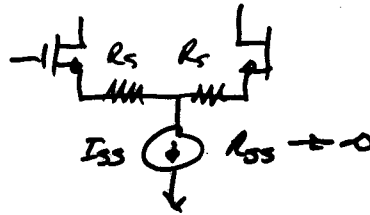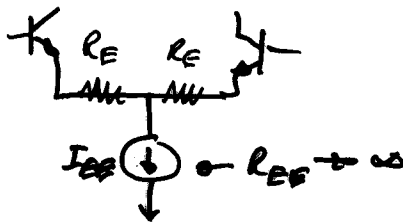

CHAPTER 17 - FREQUENCY RESPONSE

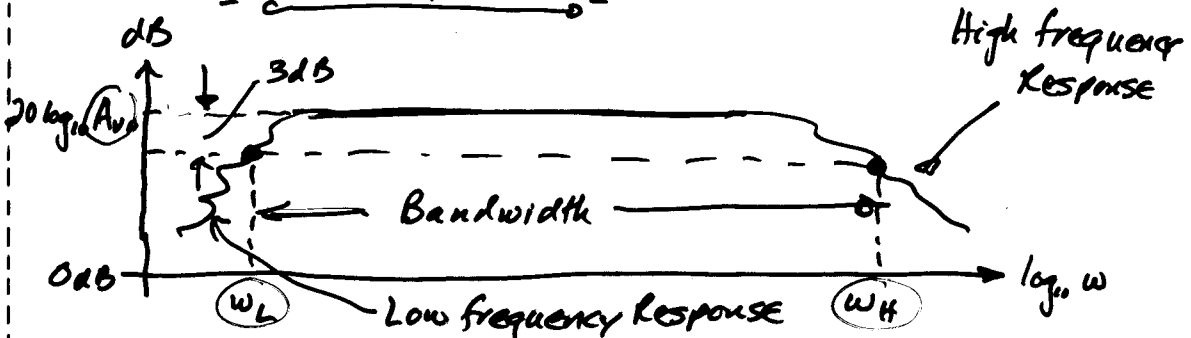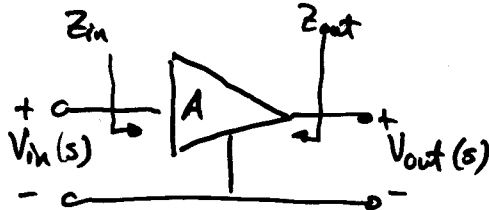

Complex Frequency Variable Perspective

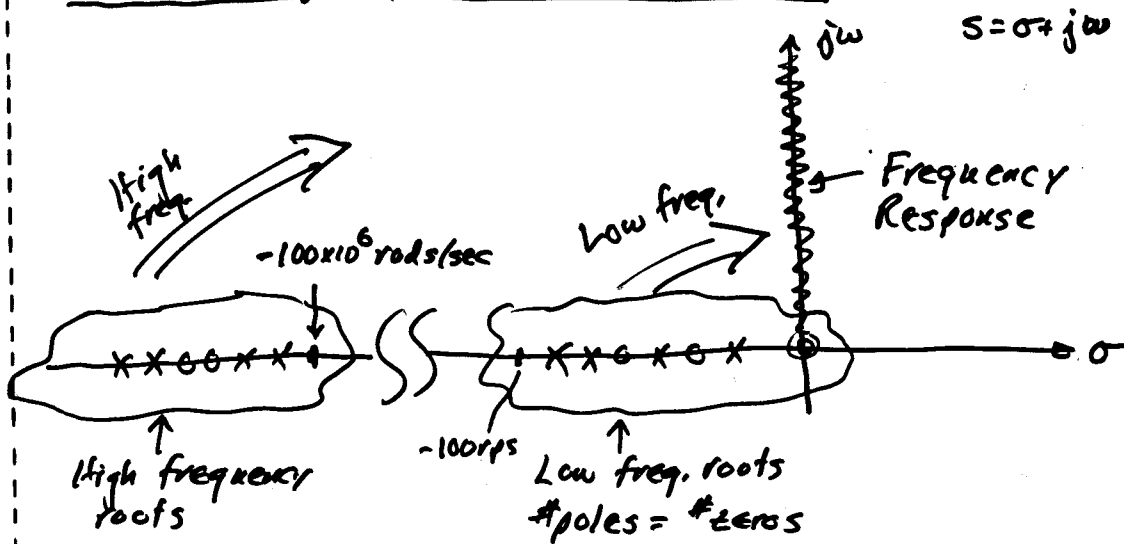

LOW FREQUENCY RESPONSE ANALYSIS


Goal: ω_L & A_0 (midband gain)

How do we find ω_L ?

- 1.) Direct analysis
- 2.) Approximation methods

a.) Dominant pole


$$\omega_L \approx \omega_p(\text{dominant}) \text{ if } |\omega_p(\text{dominant})| \geq 4 |\omega_p(\text{next})|$$

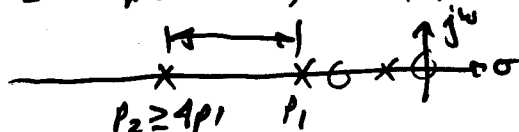

b.) No dominant pole

$$\omega_L \approx \sqrt{\sum_n p_n^2 - 2 \sum_j z_j^2}$$
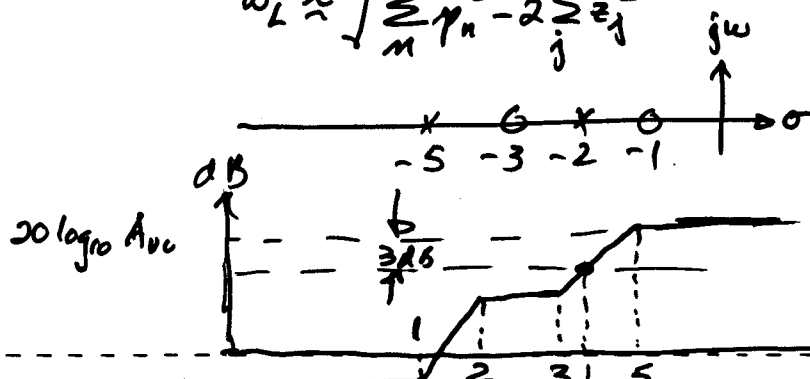
$$\omega_L = \sqrt{(5^2 + 3^2) - 2(2^2 + 1^2)} \approx \sqrt{9} = 3$$



c.) Bode plots

ω_L