

LOW FREQUENCY RESPONSE ANALYSIS


Quiz 7- Diff. Amps

Goal: Find ω_L (lower-3dB freq.) and A_0 (midband gain)

Methods for finding ω_L

- 1.) Direct analysis and numerically solve
- 2.) Approximation methods
 - a.) Dominant pole ($|w_p(\text{dominant})| \geq 4 |w_p(\text{next})|$)
 - b.) No dominant pole
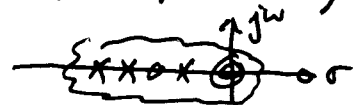
$$\omega_L \approx \sqrt{\sum_n P_n^2 - 2 \sum_j Z_j^2}$$




c.) Plot Bode plot and find ω_L

3.) Short-circuit time constant


$$\omega_L \approx \sum_{i=1}^n \frac{1}{R_{is} C_i}$$

R_{is} is the Thevenin resistance seen by C_i with all other capacitors shorted.

MOSFET LOW Frequency Example

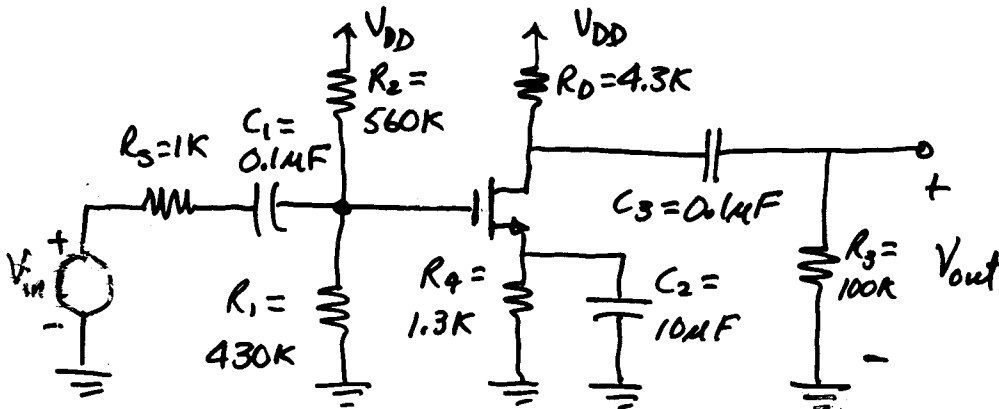

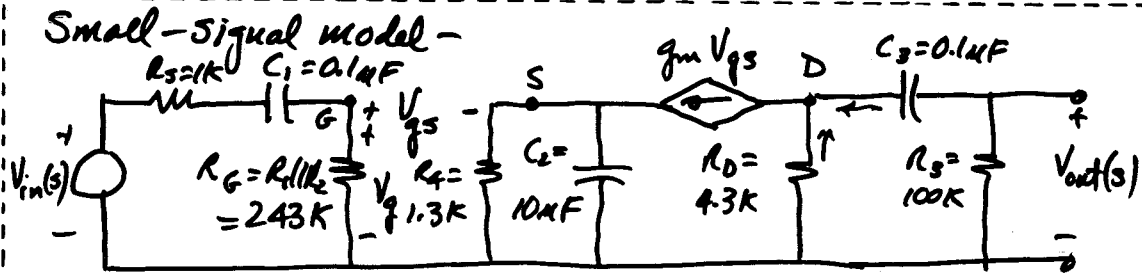Find ω_L if $g_m = 1.23\text{mS}$ and $r_o = \infty$ ($\lambda = 0$)



1.) Direct analysis

$$\frac{V_{out}}{V_{in}} = \left(\frac{V_{out}}{V_{gs}}\right) \left(\frac{V_{gs}}{V_g}\right) \left(\frac{V_g}{V_{in}}\right) \quad Z_c(s) = \frac{1}{sC}$$

$$V_{out}(s) = -g_m \left(\frac{R_D R_3}{R_D + R_3 + \frac{1}{sC_3}}\right) V_{gs} = \left(-g_m R_D R_3\right) \left(\frac{s}{s + \frac{1}{C_3(R_D + R_3)}}\right)$$

$$z_3 = 0 \quad p_3 = \frac{-1}{C_3(R_D + R_3)} = -959 \text{ rads/sec}$$

$$V_{gs} = V_g - V_s = +V_g - g_m V_{gs} \left(\frac{R_4}{R_4 + \frac{1}{sC_2}}\right) \approx V_g - \frac{g_m R_4 V_{gs}}{1 + sC_2 R_4}$$

$$V_{gs} \left[1 + \frac{g_m R_4}{sC_2 R_4 + 1}\right] = V_g \Rightarrow \frac{V_{gs}}{V_g} = \frac{sC_2 R_4 + 1}{sC_2 R_4 + 1 + g_m R_4}$$

$$\therefore \frac{V_{gs}}{V_g} = \frac{s + \frac{1}{R_4 C_2}}{s + \frac{1 + g_m R_4}{R_4 C_2}} \Rightarrow z_2 = -\frac{1}{R_4 C_2} = -76.9 \text{ rads/sec}$$

$$p_2 = -\frac{1 + g_m R_4}{R_4 C_2} = -200 \text{ rads/sec}$$

$$\frac{V_g}{V_{in}} = \frac{R_G}{R_G + R_3 + \frac{1}{sC_1}} = \left(\frac{R_G}{R_G + R_3}\right) \left(\frac{1}{1 + \frac{1}{sC_1(R_G + R_3)}}\right)$$


$$= \left(\frac{R_G}{R_G + R_3}\right) \left(\frac{s}{s + \frac{1}{C_1(R_G + R_3)}}\right) \Rightarrow z_1 = 0$$

$$p_1 = \frac{-1}{C_1(R_G + R_3)} = -41 \text{ rads/sec}$$

$$\frac{V_{out}(s)}{V_{in}(s)} = \left(-\frac{g_m R_D R_3}{R_D + R_3}\right) \left(\frac{R_G}{R_G + R_3}\right) \left[\left(\frac{s}{s + p_1}\right) \left(\frac{s + z_2}{s + p_2}\right) \left(\frac{s}{s + p_3}\right)\right]$$

↑
 Bypass
 Caps
 Coupling
 Caps


Summary-

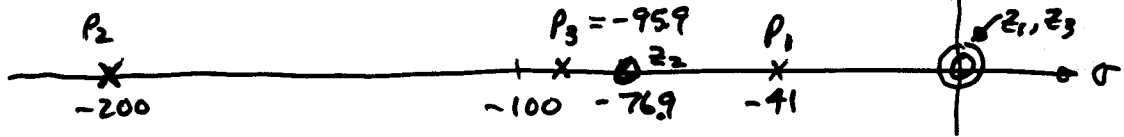


$$1.) \omega_L \approx \sqrt{(200)^2 + (75.9)^2 + (41)^2 - 2(76.9)^2} = 2\pi \cdot 31.5 \text{ Hz}$$

$$f_L = \underline{31.5 \text{ Hz}}$$

2.) Bode plot -

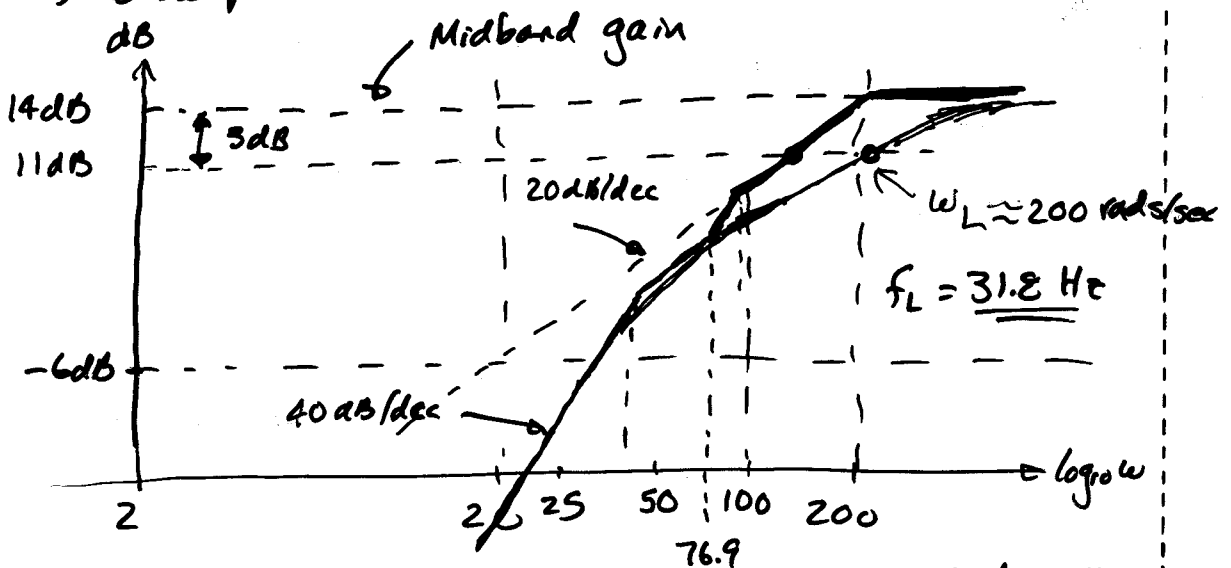

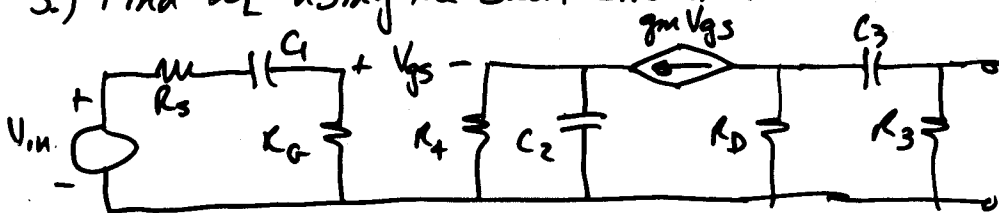3.) Find ω_L using the short-circuit time constant method.




$$C_1: R_{1S} = R_S + R_G = 244 \text{ k}$$

$$\frac{1}{C_1 R_{1S}} = \frac{1}{(0.1 \mu\text{F})(244 \text{ k})} = -41 \text{ rads/sec.}$$

$$C_2: R_{2S} = R_4 \parallel \frac{1}{g_m}$$
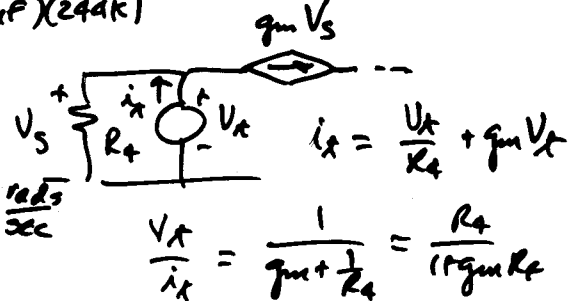
$$\frac{1}{C_2 R_{2S}} = \frac{1 + g_m R_4}{R_4 C_2} = 200 \frac{\text{rads}}{\text{sec}}$$



$$C_3: R_{3s} = R_0 + R_3$$

$$\frac{1}{C_3 R_{3s}} = \frac{1}{C_3 (R_0 + R_3)} = 95.9 \text{ rads/sec}$$


$$\omega_0 \quad \omega_L \approx \frac{1}{R_{1s} C_1} + \frac{1}{R_{2s} C_2} + \frac{1}{R_{3s} C_3} = 337 \text{ rads/sec}$$

$$f_L \approx 53.6 \text{ Hz}$$


(Not all approximation methods are that good.)

Now work the CG & CD configurations

CG

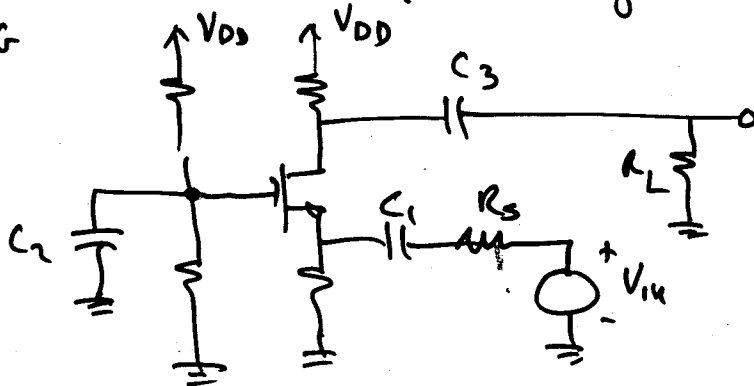

CD

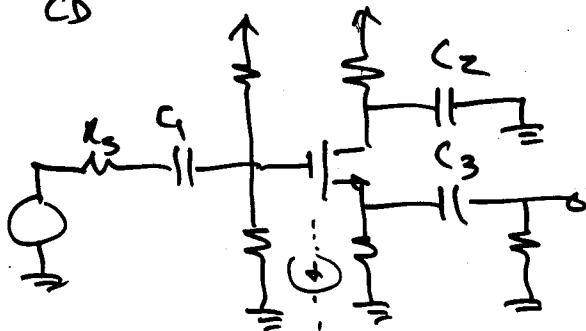

BJT Low Frequency Response

In the SC time constant method, if R_{is} does not depend on whether the other capacitors are shorted or not, then



$$\frac{1}{R_{is} C_i} = P_i$$

Problem 5 - (20 points - This problem is optional)

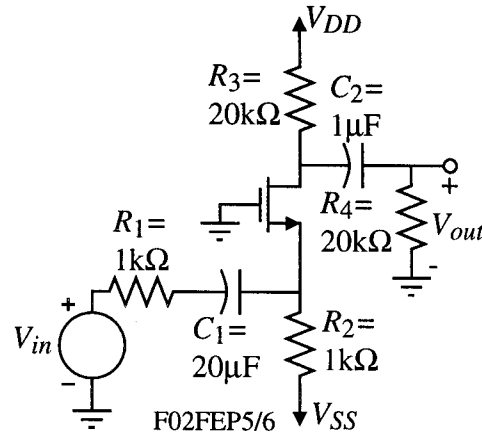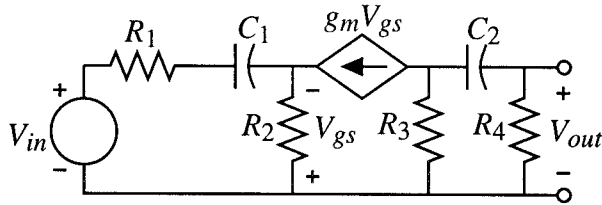- 1.) If $g_m = 2\text{mA/V}$, what is the midband voltage gain of the amplifier shown? Assume $r_d = \infty$.
- 2.) Find the lower -3dB frequency (f_L) of the amplifier shown.

Solution

The small signal model for this problem is:



$$\frac{V_{out}(s)}{V_{in}(s)} = \left(\frac{V_{out}}{V_{gs}} \right) \left(\frac{V_{gs}}{V_{in}} \right)$$

$$\therefore \frac{V_{out}}{V_{gs}} = \frac{-g_m R_3 R_4}{R_3 + R_4 + \frac{1}{sC_2}} = \left(\frac{-g_m R_3 R_4}{R_3 + R_4} \right) \left(\frac{s}{s + \frac{1}{C_2(R_3 + R_4)}} \right) = (-20) \left(\frac{s}{s + 25} \right)$$

Next, find V_{gs}/V_{in} :

$$\frac{V_{in} + V_{gs}}{R_1 + \frac{1}{sC_1}} + \frac{V_{gs}}{R_2} + g_m V_{gs} = 0 \rightarrow \frac{-V_{in}}{R_1 + \frac{1}{sC_1}} = V_{gs} \left(\frac{1}{R_1 + \frac{1}{sC_1}} + \frac{1}{R_2 \parallel (1/g_m)} \right)$$

or

$$-V_{in} \left(R_2 \parallel \frac{1}{g_m} \right) = V_{gs} \left(R_2 \parallel \frac{1}{g_m} + R_1 + \frac{1}{sC_1} \right) \rightarrow \frac{V_{gs}}{V_{in}} = \left(\frac{R_2 \parallel \frac{1}{g_m}}{R_1 + R_2 \parallel \frac{1}{g_m}} \right) \left(\frac{s}{s + \frac{1}{C_1 \left[R_1 + R_2 \parallel \frac{1}{g_m} \right]}} \right)$$

$$\frac{V_{gs}}{V_{in}} = \frac{-0.33}{1 + 0.33} \left(\frac{s}{s + 37.5} \right) = (-0.25) \left(\frac{s}{s + 37.5} \right)$$


$$\text{Thus, } \frac{V_{out}(s)}{V_{in}(s)} = 5 \left(\frac{s}{s + 25} \right) \left(\frac{s}{s + 37.5} \right)$$

$$\therefore \text{MBG} = 5, \omega_L \approx \sqrt{(25)^2 + (37.5)^2} = 45.07 \text{ rads/sec} \rightarrow f_L = 7.17 \text{ Hz}$$

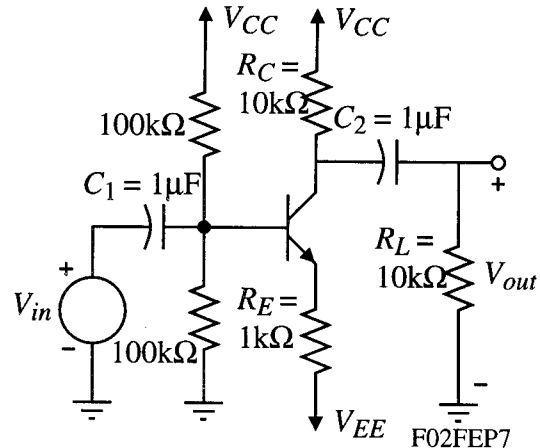Problem 7 - (20 points - This problem is optional).

A BJT amplifier is shown. Assume that the BJT has the small signal parameters of $g_m = 50\text{mA/V}$, $r_\pi = 2\text{k}\Omega$, and $r_o = \infty$.


- Find the midband voltage gain of this amplifier, V_{out}/V_{in} .
- Find the numerical value of all poles and zeros of the low frequency response.
- Find the value of the lower -3dB frequency, f_L , in Hz.



Solution

The low-frequency, small signal model for this problem is shown where $R_B = 50\text{k}\Omega$.

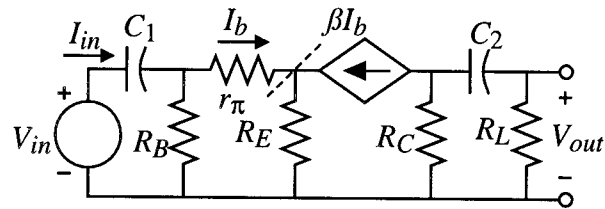The algebraic approach to this problem is:



$$\begin{aligned} \frac{V_{out}}{V_{in}} &= \left(\frac{V_{out}}{I_b} \right) \left(\frac{I_b}{I_{in}} \right) \left(\frac{I_{in}}{V_{in}} \right) = \left(\frac{-\beta R_L R_C}{R_C + R_L + \frac{1}{sC_2}} \right) \left(\frac{R_B}{R_B + r_\pi + (1+\beta)R_E} \right) \left(\frac{1}{\frac{1}{sC_1} + R_B \parallel [r_\pi + (1+\beta)R_E]} \right) \\ &= \left(\frac{-\beta R_L R_C}{(R_C + R_L)[r_\pi + (1+\beta)R_E]} \right) \left(\frac{s}{s + \frac{1}{C_2(R_C + R_L)}} \right) \left(\frac{s}{s + \frac{1}{C_1(R_B \parallel [r_\pi + (1+\beta)R_E])}} \right) \\ &= \frac{-100 \cdot 10\text{K} \cdot 10\text{K}}{20\text{K} \cdot 103\text{K}} \left(\frac{s}{s+50} \right) \left(\frac{s}{s+29.7} \right) = -4.854 \left(\frac{s}{s+50} \right) \left(\frac{s}{s+29.7} \right) \end{aligned}$$

The midband gain is $\boxed{MBG = 4.854 \text{ V/V}}$

$$\therefore \omega_L \approx \sqrt{(29.7)^2 + (50)^2} = 58.2 \text{ rads/sec.} \rightarrow \boxed{f_L = 9.26\text{Hz}}$$

The poles and zeros are,

$\boxed{\text{Two zeros at } s = 0, \text{ a pole at } s = -29.7 \text{ rads/sec. and a pole at } s = -50 \text{ rads/sec.}}$