

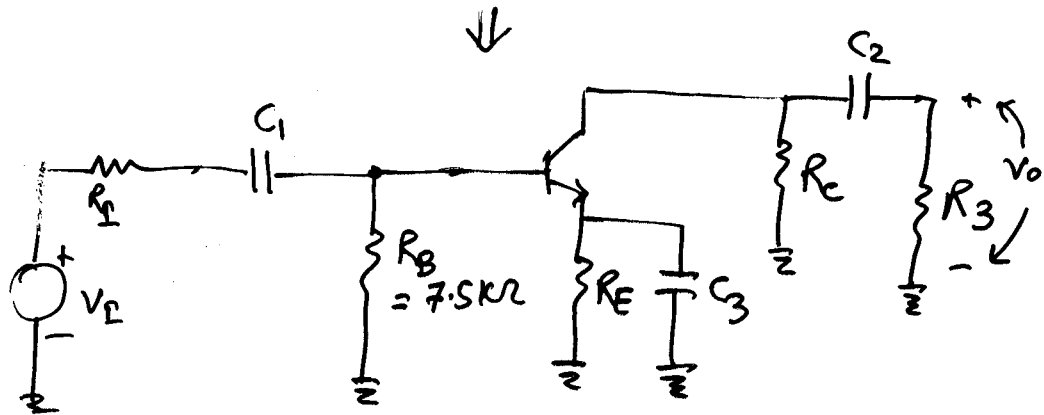


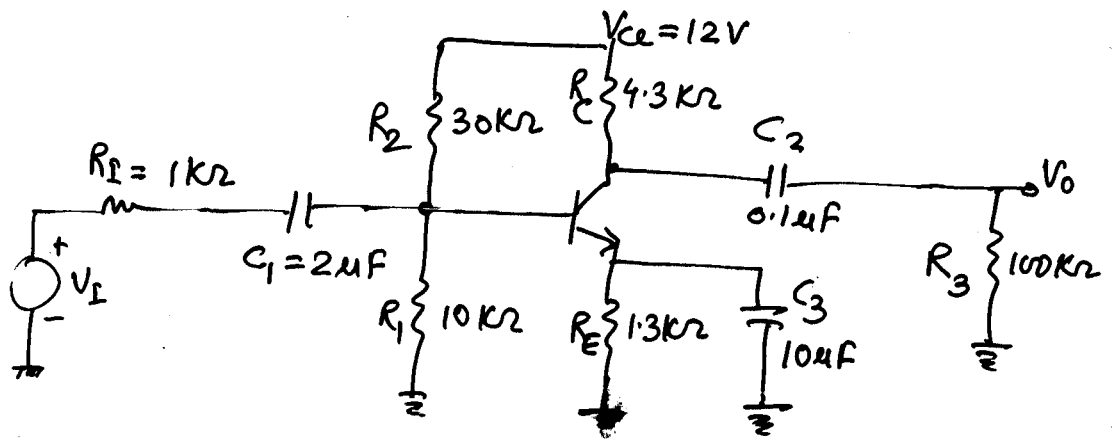Estimate of ω_L for the CE amplifier (Fig 17.6)




R_{is} (Resistance seen by C_1)

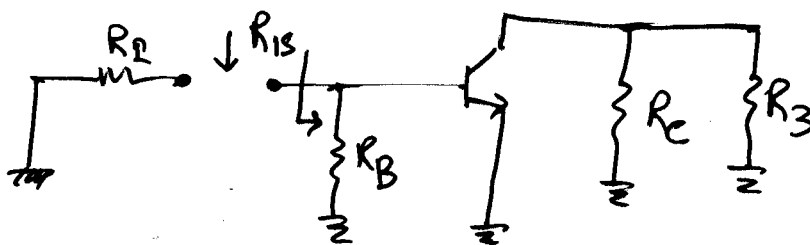

$I_C = 1.73 \text{ mA}$
 $V_{CE} = 2.32 \text{ V}$
 $\beta_0 = 100$
 $V_A = 75 \text{ V}$
 $r_{\pi} = 1.45 \text{ k}\Omega$
 $r_o = 44.7 \text{ k}\Omega$


$$R_{is} = R_I + (R_B \parallel r_{\pi}) = 1000 + (7500 \parallel 1450) = 2.22 \text{ k}\Omega$$
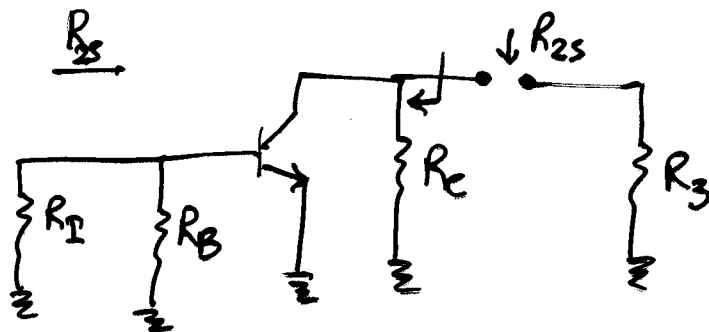
$$\frac{1}{R_{is} \cdot C_1} = \frac{1}{(2.22 \text{ k}\Omega)(2 \mu\text{F})} = 225 \text{ rad/sec}$$



$$R_{2s} = (R_C \parallel r_o) + R_L = (4.3 \text{ k}\Omega \parallel 44.7 \text{ k}\Omega) + 100 \text{ k}\Omega = 104 \text{ k}\Omega.$$
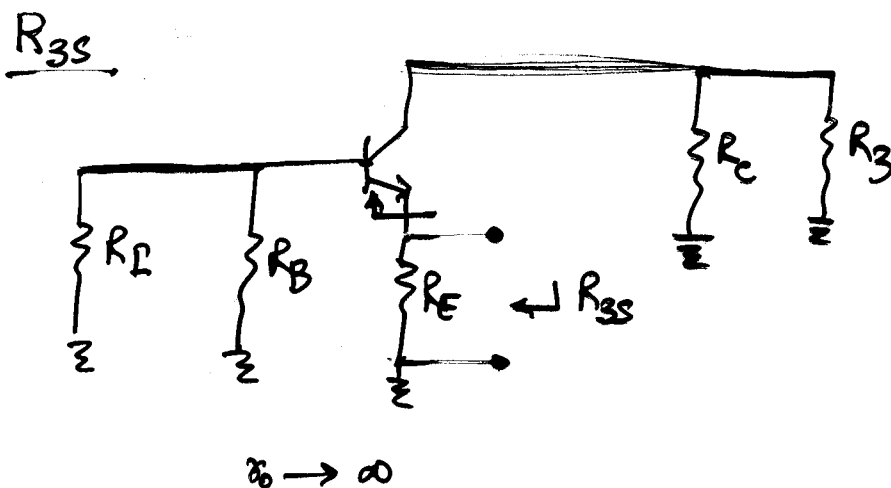
$$\frac{1}{R_{2s} \cdot C_2} = \frac{1}{(104 \text{ k}\Omega)(0.1 \mu\text{F})} = 96.1 \text{ rad/sec}$$



$$R_{3s} = \left[R_E \parallel \frac{\{r_{\pi} + (R_1 \parallel R_B)\}}{(\beta_0 + 1)} \right] = 22.7 \Omega$$

$$\frac{1}{R_{3s} C_3} = 4410 \text{ rad/sec}$$

$$\omega_L = \sum_{i=1}^3 \frac{1}{R_i C_i}$$

$$\omega_L = 225 + 96.1 + 4410$$

$$= 4730 \text{ rad/sec}$$

$$f_L = \frac{\omega_L}{2\pi} = 753 \text{ Hz.}$$