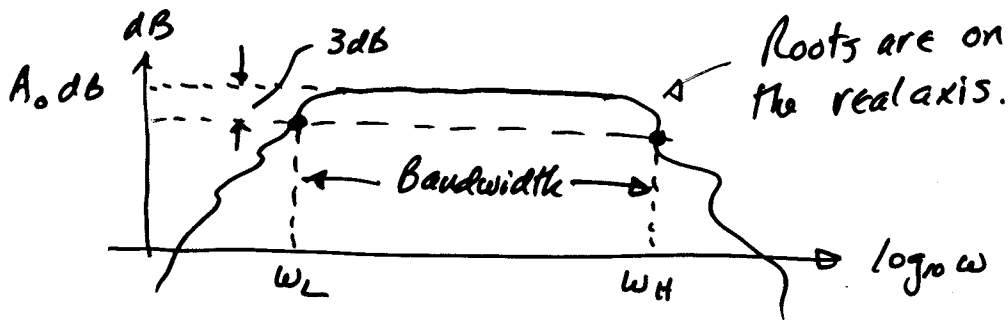


## High Frequency Response



## Methods of Finding $\omega_H$

1.) Given the roots ( $\frac{1}{s + p_i}$ )

a.) Bode plot

b.) Dominant pole

$$\omega_H \approx \omega_p(\text{dominant}) \text{ if } \omega_p(\text{dominant}) \leq \frac{\omega_p(\text{next})}{4}$$


c.)

$$\omega_H \approx \frac{1}{\sqrt{\sum_n \frac{1}{\omega_{pn}^2} - 2 \sum_n \frac{1}{\omega_{zn}^2}}} \approx \frac{1}{\sqrt{\frac{1}{\omega_{p1}^2} + \frac{1}{\omega_{p2}^2} + \dots}}$$

d.) Exact solution (quadratic)

2.) Roots not known

a.) Miller effect

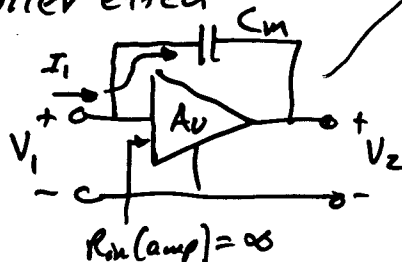

$$Z_1 = \frac{V_1}{I_1} = \frac{V_1}{\frac{V_1 - V_2}{s C_m}} \text{ Ceq.}$$

$$Z_1 = \frac{V_1}{s C_m (V_1 - V_2)} = \frac{1}{s C_m (1 + \frac{V_2}{V_1})}$$

But  $\frac{V_2}{V_1} = A_v$ , so  $Z_1 = \frac{1}{s C_m (1 - A_v)}$

If  $A_v$  is negative, then  $Z_1 = \frac{1}{s C_m (1 + |A_v|)} = \frac{1}{s C_{eq}}$

**$C_{eq} = (1 + |A_v|) C_m$**

b.) Approximate solution for a quadratic (p. 1311)

$$s^2 + as + b = (s + p_1)(s + p_2) = s^2 + s(p_1 + p_2) + p_1 p_2$$

Assume  $p_1 < p_2$



$$s^2 + as + b \approx s^2 + p_2 s + p_1 p_2 \Rightarrow \underline{p_2 = -a} \quad \underline{p_1 = \frac{b}{a}}$$

c.) Open-circuit Time Constant

$$\omega_H \approx \frac{1}{\sum_{i=1}^m R_{i0} C_i}$$


where  $R_{i0}$  is the Thevenin resistance seen from  $C_i$  with all other caps open-circuited.

Where does the high frequency response come from?


Coupling caps and bypass caps are shorts.

Ans. Transistor parasitics and other parasitics.

BJT High Frequency Model -

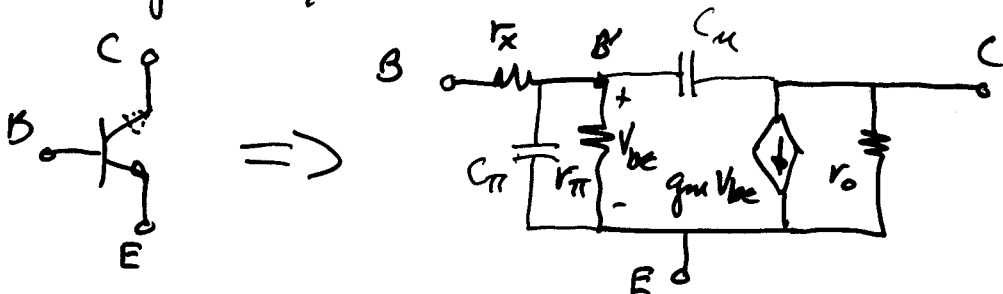


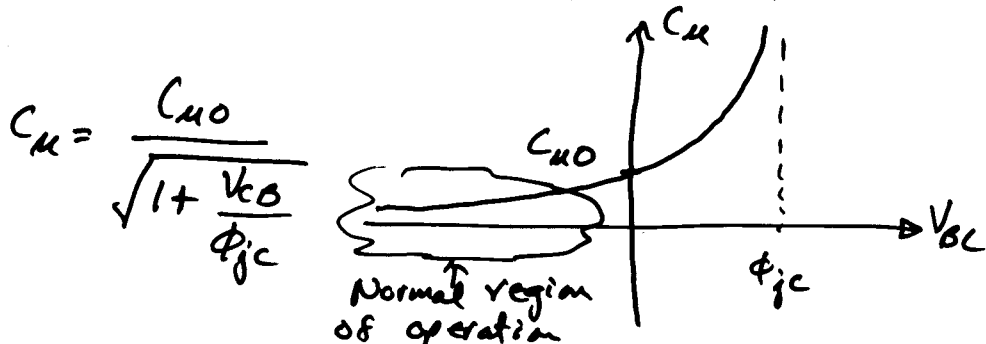$C_{\mu}$  = the reverse-biased BC junction capacitance



$$C_{\mu} = \frac{C_{\mu 0}}{\sqrt{1 + \frac{V_{CB}}{\phi_{jc}}}}$$

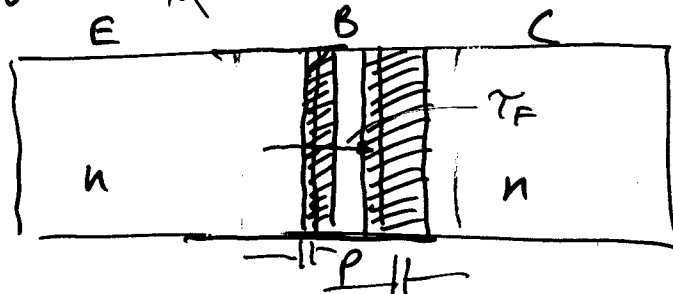
$C_T = g_m \tau_F + C_{jbe}$  where  $\tau_F$  = forward time constant



Unity-Gain Bandwidth  $C_M$

$\omega_T (f_T)$


CE configuration at high frequencies -

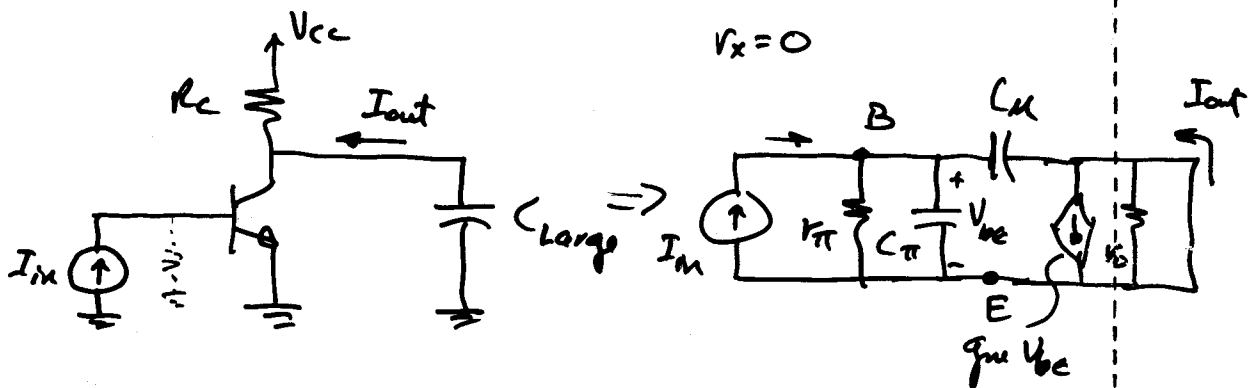

$$\frac{I_{out}}{I_{in}} = \left( \frac{I_{out}}{V_{be}} \right) \left( \frac{V_{be}}{I_{in}} \right) = (g_m) \left( \frac{V_{be}}{I_{in}} \right)$$

$$V_{be} = I_{in} \frac{1}{g_{\pi} + sC_{\pi} + sC_{\mu}}$$
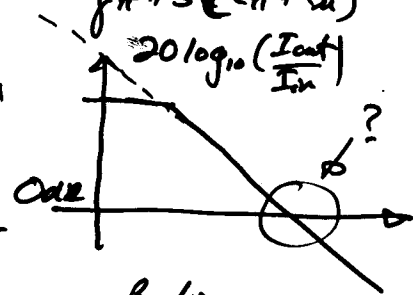
$$\frac{I_{out}}{I_{in}} = \frac{g_m r_{\pi}}{1 + s(C_{\pi} + C_{\mu})r_{\pi}} = \frac{\beta_0}{1 + s(C_{\pi} + C_{\mu})r_{\pi}}$$



$$\frac{I_{out}}{I_{in}} \approx \frac{\beta_0}{s(C_{\pi} + C_{\mu})r_{\pi}} = 1 \rightarrow \omega_T = \frac{\beta_0 / r_{\pi}}{(C_{\pi} + C_{\mu})} = \frac{g_m}{C_{\pi} + C_{\mu}}$$

$$\boxed{\omega_T = \frac{g_m}{C_{\pi} + C_{\mu}}}$$

$$\begin{aligned} C_{\pi} + C_{\mu} &= \frac{g_m}{\omega_T} \\ C_{\pi} &= \frac{g_m}{\omega_T} - C_{\mu} \end{aligned} \quad \omega_T \approx \frac{1}{\tau_F}$$

Typically  $C_{\pi} \gg C_{\mu}$

$r_x$ :  $r_x$  is a small resistance in series with base of about 100-500  $\Omega$ . It varies with  $I_c$  and is called "the base spreading resistance."

MOSFET High Frequency Model

