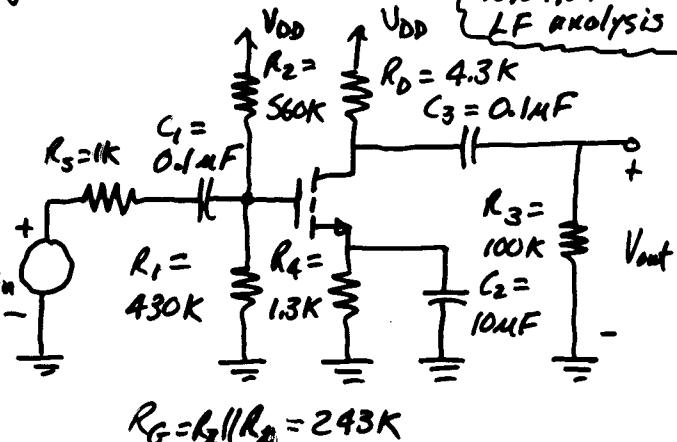


MOSFET Example of High Frequency Analysis

Quiz 8
10/29/04
HF analysis

Find w_H of the MOSFET amplifier shown if $g_m = 1.23 \text{ mS}$,

$C_{gs} = 10 \text{ pF}$, and $C_{gd} = 2 \text{ pF}$.
Note: This is the same circuit used for LF analysis (see p. 2 of 10/13/04 lecture)




$$R_G = R_2 // R_4 = 243 \text{ k}\Omega$$

$$X_C = \frac{1}{\omega C}$$

(1) Direct Analysis

Small-signal model:

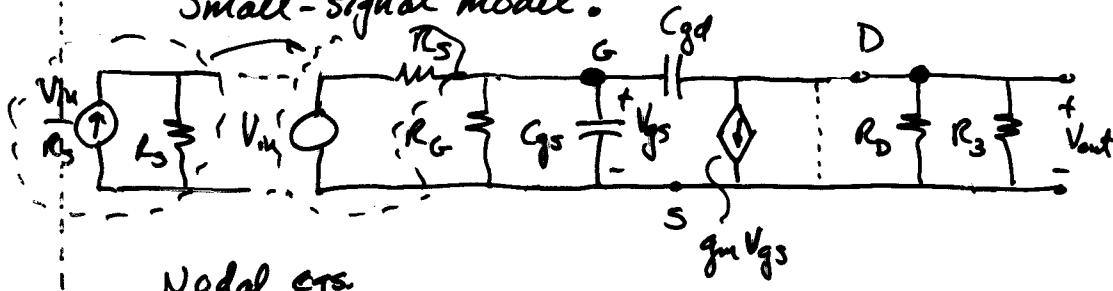

Nodal eqs.

$$\left(\frac{1}{R_s} + \frac{1}{R_G} + s(C_{gs} + sC_{gd}) \right) V_{gs} - sC_{gd} V_{out} = \frac{V_m}{R_s}$$

$$\frac{1}{R_s} = G_s \quad sC_{gd} (V_{out} - V_{gs}) + g_m V_{gs} + \left(\frac{1}{R_D} + \frac{1}{R_3} \right) V_{out} = 0$$


Two pages later

$$\frac{V_{out}}{V_m} = \frac{-G_s (g_m - sG_d)}{(G_s + G_d)(G_0 + G_3) + s[G_s(G_0 + G_3) + G_{ds}(G_0 + G_3 + G_5 + G_6) + g_m G_d]}$$

Substituting the values:

$$\frac{V_{out}(s)}{V_m(s)} = \frac{-10^{-3} (1.23 \times 10^{-3} - s 2 \text{ pF})}{20 \times 10^{-24} [s^2 + 3.628 \times 10^5 s + 1.165 \times 10^{16}]} + s^2 G_d C_{gs}$$


$$\rho_1 = -0.358 \times 10^8 \frac{\text{rad}}{\text{sec}} \quad \rho_2 = -3.272 \times 10^8 \frac{\text{rad}}{\text{sec}}$$

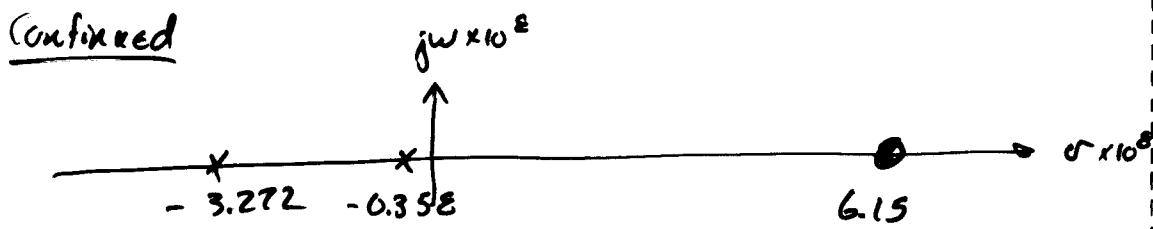(continued)

a.) Dominant pole


$$\omega_H \approx |\text{dominant pole}| \approx 0.358 \times 10^8 \frac{\text{rads}}{\text{sec}} \Rightarrow f_H = 5.67 \text{ MHz}$$

b.) Bode plot

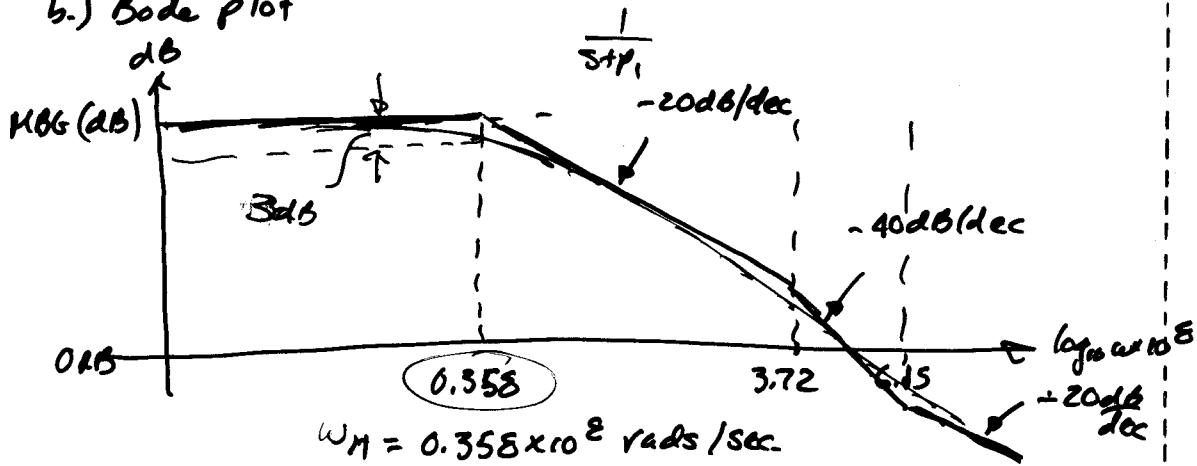

$$\omega_H = 0.358 \times 10^8 \text{ rads/sec.}$$


(2) Miller approach

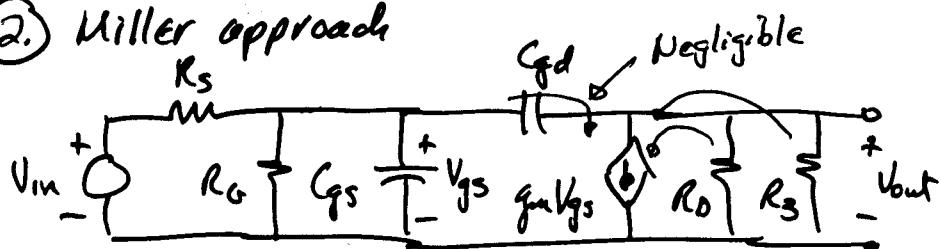

$$K = \frac{V_{out}}{V_{gs}} = ? \quad (\text{eq.} = C_{gd}(1-K))$$

$$V_{out} \approx -g_m(K_D || R_3) V_{gs} \quad \text{if} \quad \frac{1}{\omega_H C_{gd}} > R_D || R_3$$

$$(\text{eq.} = C_{gd}[1 + g_m(K_D || R_3)])$$

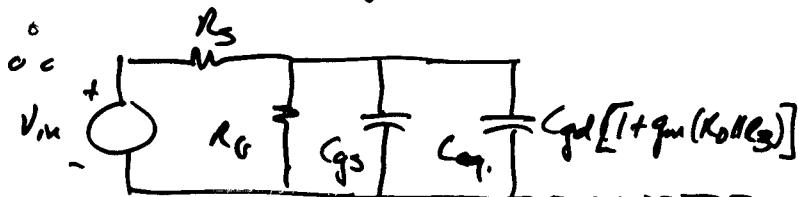


$$\omega_H \approx \frac{1}{[R_s || R_G][C_{gs} + C_{eq.}]} = \frac{1}{(0.996k)[0.9F + 2.4F \cdot 6]} = 45.3 \times 10^6 \frac{\text{rads}}{\text{sec}}$$

Cont'd

$$\frac{\omega_H}{2\pi} = f_H = 7.22 \text{ MHz} \quad \frac{1}{\omega_H C_{gd}} = \frac{1}{45.3 \times 10^6 \cdot 2 \mu F} = 11.037 \times 10^3$$


$$R_D \parallel R_3 \approx 4 \text{ k} \quad \frac{1}{\omega_H C_{gd}} > 4 \text{ k}$$

③ Open-Circuit Time Constant

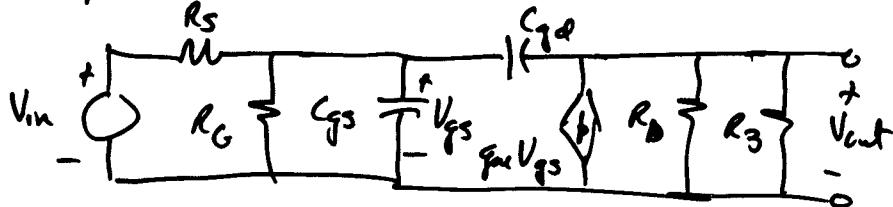

$$\omega_H = \frac{1}{\sum R_{LO} C_x}$$

$$C_{gs}: \quad R_{Cgs0} = R_G \parallel R_s \rightarrow R_{Cgs0} C_{gs} = 0.996 \text{ k} \times 2 \mu F$$

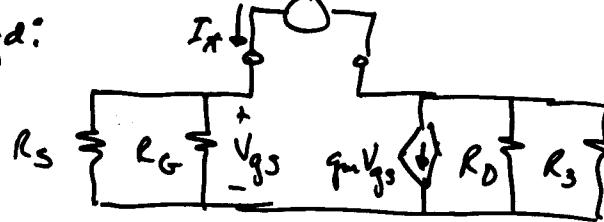C_{gd}:g_m(R_D||R₃) ↘

$$V_A = \underbrace{I_x (R_s \parallel R_G)}_{V_{gs}} + \underbrace{(I_x + g_m V_{gs})(R_D \parallel R_3)}_{I_A} = I_x \left\{ R_0 \parallel R_3 + R_s \parallel R_G [1 + g_m (R_D \parallel R_3)] \right\}$$

$$R_{Cgdo} = \frac{V_A}{I_A} = R_0 \parallel R_3 + R_s \parallel R_G [1 + g_m (R_D \parallel R_3)]$$

$$= 4.122 \text{ k} + 0.996 \text{ k} [1 + 5] = 10.16 \text{ k}$$


$$\omega_H \propto \frac{1}{R_{Cgs0} C_{gs} + R_{Cgdo} C_{gd}} = \frac{1}{(0.996 \text{ k})(2 \mu F) + (10.16 \text{ k})(2 \mu F)}$$

$$= 33.33 \times 10^6 \frac{\text{rads}}{\text{sec}} \rightarrow f_H = \underline{\underline{5.3 \text{ MHz}}}$$

There will be 2 examples of HF analysis on web site


BJT HF Analysis

generic ckt.

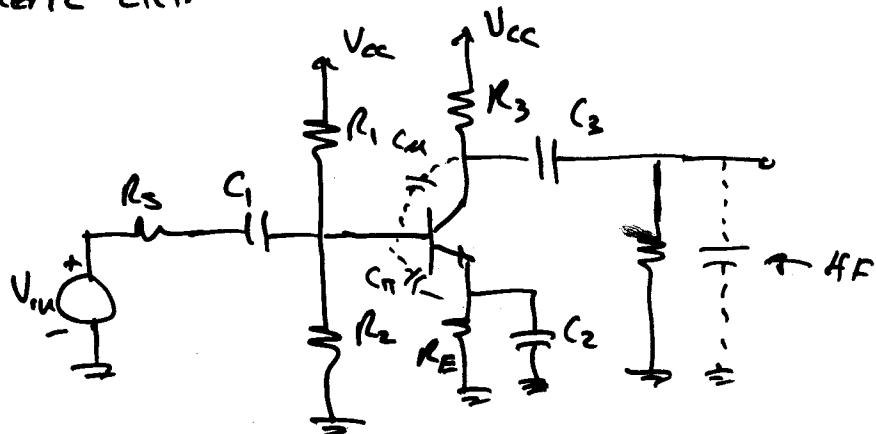

Given: g_{m1} , v_{π} , C_A & C_B

HF SS model-


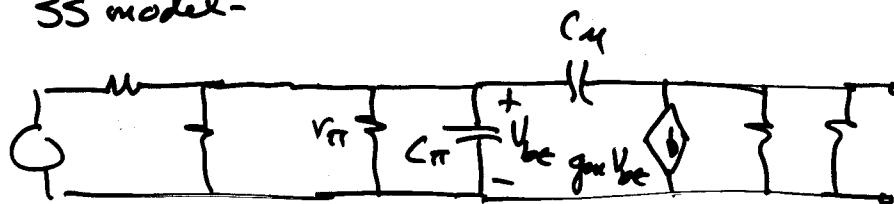


Problem 6 - (20 points - This problem is optional)

The FET in the amplifier shown has $g_m = 1\text{mA/V}$, $r_d = \infty$, $C_{gd} = 0.5\text{pF}$, and $C_{gs} = 10\text{pF}$.
 (a.) Find the midband gain, V_{out}/V_{in} . (b.) Find the upper -3dB frequency, f_H , in Hz. (Note: You cannot use the Miller's theorem on this problem because there is no bridging capacitor.)

Solution

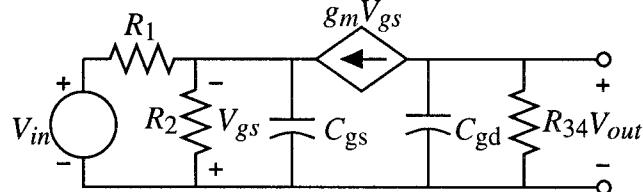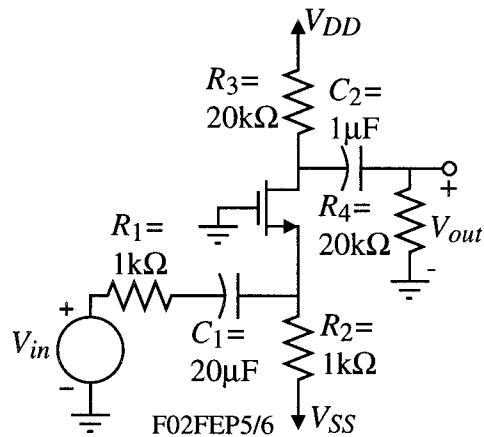The small signal model for the high frequency range is shown where $R_{34} = R_3 \parallel R_4 = 10\text{k}\Omega$.



Because the capacitors are independent, probably the best way to work this problem is by superposition (open-circuit time constants). Therefore,

C_{gs} :

$$R_{Cgs} = R_1 \parallel R_2 \parallel (1/g_m) = 1\text{k} \parallel 1\text{k} \parallel 1\text{k} = 333\Omega \rightarrow \omega_{Cgs} = \frac{1}{C_{gs} \cdot 333\Omega} = 300 \text{ Mrads/sec.}$$

C_{gd} :

$$R_{Cgd} = R_{34} = 10\text{k}\Omega \rightarrow \omega_{Cgd} = \frac{1}{C_{gd} \cdot 10\text{k}\Omega} = 200 \text{ Mrads/sec.}$$

$$\therefore \omega_H \approx \frac{1}{\sqrt{\left(\frac{1}{300\text{Mrads/sec}}\right)^2 + \left(\frac{1}{200\text{Mrads/sec}}\right)^2}} = 166 \text{ Mrads/sec.}$$

$$f_L = 26.48 \text{ MHz}$$

The midband gain is given as

$$\text{MBG} = \left(\frac{R_2 \parallel \frac{1}{g_m}}{R_1 + R_2 \parallel \frac{1}{g_m}} \right) \left(\frac{-g_m R_3 R_4}{R_3 + R_4} \right) = \left(\frac{-0.5}{1.5} \right) (-10) = 3.33 \text{ V/V}$$

Problem 8 – (20 points, this problem is optional)

A common-emitter BJT amplifier is shown. Assume that the BJT has a $\beta = h_{fe} = 100$, $C_\mu = 2\text{pF}$, $V_t = 25\text{mV}$, $f_T = 500\text{MHz}$, $r_b = 0\Omega$, and $r_o = \infty$.


- Find the numerical values of r_π , g_m , and C_π .
- If $r_\pi = 1\text{k}\Omega$, $g_m = 0.01\text{A/V}$ and $C_\pi = 10\text{pF}$ for the above amplifier, find the value of the upper -3dB frequency, f_H , in Hz.

Solution

$$\text{a.) } g_m = \frac{I_C}{V_T} = \frac{1\text{mA}}{25\text{mV}} = 0.04 \text{ A/V}$$


$$r_\pi = \frac{\beta_0}{g_m} = \frac{100}{0.04} = 2500\Omega$$
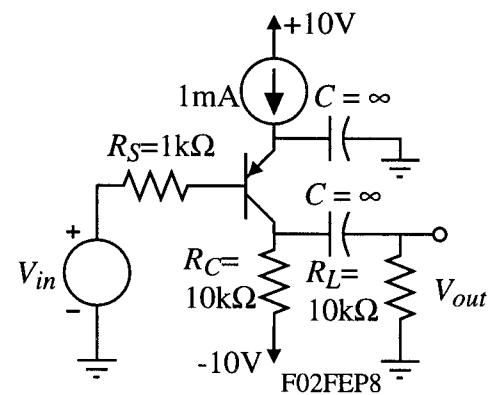
$$C_\pi = \frac{g_m}{\omega_T} - C_\mu = \frac{0.04}{2\pi \cdot 500 \times 10^6} - 2\text{pF} = 12.732\text{pF} - 2\text{pF} = 10.732 \text{ pF}$$



b.) The high-frequency, small-signal model for this problem is shown where $R_{CL} = R_C \parallel R_L = 5\text{k}\Omega$.

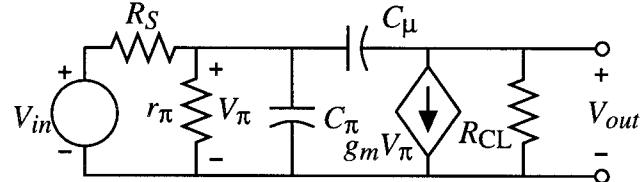The midband gain of this amplifier is given by



$$\frac{V_{out}}{V_{in}} = \left(\frac{V_{out}}{V_\pi} \right) \left(\frac{V_\pi}{V_{in}} \right) = -g_m R_C \parallel R_L \left(\frac{r_\pi}{r_\pi + R_S} \right) = (-0.01 \cdot 5\text{k}\Omega)(0.5) = -25\text{V/V}$$

$$\therefore \text{MBG} = -25 \text{ V/V}$$

Using Miller's theorem on this problem:

If $\frac{1}{\omega_H C_\mu} \gg R_C \parallel R_L$, then $C_{eq} \approx C_\pi + C_\mu (1 + g_m R_C \parallel R_L) = 10\text{pF} + 2\text{pF}(1+50) = 112\text{pF}$

We know that, $\omega_H = \frac{1}{C_{eq} (r_\pi \parallel R_S)} = \frac{1}{(112\text{pF} \cdot 500\Omega)} = 17.86 \text{ Mrads/sec.}$

$$\therefore f_H = \frac{\omega_H}{2\pi} = 2.842 \text{ MHz}$$

Note that:

$$\frac{1}{\omega_H C_\mu} = \frac{10^6}{17.86 \cdot 2} = 28.06\text{k}\Omega > 5\text{k}\Omega \text{ so that the Miller approximation (neglecting } C_\mu)$$

is valid.