

CHAPTER 18: FEEDBACK, STABILITY, AND OSCILLATORS


→ Introduction

- series-shunt
- shunt-shunt
- shunt-series
- series-series

What can feedback do??

- Increase/decrease  $R_{in}/R_{out}$
- Increase accuracy
- Remove non-linearity
- Increase  $f_H$  and decrease  $f_L$
- Create oscillators

Classical single-loop feedback

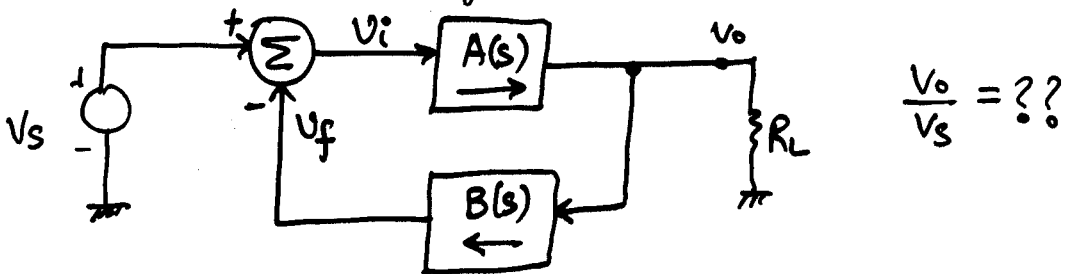


$$V_o = A(s) V_i = A(s) \cdot \{ V_s - V_f \} = A(s) \{ V_s - B(s) \cdot V_o \}$$

$$V_o = A(s) \cdot V_s - A(s) \cdot B(s) \cdot V_o$$

$$\frac{V_o}{V_s} = \frac{A(s)}{1 + A(s)B(s)} = \frac{A(s)}{1 + T(s)}$$

$$T(s) = A(s)B(s) = \text{Loop gain}$$

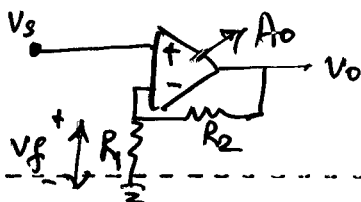
$$T(s) \gg 1 \Rightarrow \frac{V_o}{V_s} \approx \frac{A(s)}{T(s)} \approx \frac{1}{B(s)}$$



$$\Rightarrow \left. \begin{array}{l} A = A_o \\ B = \frac{R_1}{R_1 + R_2} \end{array} \right\} \rightarrow \frac{V_o}{V_s} \approx \frac{1}{B} = \frac{R_1 + R_2}{R_1}$$

Voltage Amplifiers → Series-shunt Feedback

(Input) (Output)

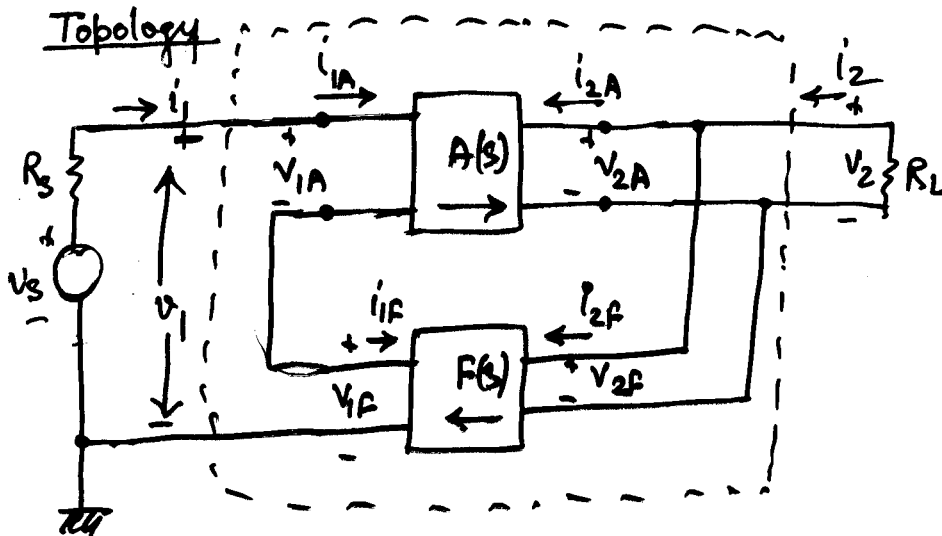

$$V_1 = V_{1A} + V_{1F} \quad ; \quad i_2 = i_{2A} + i_{2F}$$

A network

F network

$$\begin{bmatrix} V_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} V_{1A} = h_{11A} i_{1A} + h_{12A} V_{2A} \\ i_{2A} = h_{21A} i_{1A} + h_{22A} V_{2A} \end{bmatrix} + \begin{bmatrix} V_{1F} = h_{11F} i_{1F} + h_{12F} V_{2F} \\ i_{2F} = h_{21F} i_{1F} + h_{22F} V_{2F} \end{bmatrix}$$

$$V_1 = (h_{11A} + h_{11F}) i_1 + (h_{12A} + h_{12F}) V_2$$

$$i_2 = (h_{21A} + h_{21F}) i_1 + (h_{22A} + h_{22F}) V_2$$

$$h_{11T} = h_{11A} + h_{11F}$$

$$h_{12T} = \cancel{h_{12A}} + h_{12F} \equiv h_{12F}$$

$$h_{21T} = h_{21A} + \cancel{h_{21F}} \equiv h_{21A}$$

$$h_{22T} = h_{22A} + h_{22F}$$

$$V_1 = h_{11T} i_1 + h_{12T} V_2$$

$$i_2 = h_{21T} i_1 + h_{22T} V_2$$

$$\frac{V_2}{V_s} = ? \quad \text{with } R_s \text{ and } R_L$$

$$V_s = i_1 R_s + V_1 = i_1 R_s + \{ h_{11T} \cdot i_1 + h_{12F} V_2 \} = i_1 (R_s + h_{11T}) + h_{12F} V_2 \quad (1)$$

$$V_2 = -i_2 R_L \Rightarrow i_2 = -\frac{V_2}{R_L} \Rightarrow (h_{21A} \cdot i_1 + h_{22T} V_2) = -\frac{V_2}{R_L}$$

$$\downarrow$$

$$i_1 = -\frac{(h_{22T} + G_L)}{h_{21A}} \cdot V_2 \rightarrow (2)$$

$$V_s = -(R_s + h_{11T}) \underbrace{\left( \frac{h_{22T} + G_L}{h_{21A}} \right)}_{i_1} V_2 + h_{12F} V_2$$

$$\left( \frac{V_2}{V_s} \right) = \text{Closed-loop T.F} = A_{VF}$$

$$\left( \frac{V_2}{V_s} \right) = A_{VF} = \frac{-h_{21A}}{(R_s + h_{11T})(h_{22T} + G_L)}$$

$$1 + \left\{ \frac{-h_{21A}}{(R_s + h_{11T})(h_{22T} + G_L)} \right\} (h_{12F})$$

$$= \frac{A}{1 + A \cdot F}$$

$$A = \frac{-h_{21A}}{(R_s + h_{11T})(h_{22T} + G_L)} ; F = h_{12F}$$