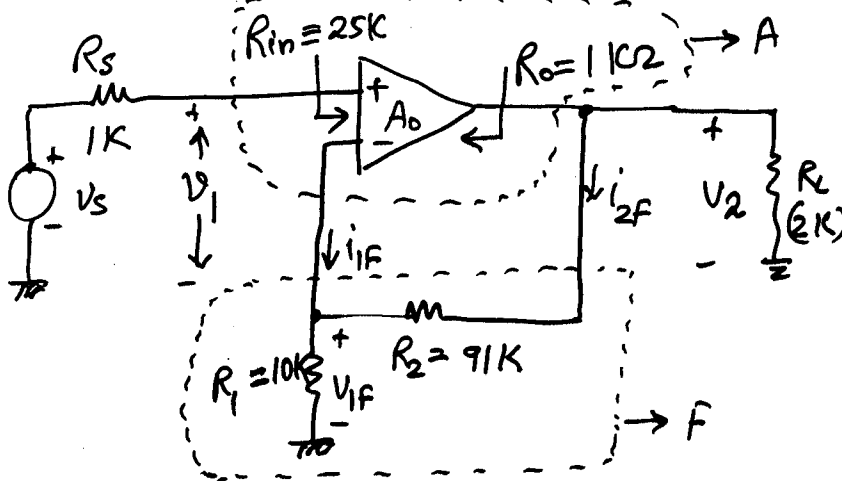


Example of series-shunt feedback



$A_0 = 10^4 \text{ V/V}$

- Find
- A_V (open-loop gain) = $\left. \frac{V_2}{V_s} \right|_{\text{open-loop}}$ (without feedback)
 - F (feedback factor)
 - A_{VF} (closed-loop gain) = $\left. \frac{V_2}{V_s} \right|_{\text{(with feedback)}}$

$$A = \frac{-h_{21A}}{(R_s + h_{11T})(G_L + h_{22T})}$$

$$F = h_{12F}$$

$$h_{11T} = h_{11A} + h_{11F} = 25\text{K}\Omega + \left. \frac{V_{1F}}{i_{1F}} \right|_{V_2=0} = 25\text{K}\Omega + R_1 \parallel R_2 = 34.01\text{K}\Omega$$

$$h_{22T} = h_{22A} + h_{22F} \quad ; \quad h_{22F} = \left. \frac{i_{2F}}{V_2} \right|_{i_{1F}=0} = \frac{1}{R_1 + R_2} = \frac{1}{101\text{K}}$$

$$h_{12F} = \left. \frac{V_{1F}}{V_2} \right|_{i_{1F}=0} = \frac{R_1}{R_1 + R_2} = 0.099 = F = \beta$$


$$h_{21A} = \frac{i_2}{i_1} \Big|_{V_2=0}$$

$$A_{VF} = \frac{A_v}{1 + (A_v)F}$$

$$F = h_{21F} = 0.099$$

$$A_v = ??$$

Open-loop

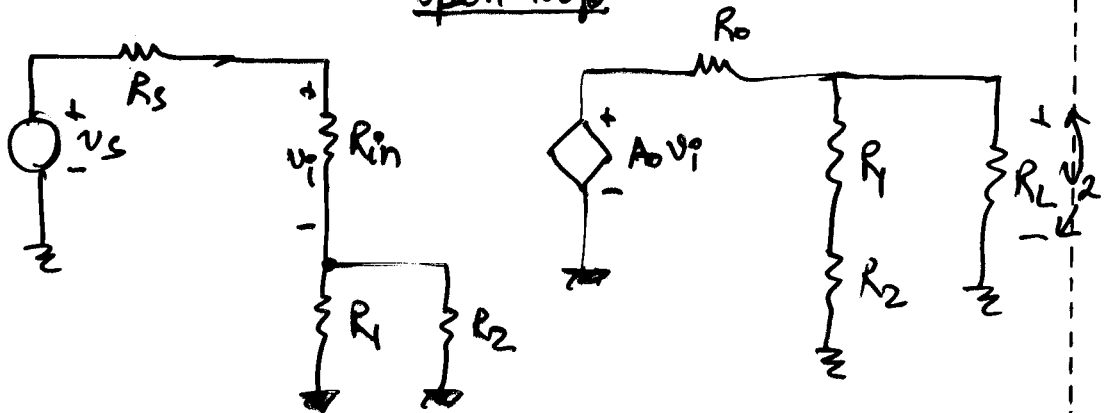

$$A_v = \frac{v_2}{v_s} = \left(\frac{R_{in}}{R_s + R_{in} + R_1 \parallel R_2} \right) A_o \cdot \left(\frac{(R_1 + R_2) \parallel R_L}{R_o + (R_1 + R_2) \parallel R_L} \right)$$

$$= 4730 \text{ V/V}$$

$$A_{VF} = \frac{A_v}{1 + F A_v} = \frac{4730}{1 + 0.099 \cdot 4730} \approx 10.08 \text{ V/V}$$