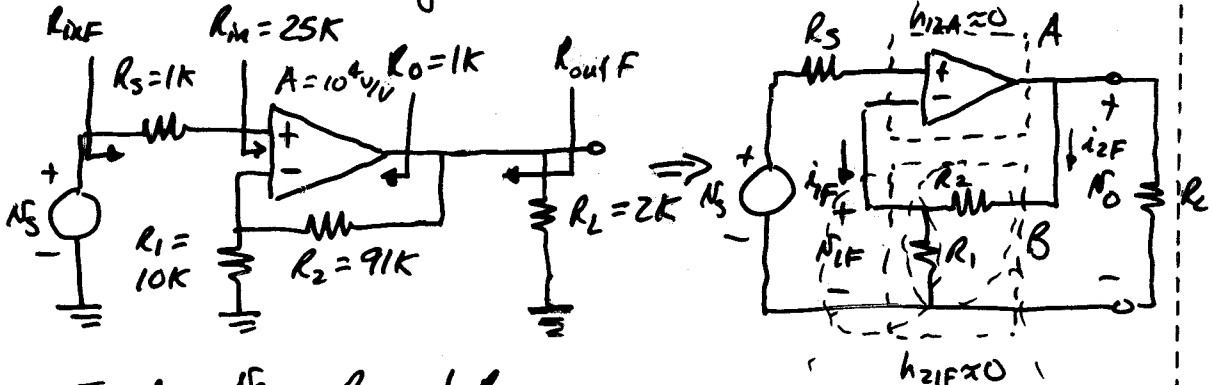


Example of Series-Shunt Feedback using an Op Amp

Consider the following series-shunt feedback circuit:



Find  $\frac{N_0}{N_S}$ ,  $R_{INF}$  &  $R_{OUT F}$

From previous work we know that,

$$\frac{N_0}{N_S} = \frac{h_{21A}}{h_{12F}h_{21A} - (R_S + h_{11T})(G_L + h_{22T})} = \frac{A}{1 + AF}$$


where  $A = \frac{-h_{21A}}{(R_S + h_{11T})(G_L + h_{22T})}$  and  $F = h_{21F}$

$$h_{11F} = \left. \frac{N_{1F}}{i_{1F}} \right|_{N_0=0} = R_1 || R_2 = 9.01K \quad h_{22F} = \left. \frac{i_{2F}}{N_0} \right|_{i_{1F}=0} = \frac{1}{R_1 + R_2} = \frac{1}{101K}$$

$$h_{12F} = \left. \frac{N_{1F}}{N_0} \right|_{i_{1F}=0} = \frac{R_1}{R_1 + R_2} = 0.099$$

$$\begin{cases} N_1 = h_{11}i_1 + h_{12}N_2 \\ i_2 = h_{21}i_1 + h_{22}N_2 \end{cases}$$

A = ? Use the following model for A

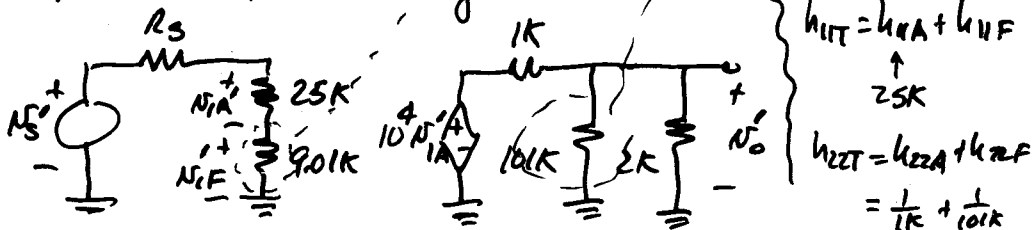


$$\begin{cases} h_{11T} = h_{11A} + h_{11F} \\ \quad \quad \quad \uparrow \\ \quad \quad \quad 25K \\ h_{22T} = h_{22A} + h_{22F} \\ \quad \quad \quad \quad \quad \quad \uparrow \\ \quad \quad \quad \quad \quad \quad \frac{1}{1K} + \frac{1}{101K} \end{cases}$$

$$A = \frac{N_0'}{N_S'} = \left( \frac{25K}{1K + 25K + 9.01K} \right) (10^4) \left( \frac{2K || 101K}{1K + 2K || 101K} \right) = 4730 V/V$$

$$\beta = h_{12F} = 0.099$$

$$\therefore \frac{N_0}{N_S} = \frac{A}{1 + \beta A} = \frac{4730}{1 + 4730(0.099)} = \underline{\underline{10.08 V/V}}$$

$R_{inF} = ?$

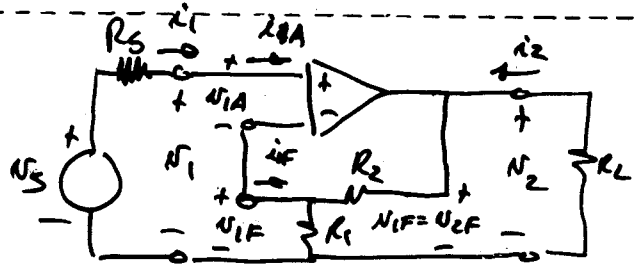

$$N_S = N_1 = (R_S + h_{11T})i_1 + h_{12T}N_2 \quad N_2 = -R_L i_2$$

$$i_2 = h_{21T}i_1 + h_{22T}N_2 \quad \leftarrow \quad i_2 = G_L N_2$$

$$-G_L N_2 = h_{21T}i_1 + h_{22T}N_2$$

$$\text{at } 0 = (h_{21F} + h_{21A})i_1 + (h_{22} + G_L)N_2$$

$$N_1 = h_{11T}i_1 + h_{12F}N_2 \quad \leftarrow \quad N_1$$

$$0 = h_{21A}i_1 + (h_{22} + G_L)N_2$$

$$\begin{cases} N_S = (R_S + h_{11T})i_1 + h_{12F}N_2 \\ 0 = h_{21A}i_1 + (h_{22} + G_L)N_2 \end{cases} \quad \frac{N_S}{i_1} = ?$$


$$\frac{N_S}{i_1} = R_{inF} = R_S + h_{11T} + \frac{-h_{21A} h_{12F}}{(h_{22} + G_L)}$$

$$= (R_S + h_{11T}) \left[ 1 + \frac{-h_{21A} h_{12F}}{(R_S + h_{11T})(h_{22} + G_L)} \right] = R_{in}(1 + AF)$$

$A F = AB$

$R_{inF} = \underline{16.47 M\Omega}$

$R_{outF} = ?$

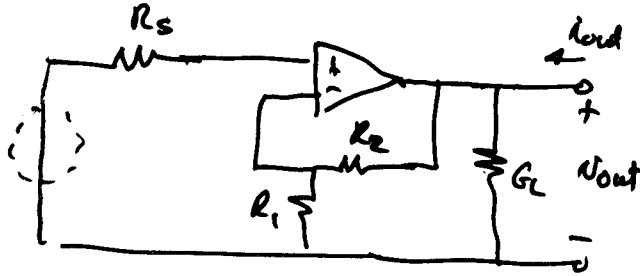


$R_{outF} =$

$$= \frac{662 \Omega}{1 + (4730)(0.099)} = \underline{1.41 \Omega}$$

◦◦ The general approach to analyzing series-shunt feedback networks is ◦◦

- 1.) Find  $h_{iif}$  (input resistance of the F network with the output short-circuited)
- 2.) Find  $h_{oof}$  (output conductance of the F network with the input open-circuited)
- 3.) Find  $h_{vof} = \beta = F$  (voltage gain from output to input with input open-circuited)
- 4.) Use the A circuit including the loading of the F circuit ( $h_{iif}$  &  $h_{oof}$ ) to find A.
- 5.)  $A_F = \frac{A}{1 + AF} = \frac{A}{1 + AB}$
- 6.)  $R_{inF} = (R_s + h_{iif})(1 + AF) = (R_s + h_{iif})(1 + AB)$
- 7.)  $h_{outF} = \frac{(h_{oof} + G_L)}{1 + AF} = \frac{h_{oof} + G_L}{1 + AB}$

Example

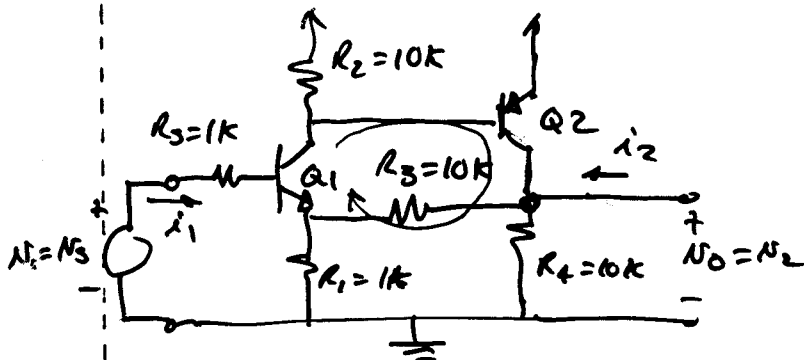

If  $\beta_1 = \beta_2 = 100$  &  $r_{\pi 1} = r_{\pi 2} = 10k$ , find  $\frac{v_2}{v_1}$ ,  $\frac{v_1}{i_1}$  and  $\frac{v_2}{i_2}$

To be continued ...