

- Units of A? Should be V/V.

$$A = \frac{-h_{21A}}{(R_S + h_{11T})(G_L + h_{22T})} \frac{(A/A)}{(R_S)(V_S)} \rightarrow \frac{A \cdot R_S}{A \cdot R_S} = \frac{V}{V}$$

- Quiz 9 - High Frequency Response (Quiz? 11/22 at 7pm)


Series-Shunt Feedback Example

If $\beta_1 = \beta_2 = 100$ and


$r_{\pi 1} = r_{\pi 2} = 10k\Omega$, find

the value of $\frac{N_2}{N_S}$,

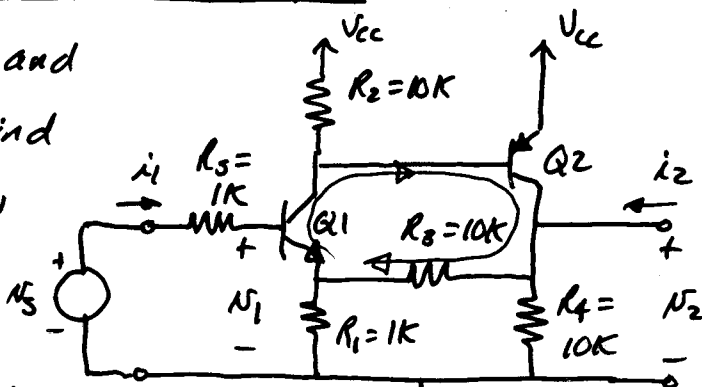$\frac{N_S}{N_1}$, and $\frac{N_2}{N_2}$.



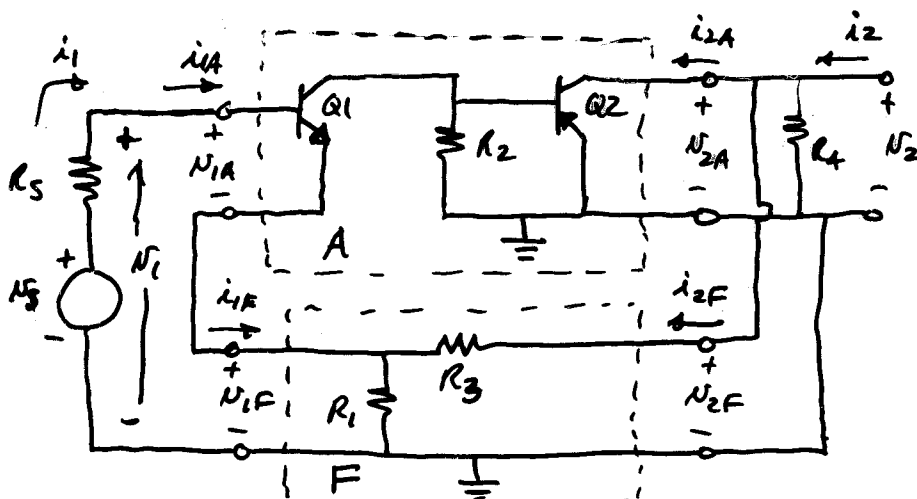Redraw to help identify the A & F circuits: \equiv



Note: $i_1 = i_{1A} \approx i_{1F}$ and $N_2 = N_{2A} = N_{2F}$
 $N_1 = N_{1A} + N_{1F}$ $i_2 = i_{2A} + i_{2F}$

1.) $h_{11F} = \left. \frac{N_{1F}}{i_{1F}} \right|_{N_{2F}=0} = R_1 || R_3 = 0.91k$

3.) $h_{12F} = \left. \frac{N_{1F}}{N_{2F}} \right|_{i_{1F}=0}$


2.) $h_{22F} = \left. \frac{i_{2F}}{N_{2F}} \right|_{i_{1F}=0} = \frac{1}{R_1 + R_3} = \frac{1}{11k}$

$= \frac{R_1}{R_1 + R_3} = \frac{1}{11}$



(If $AF \gg 1$, then $AF \approx \frac{1}{h_{12F}} = 11 \text{ V/V} ??$)

Time out:

F network -

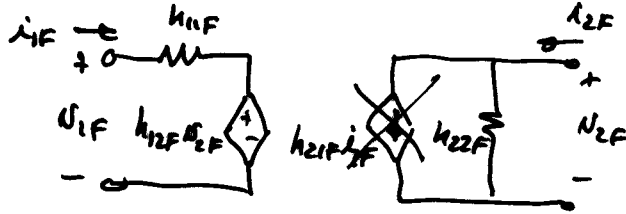


a.) Redrawing the previous ckt. -

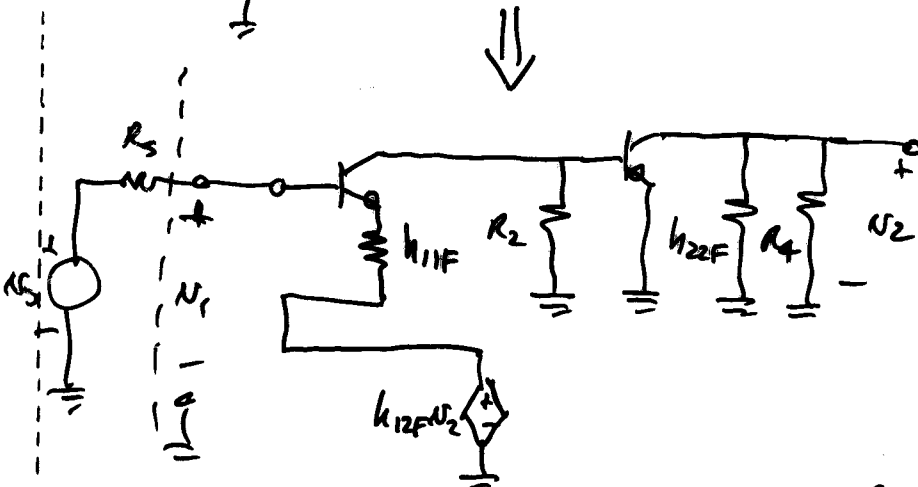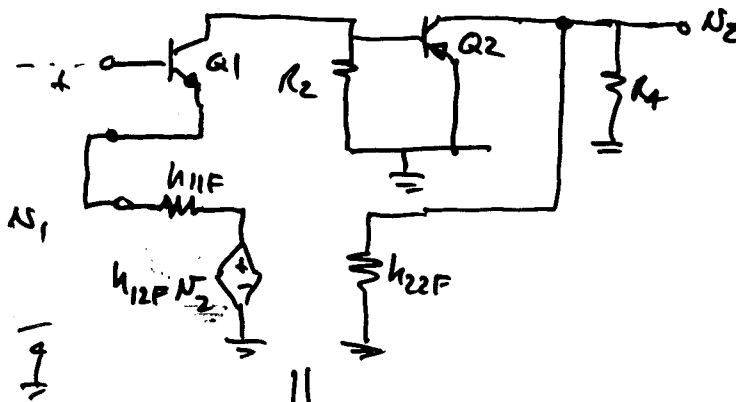


Now, if $h_{22F} = 0$, the loop is open (use primed variables)

c. The ckt. to find A is -

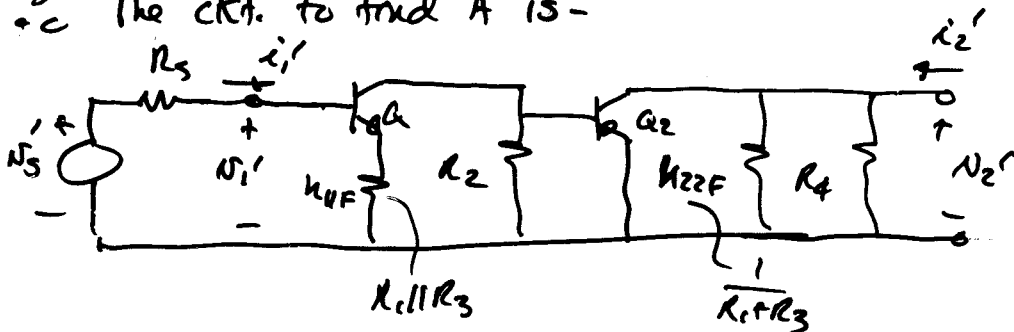

4.) Cont'd

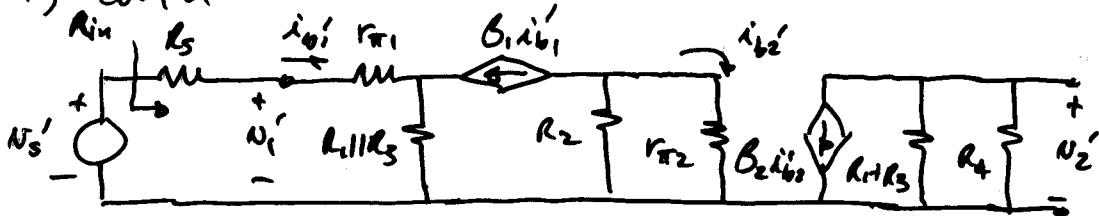

$$A = \frac{N_2'}{N_s'} = \left[-\beta_2 R_4 \parallel (R_1 + R_3) \right] \left[-\frac{\beta_1 R_2}{r_{\pi 2} + R_2} \right] \left[\frac{1}{R_s + r_{\pi 1} + (1 + \beta_1) R_1 \parallel R_3} \right]$$

$$(A = 255 \frac{V}{V}) \quad (F = \frac{1}{17})$$

For neg. fb. $AF > 0$ $AF = \frac{255}{17} = 23.17$

$$R_{in} = R_s + r_{\pi 1} + (1 + \beta_1) R_1 \parallel R_3 = 102.8 \text{ k}\Omega$$

$$R_{out} = (R_1 + R_2) \parallel R_4 = 5.23 \text{ k}\Omega$$


5.) Go back to closed loop -

$$A_F = \frac{A}{1 + AF} = \frac{255}{1 + 23.17} = \frac{255}{24.17} = 10.54 \text{ V/V} = \frac{N_o}{N_s} \approx \frac{1}{112F}$$

$$\frac{N_s}{i_1} = R_{in} F = R_{in} (1 + AF) = 102.8 \text{ k}\Omega (24.17) = \underline{\underline{2.455 \text{ M}\Omega}}$$

$$R_{out} = \frac{N_2}{i_2} = \frac{R_{out}}{1 + AF} = \frac{5230 \Omega}{24.17} = \underline{\underline{216 \Omega}}$$

Recall op amp cts.

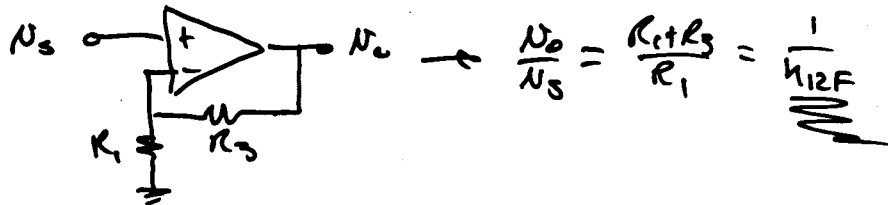

General ApproachLet $x = g, h, y$ or z

- 1.) Find N_{11F}
- 2.) Find N_{22F}
- 3.) Find N_{12F}

} assume $N_{21F} \approx 0$ ($N_{21F} \ll N_{21A}$)

- 4.) Find A (the open loop amplifier gain) incorporating N_{11F} & N_{22F} and the correct N_{21} variable.

5.) $A_F = \frac{A}{1+AF}$

$$6.) R_{inF} = \begin{cases} (R_s + N_{11F})(1+AF) & \text{if series at input} \\ \frac{1}{(G_s + N_{11F})(1+AF)} & \text{if shunt at input} \end{cases}$$

$$R_{inF} = R_{in}(1+AF) \text{ or } \frac{R_{in}}{1+AF}$$

$$R_{outF} = \begin{cases} \frac{1}{(G_L + N_{22F})(1+AF)} & \text{shunt at output} \\ (R_L + N_{22F})(1+AF) & \text{series " " } \end{cases}$$

Feedback Topology	Two-Port Parameter
Shunt-shunt (Transresistance Amplifier)	$i_1 = g_{11} v_1 + g_{12} v_2$ $i_2 = g_{21} v_1 + g_{22} v_2$
Shunt-series (Current Amplifier)	$i_1 = g_{11} v_1 + g_{12} i_2$ $v_2 = g_{21} v_1 + g_{22} i_2$
Series-series (Transconductance Amplifier)	$v_1 = g_{11} i_1 + g_{12} i_2$ $v_2 = g_{21} i_1 + g_{22} i_2$
Series-shunt (Voltage amplifier)	$v_1 = h_{11} i_1 + h_{12} v_2$ $i_2 = h_{21} i_1 + h_{22} v_2$