

Note: Quiz 12 - 6:30pm, Nov. 22, IEEE SCS/CAS Chapter Lecture - Dr. Eric Vittor. Quiz will be to attend and submit to me by 11/24 a summary of what was said and your impressions.

Shunt-Shunt Feedback (Transresistance Amplifiers)

Approach to analyzing:

$$1.) \text{Find } \gamma_{11F} = \frac{i_{1F}}{N_{1F}} \Big|_{N_{2F}=0}$$

$$2.) \text{Find } \gamma_{22F} = \frac{i_{2F}}{N_{2F}} \Big|_{N_{1F}=0}$$

$$3.) \text{Find } \gamma_{12F} = \frac{i_{1F}}{N_{2F}} \Big|_{N_{1F}=0}$$

$$4.) \text{Find } A \text{ (note: it will have units of } \frac{\text{Volts}}{\text{Amps}} = \Omega \text{)}$$


Example

Find $\frac{V_{out}}{V_{in}}$, R_{in} ,

and R_{out} if

$$g_{m1} = g_{m2} = g_{m3} = 0.2 \text{ mS}$$
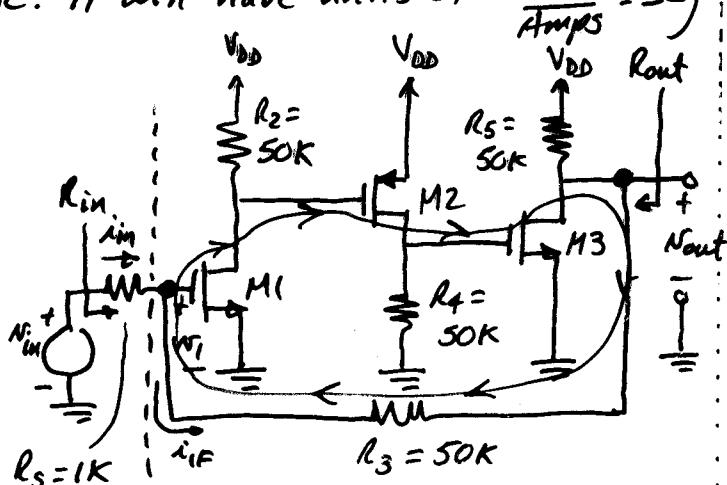
$$\text{and } r_{ds1} = r_{ds2} = r_{ds3} = \infty.$$





$$1.) \gamma_{11F} = \frac{i_{1F}}{R_3} = \frac{1}{50K}$$

$$2.) \gamma_{22F} = \frac{i_{2F}}{R_3} = \frac{1}{50K}$$

$$3.) \gamma_{12F} = \frac{i_{1F}}{N_{2F}} \Big|_{N_{1F}=0} = -\frac{1}{50K}$$

4.) A (open loop)

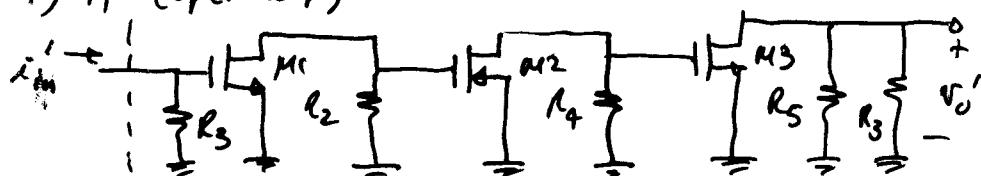

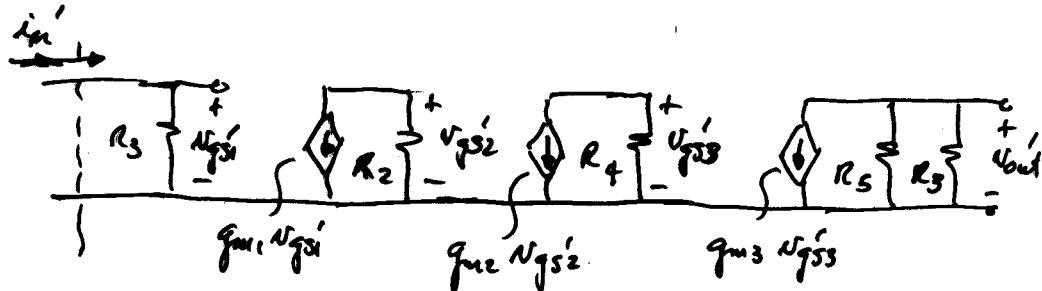Example - Cont'd

$$\begin{aligned}
 A &= \frac{V_{out}'}{i_{in}} = \left(\frac{N_{g1}'}{N_{g2}} \right) \left(\frac{N_{g2}'}{N_{g3}} \right) \left(\frac{N_{g3}'}{N_{g4}} \right) \left(\frac{N_{g4}'}{i_{in}} \right) \\
 &= (-q_{m3} R_3 || R_5) (-q_{m2} R_2) (-q_{m1} R_1) (R_3) = -25 M\Omega
 \end{aligned}$$


5.) $A_F = \frac{V_{out}}{i_{in}} = \frac{A}{1+AF} = \frac{-25 M\Omega}{1 + 25 M\Omega} = \frac{-25 M\Omega}{50 M\Omega} = -49.9 K\Omega$

$$R_{inF} = \frac{R_{in}}{1+AF} = \frac{R_1}{501} = \underline{\underline{99.85\Omega}}$$

$$R_{outF} = \frac{R_{out}}{1+AF} = \frac{R_3 || R_5}{501} = \underline{\underline{49.9\Omega}}$$

6.) Post-processing

$$\frac{N_{out}}{N_{in}} = ?$$

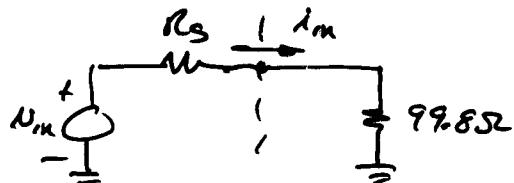

$$i_{in} = \frac{N_{in}}{R_3 + R_{inF}} = \frac{N_{in}}{1099.8}$$


$$\therefore \frac{N_{out}}{N_{in}} = \left(\frac{N_{out}}{i_{in}} \right) \left(\frac{i_{in}}{N_{in}} \right) = (-49.9 K\Omega) \frac{1}{1.099 K\Omega}$$

$$\frac{N_{out}}{N_{in}} = \underline{\underline{-45.5 V}}$$

SHUNT INPUT FEEDBACK VERSUS A THEVINEN AND NORTON INPUT SOURCE

This example illustrates how to apply shunt-input feedback with either a Thevenin or Norton input source. The inverting voltage amplifier with a gain of K and infinite input and zero output resistance is shown in a shunt-shunt configuration but all results of this example are also applicable to shunt-series.

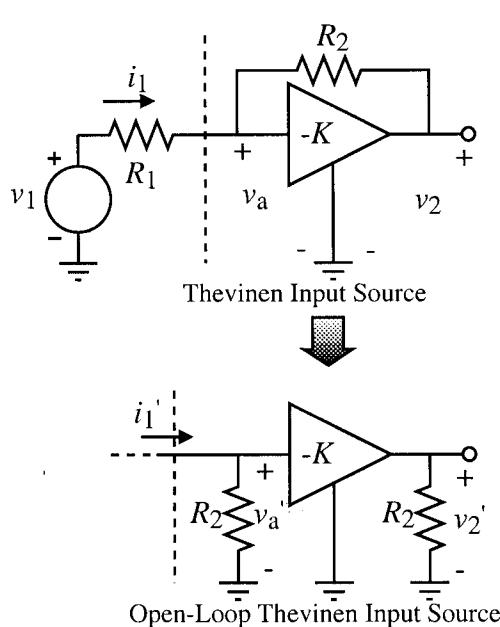In the following, we will find the voltage gain, v_2/v_1 , and the input resistance defined as v_1/i_1 . The results for either case will be shown to be the same. The vertical dotted line illustrates the boundary for the feedback analysis method for either case.




$$\beta = \frac{-1}{R_2}$$

$$v_2' = -KR_2 i_1' \Rightarrow \frac{v_2'}{i_1'} = R_T = -KR_2$$

$$\frac{v_2}{i_1} = \frac{-KR_2}{1 + (-KR_2) \left(\frac{-1}{R_2} \right)} = \frac{-KR_2}{1 + K}$$

$$\frac{v_a}{i_1} = R_{inF} = \frac{R_2}{1 + K}$$
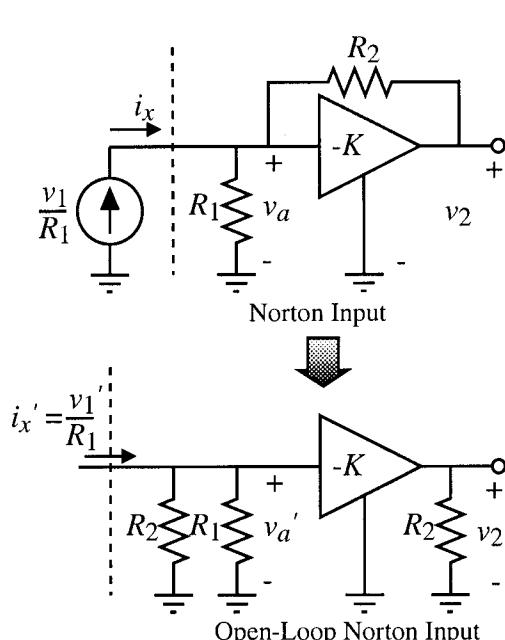
$$\boxed{\frac{v_1}{i_1} = R_1 + R_{inF} = R_1 + \frac{R_2}{1 + K}}$$



$$\beta = \frac{-1}{R_2}$$

$$v_2' = -K(R_1 \| R_2) i_x' \Rightarrow \frac{v_2'}{i_x'} = R_T = -K(R_1 \| R_2)$$

$$\frac{v_2}{i_1} = \frac{-K(R_1 \| R_2)}{1 + (-K(R_1 \| R_2)) \left(\frac{-1}{R_2} \right)} = \frac{-K \frac{R_1 R_2}{R_1 + R_2}}{1 + K \frac{R_1}{R_1 + R_2}}$$

$$\frac{v_a}{i_x} = R_{inF} = \frac{\frac{R_1 R_2}{R_1 + R_2}}{1 + K \frac{R_1}{R_1 + R_2}}$$

$$\frac{v_a}{i_x} = \frac{v_a R_1}{v_1} \text{ which gives,}$$

$$\frac{v_2}{v_1} = \frac{v_2}{i_1} \frac{i_1}{v_1} = \left(\frac{-KR_2}{1+K} \right) \left(\frac{1}{R_1 + \frac{R_2}{1+K}} \right)$$

$$= \frac{-KR_2}{R_1(1+K) + R_2} = \frac{-KR_2}{R_1 + R_2 + KR_1}$$

$$\boxed{\frac{v_2}{v_1} = \frac{R_2}{R_1} \frac{\frac{KR_1}{R_1+R_2}}{1 + \frac{KR_1}{R_2+R_1}}}$$

$$v_a = \frac{\frac{R_2}{R_1+R_2}}{1 + K \frac{R_1}{R_1+R_2}} v_1$$

i_1 can be expressed from the Thevenin form as,

$$i_1 = \frac{v_1}{R_1} - \frac{v_a}{R_1} = \frac{v_1}{R_1} - \frac{\frac{R_2}{R_1+R_2}}{1 + K \frac{R_1}{R_1+R_2}} \frac{v_1}{R_1}$$

$$\therefore \frac{i_1}{v_1} = \frac{1}{R_1} \left(1 - \frac{\frac{R_2}{R_1+R_2}}{1 + K \frac{R_1}{R_1+R_2}} \right)$$

$$= \frac{1}{R_1} \left(\frac{1 + K \frac{R_1}{R_1+R_2} - \frac{R_2}{R_1+R_2}}{1 + K \frac{R_1}{R_1+R_2}} \right) = \frac{1+K}{R_1+R_2+KR_1}$$

Finally,

$$\boxed{\frac{v_1}{i_1} = R_1 + \frac{R_2}{1+K}}$$

Lastly,

$$\frac{v_2}{v_1} = \frac{v_2}{i_x} \frac{i_x}{v_1} = \frac{\frac{R_1 R_2}{R_1+R_2}}{1 + K \frac{R_1}{R_1+R_2}} \left(\frac{1}{R_1} \right)$$

$$\boxed{\frac{v_2}{v_1} = \frac{R_2}{R_1} \frac{\frac{KR_1}{R_1+R_2}}{1 + \frac{KR_1}{R_2+R_1}}}$$

So the results are identical although one method is a lot more work than the other.