

Quiz #10 - Series-shunt feedback

Quiz #11 - ? feedback

A Simple Approach to the Analysis of Feedback Amplifiers

- 1.) Trace the loop (direction and \pm feedback)
- 2.) Identify the F network (feedback path)
- 3.) Find $M_{12F} = F$
- 4.) Find A by:

a.) At the input -

The loading of the fb. network on the amplifier is found by looking in the fb. network and shorting (opening) the output if the output of the fb. amplifier is shunt (series).

b.) At the output -

The loading of the fb. network on the amplifier is found by looking back into the fb. network with the input short-circuited (open circuited) if the input of the feedback amplifier is shunt (series).

5.) Helps -




a.) $AF > 0$

b.) Units of A and F

Feedback	A	F
Series-shunt	V/V	V/V
Shunt-shunt	V/A	A/V
Shunt-series	A/A	A/A
Series-series	A/V	V/A

Series-Series Feedback Example

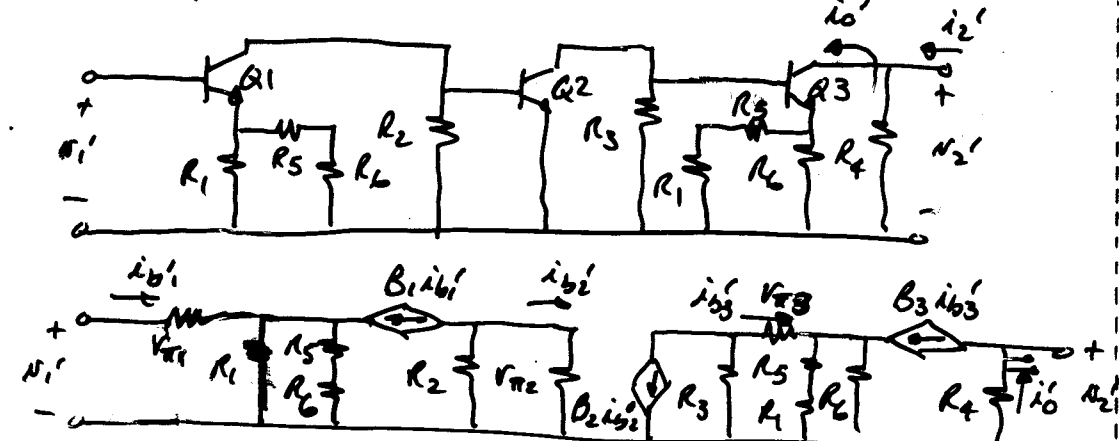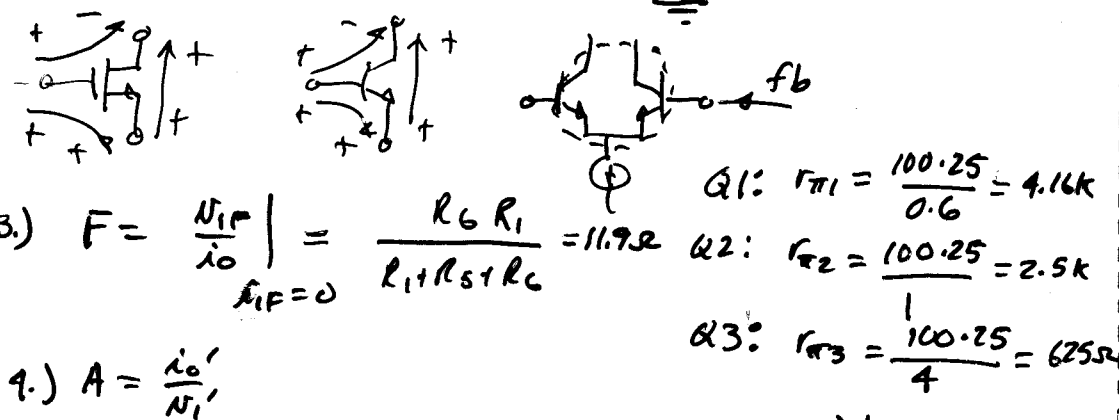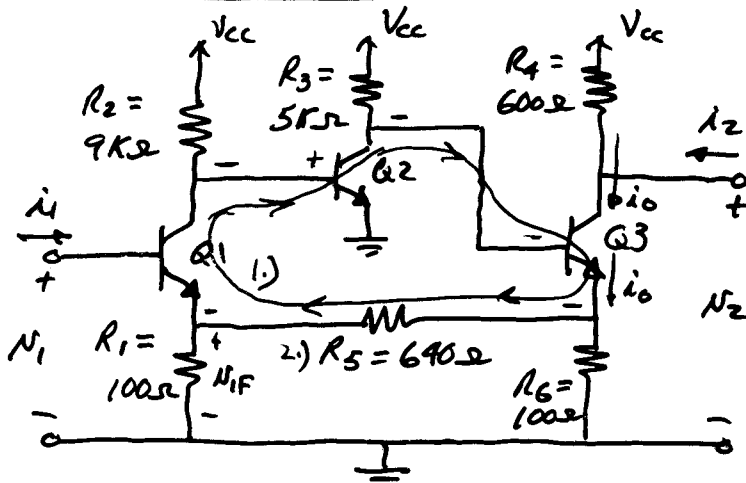If $\beta = h_{fe} = 100$
 and $I_{C1} = 0.6 \text{ mA}$,
 $I_{C2} = 1 \text{ mA}$, and
 $I_{C3} = 4 \text{ mA}$ find
 $\frac{N_2}{N_1}$, $\frac{N_1}{i_1}$ and
 $\frac{N_2}{i_2}$ using fb.
 analysis methods.



$$A = \frac{i_o'}{N_1'} = \left(\frac{i_o'}{i_{b3}'} \right) \left(\frac{i_{b3}'}{i_{b2}'} \right) \left(\frac{i_{b2}'}{i_{b1}'} \right) \left(\frac{1}{r_{in}} \right)$$

$$= (\beta_3) \left(\frac{-\beta_2 R_3}{R_3 + r_{\pi 3} + (1 + \beta_3) [R_6 || (R_1 + R_5)]} \right) \left(\frac{-\beta_1 R_2}{R_2 + r_{\pi 2}} \right) \left(\frac{1}{r_{\pi 1} + (1 + \beta_1) [R_1 || (R_5 + R_6)]} \right)$$

$$= (100) (-34.43) (-78.3) \left(\frac{1}{12.97 \text{ k}} \right) = 20.78 \text{ MV}$$

$R_O = R_4 + \infty = \infty$???

5.) Back to closed loop

$$A_F = \frac{i_o}{N_i} = \frac{A}{1+AF} = \frac{20.78}{1+(20.78)(11.9)} = \frac{20.78}{1+247.2} = 0.0837 \frac{A}{V}$$

6.) Post processing -

$$\frac{N_1}{\lambda_1} = R_{in}(1+AF) = 12.97k(1+247.2) = \underline{\underline{3.22M\Omega}}$$


$$\frac{N_2}{\lambda_2} = \frac{-i_o R_f}{N_i} = \left(\frac{i_o}{N_i}\right)(-R_f) = \underline{\underline{-50.2 \frac{V}{V}}}$$

$$\frac{N_2}{\lambda_2} = R_f = \underline{\underline{600\Omega}}$$

Principle: If R_{in} or R_o is not in the feedback, it is not influenced by the feedback.

Proof:

$$R_{outF} = R_o(1+AF)$$

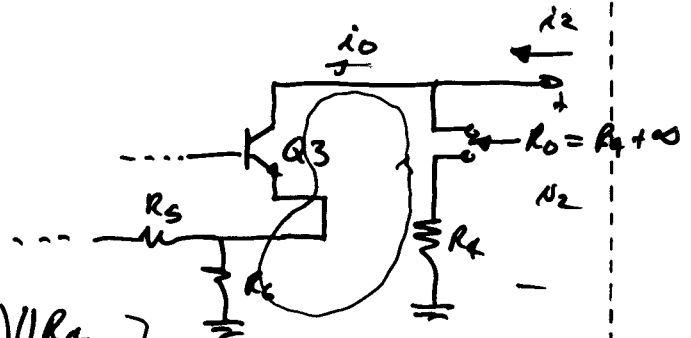

$$R_{out} = \frac{N_2}{\lambda_2} = (R_{outF} - R_f) \parallel R_f$$

$$R_{outF} = 248.2 \times \infty = \infty$$

$$R_{out} = \infty \parallel R_f = \underline{\underline{R_f}}$$


ANALYSIS OF TRANSISTOR FEEDBACK AMPLIFIERS

Steps In Analyzing Transistor Feedback Amplifiers

1. Identify the topology.
2. Determine whether the feedback is positive or negative.
3. Open the loop and calculate A , β , R_i , and R_o .
4. Use the Table to find A_f , R_{if} and R_{of} or A_F , R_{iF} , and R_{oF} .
5. Use the information in 4.) to find whatever is required (v_{out}/v_{in} , R_{in} , R_{out} , etc.)

Generic Transistor Concept

Properties of a Generic Transistor

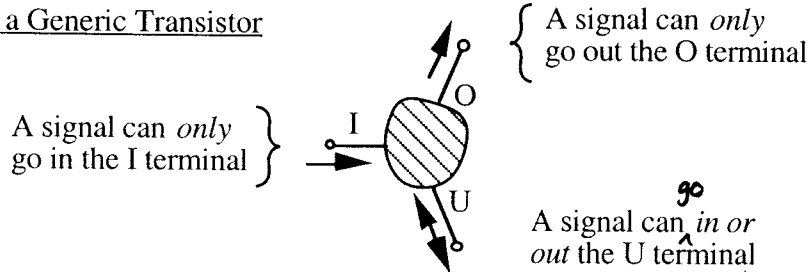


Identification of the Feedback Topology


Isolate the input and output transistor(s) and apply the following identification.

Input


Series:

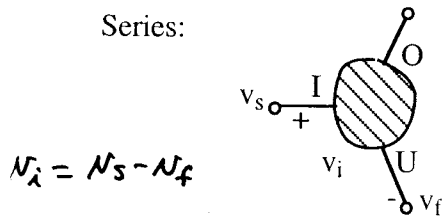


or

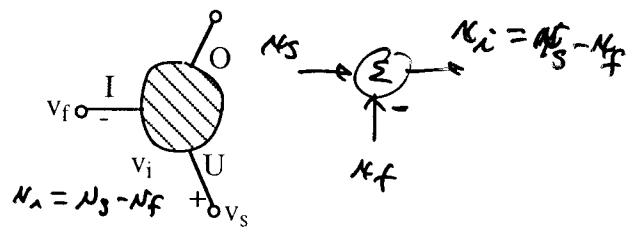

Shunt:

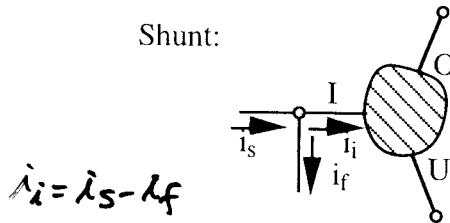


or

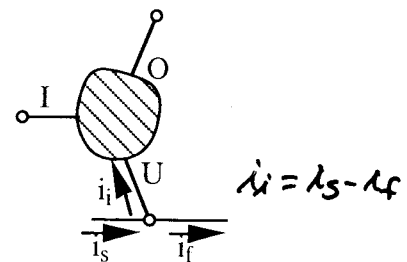


Output


Series:

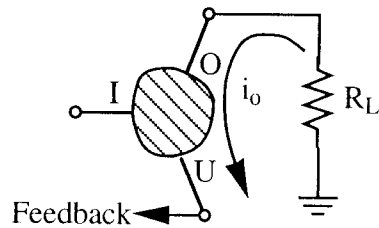


or

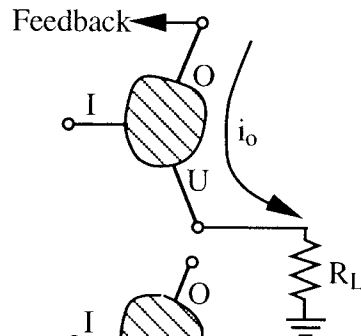

Shunt:

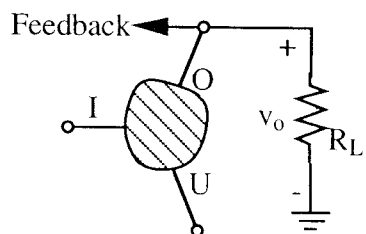


or

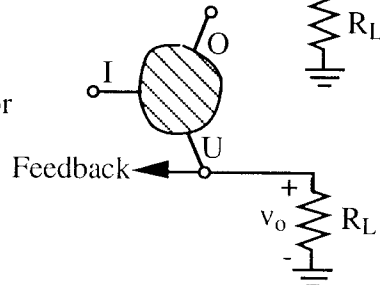

EXAMPLE OF FEEDBACK TOPOLOGY IDENTIFICATION


Use the rules of identifying feedback topologies to identify the four different topologies for the circuits shown below.

Circuits 1 and 2

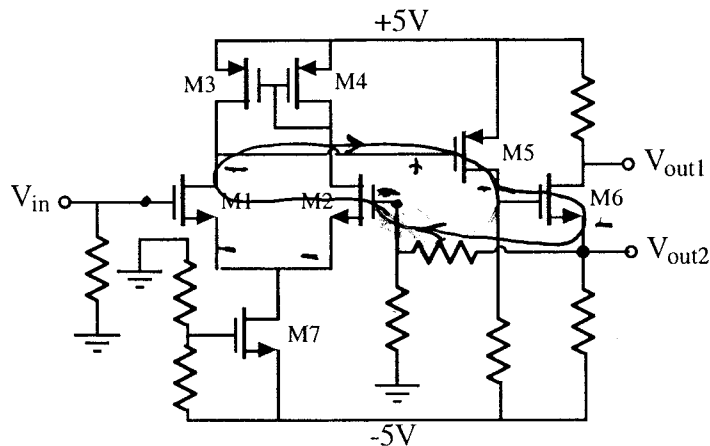

*Series - shunt (V_{out2})
Series - series (V_{out1})*

Circuits 3 and 4

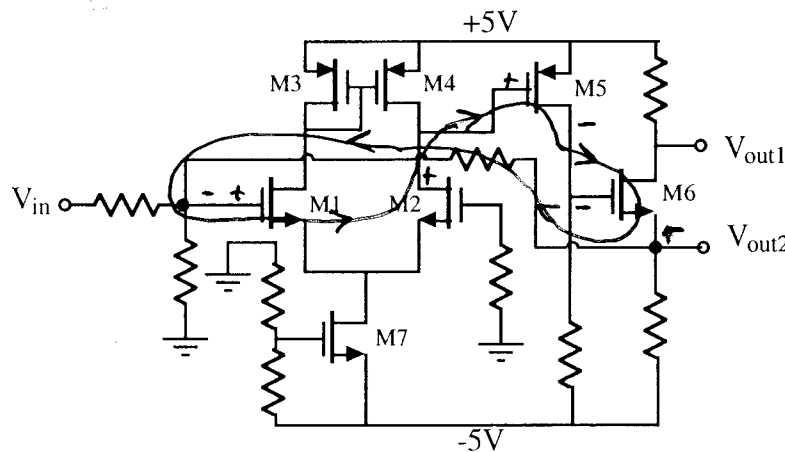

*(shunt - series)
(shunt - shunt)*